

MAHA BARATHI ENGINEERING COLLEGE

NH-79, SALEM-CHENNAI HIGHWAY, A.VASUDEVANUR, CHINNASALEM (TK), KALLAKURICHI (DT) 606 201.

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

Accredited by NAAC and Recognized under section 2(f) & 12(B) status of UGC, New Delhi

www.mbec.ac.in | Ph: 04151-256333, 257333 | E-mail: mbec123@gmail.com



DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

EC 3271 CIRCUITS ANALYSIS LAB MANUAL

I Year/ II Semester B.E ECE

Regulation 2021

(As Per Anna University, Chennai syllabus)

EC3271 CIRCUITS ANALYSIS LABORATORY

List of Experiments

1. A. Verification of Thevenin Theorems.
B. Verification of Norton's Theorems.
2. A. Verification of KVL
B. Verification of KCL.
3. Verification of Superposition Theorem.
4. A. Verification of Maximum Power Transfer
B. Verification of reciprocity Theorems.
5. Frequency response of series & parallel resonance circuits.
6. Transient analysis of RL and RC circuits

INDEX

Expt.No.	NAME OF THE EXPERIMENT	Pg.No
1a.	Verification of Thevenin's Theorem	
1b.	Verification of Norton's Theorems	
2a.	Verification of KVL	
2b.	Verification of KCL.	
3.	Verification of Superposition Theorem.	
4a.	Verification of Maximum Power Transfer	
4b.	Verification of reciprocity Theorems	
5	Frequency response of series & parallel resonance circuits	
6	Transient analysis of RL and RC circuits	

VERIFICATION OF THEVENIN'S THEOREM

EX.NO:1(a)

AIM:

To verify the Thevenin's theorem for the given circuit.

APPARATUS REQUIRED:

S.NO	APPARATUS	TYPE	RANGE	QUANTITY
1	RPS	DC	(0-30)V	1
2	Resistor	-	1KΩ	3
3	Ammeter	DC	(0-10)mA	1
4	Breadboard	-	-	1
5	Connecting wires	-	-	Few


THEORY:

THEVENIN'S THEOREM:

Any linear active network with output terminals C and D can be replaced by a single voltage source ($V_{Th} = V_{OC}$) in series with a single impedance ($Z_{Th} = Z_i$).

V_{Th} is the Thevenin's voltage. It is the voltage between the terminals C and D on open circuit condition. Hence it is called open circuit voltage denoted by V_{OC} .

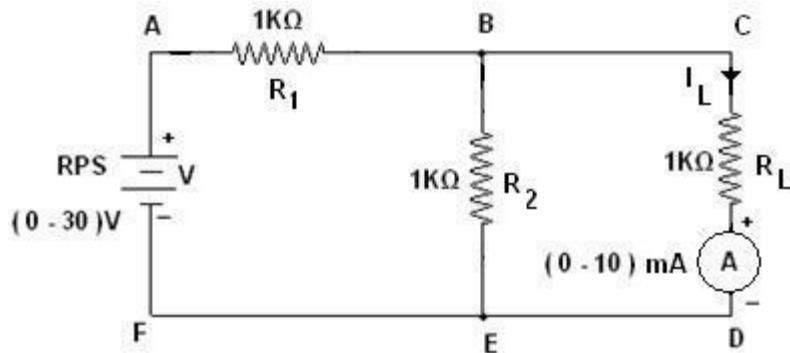
Z_{Th} is called Thevenin's impedance. It is the driving point impedance at the terminals C and D when all the internal sources are set to zero. In case of DC Z_{Th} is replaced by R_{Th} .



Circuit Diagram for Thevenin's Theorem


CALCULATION:

The Thevenin's equivalent circuit is,

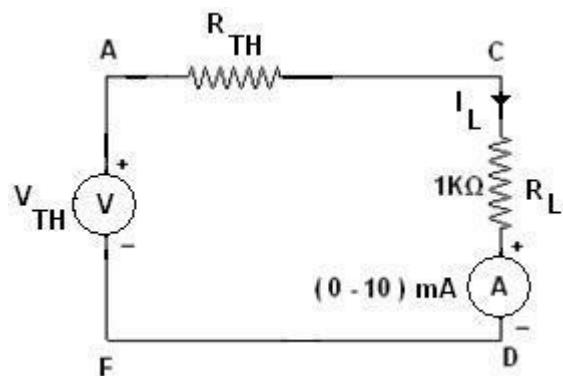

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

To Find RTH:

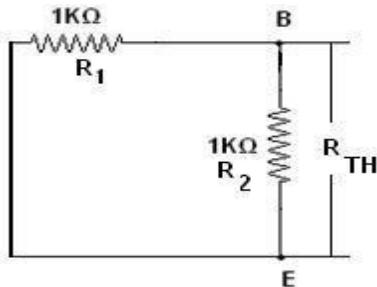


$$R_1 = 1\text{K } \Omega ; R_2 = 1\text{K } \Omega$$

; RTH =

$$\frac{R_1 * R_2}{R_1 + R_2}$$

To Find VTH:

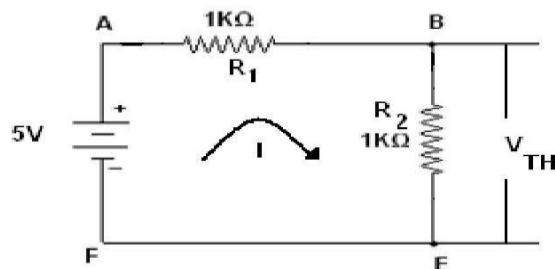

$$I = \frac{V}{R_T}$$

$$V_{TH}=V_{BE}$$

$$\therefore I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

PROCEDURE:

1. The circuit connections are given as per the circuit diagram.
2. Switch ON the power supply.
3. Initially set 5V as input voltage from RPS.
4. The ammeter reading is noted and the value is tabulated.

Table:

Let V= 5V

S.NO	Voltage in Volts	Load Current in Amps	
		Theoretical Value	Practical Value

RESULT:

Thus the Thevenin's theorem for the given circuit is verified successfully

NORTON'S THEOREM

EX.NO:1(b)

AIM:

To verify the Norton's theorem for the given circuit.

APPARATUS REQUIRED:

S.NO	APPARATUS	TYPE	RANGE	QUANTITY
1	RPS	DC	(0-30)V	1
2	Resistor	-	1KΩ	3
3	Ammeter	DC	(0-10)mA	1
4	Breadboard	-	-	1
5	Connecting wires	-	-	Few


THEORY:

NORTON'S THEOREM:

Any linear active network with output terminals C and D can be replaced by a single current source ISC (IN) in parallel with a single impedance ($Z_{Th} = Z_n$).

ISC is the current through the terminals C and D on short circuit condition. Z_{Th} is called Thevenin's impedance. In case of DC Z_{Th} is replaced by R_{Th} .

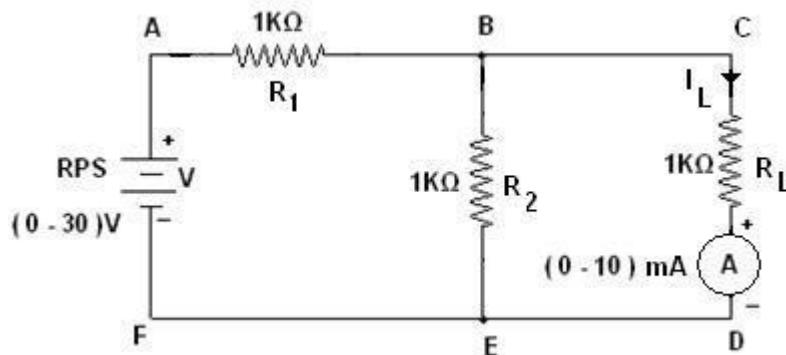
The current through impedance connected to the terminals of the Norton's equivalent circuit must have the same direction as the current through the same impedance connected to the original active network.



Circuit Diagram for Norton's Theorem


CALCULATION:

The Norton's equivalent circuit is,

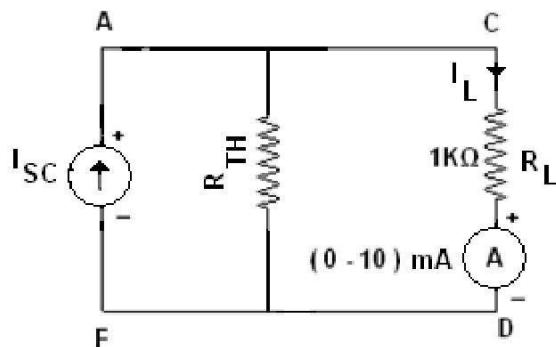

$$I_L = \frac{I_{SC} R_{TH}}{R_{TH} + R_L}$$

To Find R_{TH}:

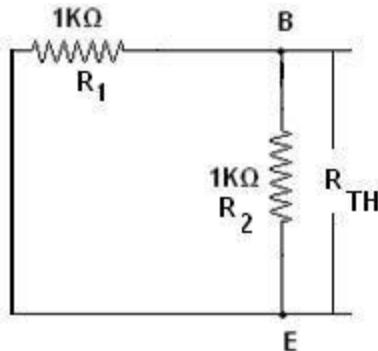


$$R_1 = 1K \Omega ; R_2 = 1K \Omega$$

$$; R_{TH} =$$

$$\frac{R_1 * R_2}{R_1 + R_2}$$

To Find I_{SC}:

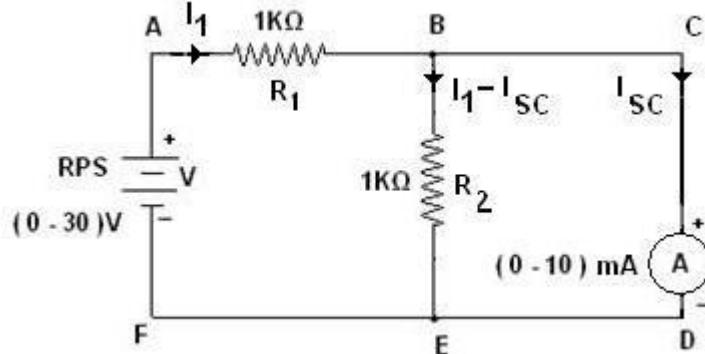

Let V=5V

In the loop ABEFA by applying KVL,

$$I_1 R_1 + (I_1 - I_{SC}) R_2 = V$$

$$I_1 \times 1 + (I_1 - I_{SC}) \times 1 = 5$$

$$2I_1 - I_{SC} = 5 \quad \dots \dots \dots \quad (1)$$

In the loop BCDEB by applying KVL,

$$(I_1 - I_{SC}) R_2 = V$$

$$(I_1 - I_{SC}) \times 1 = 0$$

$$I_1 - I_{SC} = 0 \quad \dots \dots \dots \quad (2)$$

From the equation (1) and (2),

$$\dot{I}_1 = 5 \text{ mA}$$

$$IL = \frac{ISC * RTH}{RTH + RL}$$

PROCEDURE:

1. The circuit connections are given as per the circuit diagram.
2. Switch ON the power supply.
3. Initially set 5V as input voltage from RPS.
4. The ammeter reading is noted and the value is tabulated.

RESULT:

Thus the Norton's theorem for the given circuit is verified successfully.

KIRCHHOFF'S VOLTAGE LAW

EX.NO:2(a)

AIM:

To verify the Kirchoff's Voltage Law (KVL) for the given circuit.

APPARATUS REQUIRED:

S.NO	APPARATUS	TYPE	RANGE	QUANTITY
1	RPS	DC	(0-30)V	1
2	Resistor	-	1KΩ	3
3	Voltmeter	DC	(0-10)V	3
4	Breadboard	-	-	1
5	Connecting wires	-	-	Few

FORMULA USED:

1. CURRENT DIVISION RULE:

$$I = \frac{\text{TOTAL CURRENT} \times \text{OPPOSITERESISTANCE}}{\text{TOTALRESISTANCE}}$$

2. OHM'S LAW:

$$V = IR$$

Where, V =Voltage in Volts

I =Current in Amperes

R =Resister in Ohms

THEORY:

KIRCHHOFF'S VOLTAGE LAW:

It states that the algebraic sum of all the voltages in a closed loop is equal to zero.

$$\sum V = 0$$

CALCULATION:

$$R_1 = 1\text{K } \Omega ; R_2 = 1\text{K } \Omega ; R_3 = 1\text{K } \Omega$$

$$R_T = R_3 + R_p$$

$$= R_3 + \frac{R_1 R_2}{R_1 + R_2}$$

$$I = \frac{V}{R_T}$$


Let $V = 5\text{V}$,

$$I_1 = \frac{I * R_2}{R_1 + R_2}$$

$$V_1 = I_1 * R_1$$

In the loop ABEFA,

$$V = V_3 + V_1$$

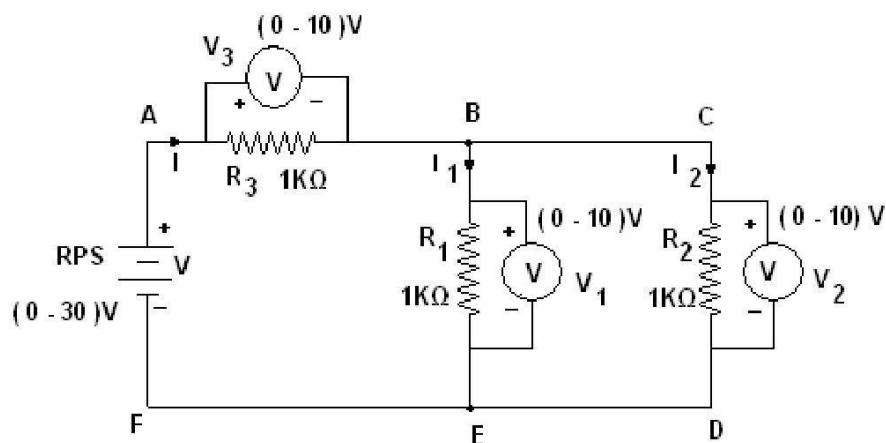

Circuit Diagram for Kirchoff's Voltage Law

PROCEDURE:

KIRCHHOFF'S VOLTAGE LAW:

1. The circuit connections are given as per the circuit diagram.
2. Switch ON the power supply.
3. Initially set 5V as input voltage from RPS.
4. The voltmeter readings are noted and the values are tabulated.
5. The same procedure is repeated for various values.

Table:

Let $V = 5V$

S.NO	Applied voltage	Voltage in Volts		
		V1	V2	V3

RESULT:

Thus the Kirchoff's Voltage Law (KVL) for the given circuit is verified.

KIRCHHOFF'S CURRENT LAW

EX. NO:

2(b) AIM:

To verify the Kirchoff's Current Law (KCL) for the given circuit.

APPARATUS REQUIRED:

S.NO	APPARATUS	TYPE	RANGE	QUANTITY
1	RPS	DC	(0-30)V	1
2	Resistor	-	1KΩ	3
3	Ammeter	DC	(0-30)mA	3
4	Breadboard	-	-	1
5	Connecting wires	-	-	Few

FORMULA USED:

1. CURRENT DIVISION RULE:

$$I = \frac{\text{TOTAL CURRENT} \times \text{OPPOSITERESISTANCE}}{\text{TOTALRESISTANCE}}$$

2. OHM'S LAW:

$$V = IR$$

Where, V= Voltage in Volts

I= Current in Amperes

R= Resister in Ohms

THEORY:

KIRCHHOFF'S CURRENT LAW:

It states that the algebraic sum of the currents meeting at a node is equal to zero.

$$\sum \text{Current flow towards the node} = \sum \text{Current flow away from the node}$$

CALCULATION:

$$R_1 = 1\text{K } \Omega ; R_2 = 1\text{K } \Omega ; R_3 = 1\text{K } \Omega$$

$$R_T = R_3 + R_p$$


$$= R_3 + \frac{R_1 R_2}{R_1 + R_2}$$

$$I = \frac{V}{R_\tau}$$

Let $V = 5V$,

$$I_1 = \frac{I \cdot R_2}{R_1 + R_2}$$

At node B the current $I = I_1 + I_2$

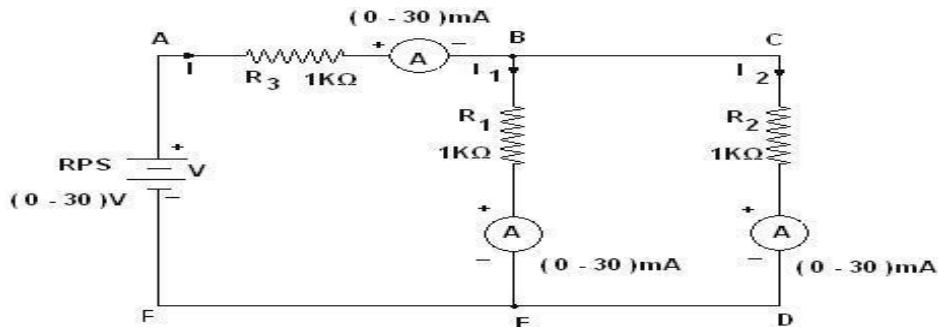

Circuit Diagram for Kirchoff's Current Law

PROCEDURE:

KIRCHOFF'S CURRENT LAW:

1. The circuit connections are given as per the circuit diagram.
2. Switch ON the power supply.
3. Initially set 5V as input voltage from RPS.
4. The ammeter readings are noted and the values are tabulated.
5. The same procedure is repeated for various values.

Table:

S.NO	Applied voltage	Current in amps		
		I_1	I_2	$I = I_1 + I_2$

RESULT:

Thus the Kirchoff's Current Law (KCL) for the given circuit is verified.

VERIFICATION OF SUPERPOSITION THEOREM

EX.NO:3

AIM:

To verify the superposition theorem for the given circuit.

APPARATUS REQUIRED:

S.NO	APPARATUS	TYPE	RANGE	QUANTITY
1	RPS	DC	(0-30)V	2
2	Resistor	-	1KΩ, 2K, 10K	3
3	Ammeter	DC	(0-50)mA	1
4	Breadboard	-	-	1
5	Connecting wires	-	-	Few

THEORY:


SUPERPOSITION THEOREM:

The superposition theorem for electrical circuits states that the total current in any branch of a bilateral linear circuit equals the algebraic sum of the currents produced by each source acting separately throughout the circuit.

To ascertain the contribution of each individual source, all of the other sources first must be "killed" (set to zero) by:

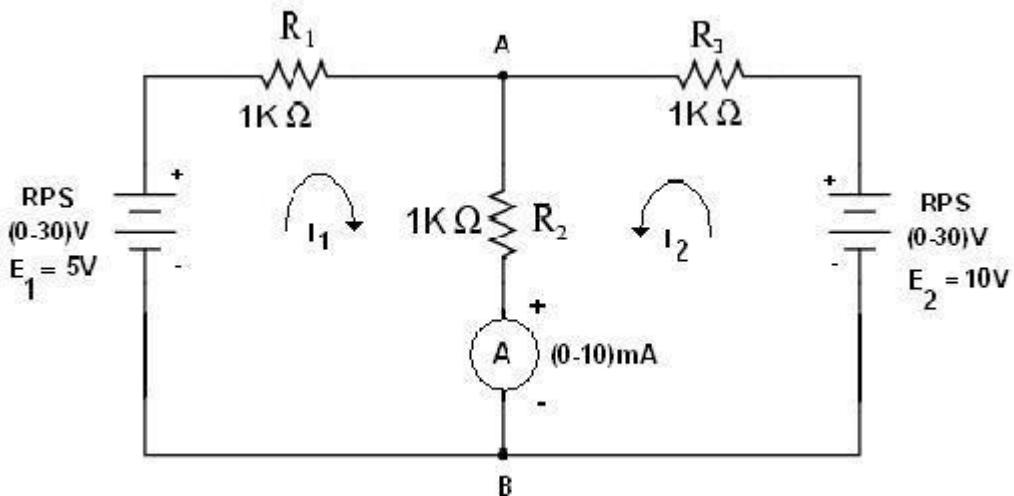1. replacing all other voltage sources with a short circuit (thereby eliminating difference of potential. i.e. $V=0$)
2. replacing all other current sources with an open circuit (thereby eliminating current. i.e. $I=0$)

This procedure is followed for each source in turn, and then the resultant currents are added to determine the true operation of the circuit. The resultant circuit operation is the superposition of the various voltage and current sources.




Circuit Diagram for Superposition Theorem

Table:

S.No	E1 voltage(Volts)	E2 voltage(Volts)	Load current across the branch AB (mA)	
			Theoretical	Practical
1				

E1 SOURCE IS

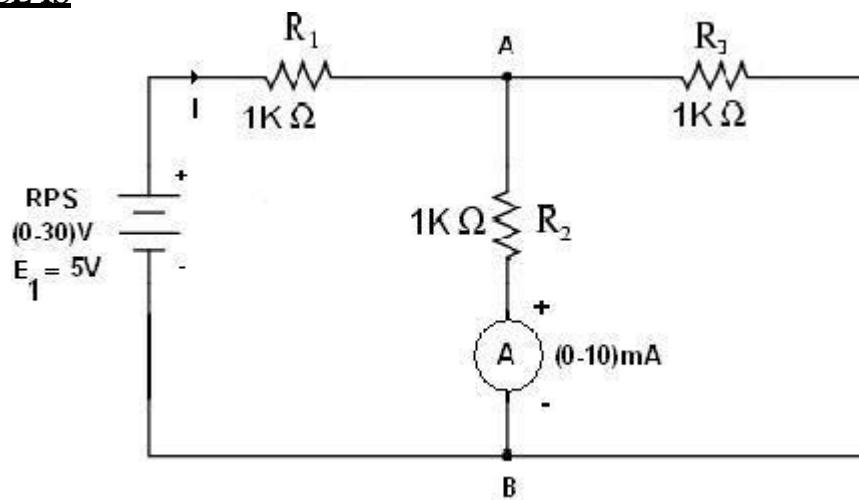

CALCULATION:

$$R_1 = 1\text{K } \Omega ; R_2 = 1\text{K } \Omega ; R_3 = 1\text{K } \Omega$$

$$R_T = R_1 + R_p$$

$$= R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

$$I = \frac{V}{R_T}$$


Let V=5V,

$$I_{AB1} = I \times \frac{R_3}{R_2 + R_3} = 3.3 \times 10^{-3} \times \frac{1000}{1000+1000}$$

Table:

S.No	E1 voltage(Volts)	Load current across the branch AB(mA)	
		Theoretical	Practical
1	5		

E2 SOURCE IS ACTING:

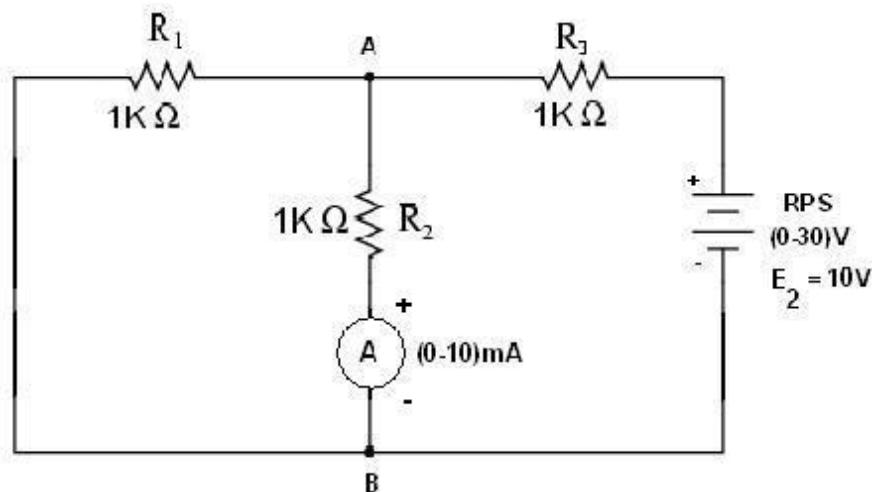

CALCULATION:

$$R_1 = 1\text{K } \Omega ; R_2 = 1\text{K } \Omega ; R_3 = 1\text{K } \Omega$$

$$\begin{aligned} R_T &= R_3 + R_p \\ &= R_3 + \frac{R_1 R_2}{R_1 + R_2} \end{aligned}$$

$$I = \frac{V}{R_T}$$

Let V=10V,

$$I_{AB2} = I \times \frac{R_3}{R_2 + R_3} = 6.66 \times 10^{-3} \times \frac{1000}{1000+1000}$$

Table:

S.No	E2 voltage(Volts)	Load current across the branch AB(mA)	
		Theoretical	Practical
1	10		

E1 and E2 SOURCES ARE ACTING:

$$I_{AB} = I_{AB1} + I_{AB2}$$

RESULT:

Thus the superposition theorem for the given circuit is verified.

VERIFICATION OF MAXIMUM POWER TRANSFER THEOREM

EX.NO:4(a)

AIM:

To verify the maximum power transfer theorem for the given circuit.

APPARATUS REQUIRED:

S.NO	APPARATUS	TYPE	RANGE	QUANTITY
1	RPS	DC	(0-30)V	1
2	Resistor	-	1KΩ	2
3	Variable Resistor		1KΩ	1
4	Ammeter	DC	(0-10)mA	1
5	Breadboard	-	-	1
6	Connecting wires	-	-	Few


THEORY:

MAXIMUM POWER TRANSFER THEOREM:

In electrical engineering, the **maximum power (transfer) theorem** states that, to obtain maximum external power from a source to a load with a finite internal resistance, the resistance of the load must be made the same as that of the source.

The theorem applies to maximum power, and not maximum efficiency. If the resistance of the load is made larger than the resistance of the source, then efficiency is higher, since most of the power is generated in the load, but the overall power is lower since the total circuit resistance goes up.

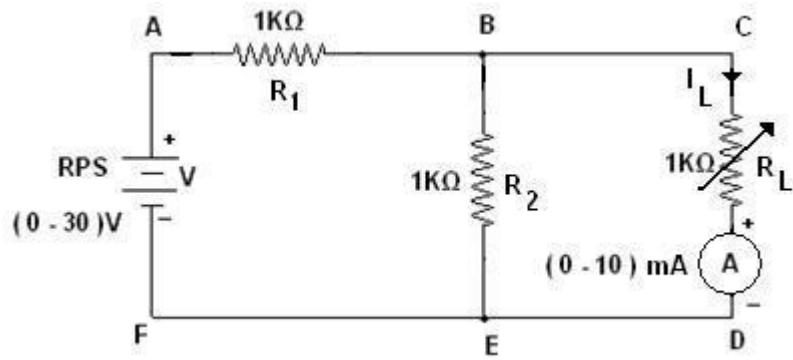
If the internal impedance is made larger than the load then most of the power ends up being dissipated in the source, and although the total power dissipated is higher, due to lower circuit resistance, it turns out that the amount dissipated in the load is reduced.



Circuit Diagram for Maximum Power Transfer Theorem CA

LCULATION:


To Find R_{TH}:

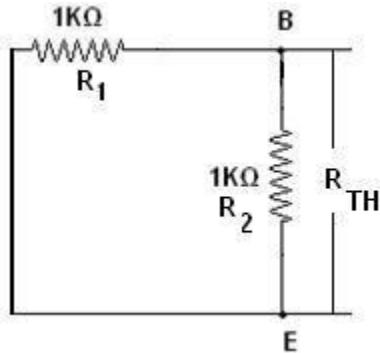

$$R_1 = 1\text{ k}\Omega ; \quad R_2 = 1\text{ k}\Omega ;$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{1000 \times 1000}{1000 + 1000}$$

To Find V_{TH}:

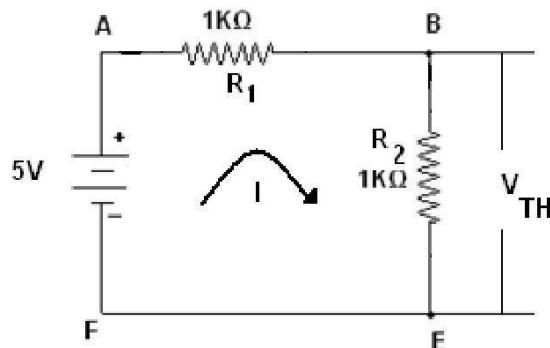

$$I = \frac{V}{R_T}$$

Let $V = 5V$,

$$V_{TH} = V_{BE} = 5 - 1K \times I$$

$$\therefore I_L = \frac{V_{TH}}{2 \times R_{TH}} = \frac{2.5}{2 \times 500} = 2.5mA$$

$$\therefore P_{max} = I_L^2 \times R_{TH} = 2.5 \times 10^{-3} \times 2.5 \times 10^{-3} \times 500$$

$\therefore Load\ Resistance\ R_L =$

PROCEDURE:

1. The circuit connections are given as per the circuit diagram.
2. Switch ON the power supply.
3. Initially set 5V as input voltage from RPS.
4. The ammeter reading is noted for various values of load resistance and the values are tabulated.
5. The load resistance for the maximum power is obtained from the table.

Table:

Let $V = 5V$

S.No	Resistance(RL) in Ohms	Current(IL) in mA	Power(IL ² RL) in mW
1	100		
2	200		
3	300		
4	400		
5	500		
6	700		
7	900		

RESULT:

Thus the maximum power transfer theorem for the given circuit is verified successfully.

RECIPROCITYTHEOREM

EX.NO:4(b)

AIM:

To verify the reciprocity theorem for the given circuit.

APPARATUS REQUIRED:


S.NO	APPARATUS	TYPE	RANGE	QUANTITY
1	RPS	DC	(0-30)V	1
2	Resistor	-	1KΩ	4
3	Ammeter	DC	(0-5)mA	1
4	Breadboard	-	-	1
5	Connectingwires	-	-	Few

THEORY:

RECIPROCITYTHEOREM:

The reciprocity theorem states that if an emf 'E' in one branch of a reciprocal network produces a current I in another, then if the emf 'E' is moved from the first to the second branch, it will cause the same current in the first branch, where the emf has been replaced by a short circuit. We shall see that any network composed of linear, bilateral elements (such as R, L and C) is reciprocal.

Before interchanging:

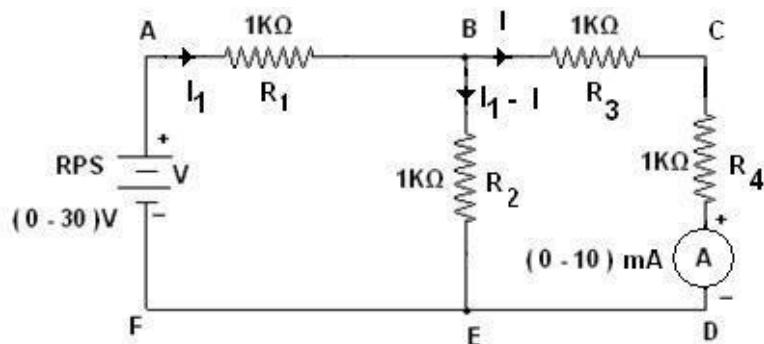

Circuit Diagram for Reciprocity Theorem

CALCULATION:

Let $V = 5V$

In the loop ABEF by applying KVL,

$$I_1 R_1 + (I_1 - I)R_2 = V$$

$$I_1 \times 1 + (I_1 - I) \times 1 = 5$$

$$2I_1 - I = 5 \quad \text{--- --- --- --- ---} \quad (1)$$

In the loop BCDE by applying KVL,

$$IR_3 + IR_4 - (I_1 - I)R_2 = V$$

$$I \times 1 + I \times 1 - (I_1 - I) \times 1 = 0$$

$$-I_1 + 3I = 0 \quad \text{--- --- --- --- ---} \quad (2)$$

$$D = \begin{vmatrix} 2K & -1K \\ -1K & 3K \end{vmatrix} = 6K^2 - 1K^2 = 5K^2 = 5 \times 10^6$$

$$D_2 = \begin{vmatrix} 2K & 5 \\ -1K & 0 \end{vmatrix} = 5K = 5 \times 10^3$$

$$I = \frac{D_2}{D} = \frac{5 \times 10^3}{5 \times 10^6} = 1mA$$


PROCEDURE:

1. The circuit connections are given as per the circuit diagram.
 2. Switch ON the power supply.
 3. Initially set 5V as input voltage from RPS.
 4. The ammeter reading is noted and tabulated.

Table for before interchanging:

V(Volts)	Current(mA)	
	Theoritical	Practical
5		

After interchanging:

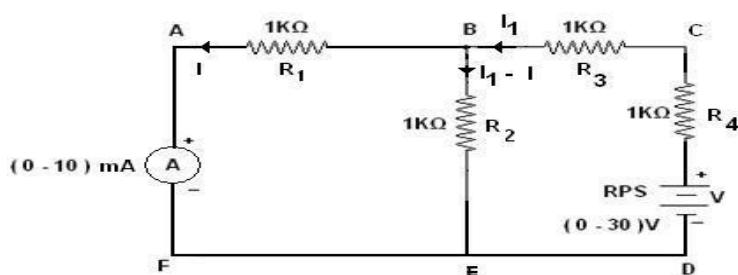

Circuit Diagram for Reciprocity Theorem

CALCULATION:

Let $V=5V$.

In the loop ABEFA by applying KVL,

$$\begin{aligned} IR_1 - (I_1 - I)R_2 &= V \\ I \times 1 - (I_1 - I) \times 1 &= 0 \\ -I_1 + 2I &= 0 \end{aligned} \quad (1)$$

In the loop BCDE B by applying KVL,

$$\begin{aligned} I_1 R_4 + I_1 R_3 + (I_1 - I) R_2 &= V \\ I_1 \times 1 + I_1 \times 1 + (I_1 - I) \times 1 &= 5 \\ 3I_1 - I &= 5 \end{aligned} \quad (2)$$

$$D = \begin{vmatrix} -1K & 2K \\ 3K & -1K \end{vmatrix} = 1K^2 - 6K^2 = -5K^2 = -5 \times 10^6$$

$$D_2 = \begin{vmatrix} -1K & 0 \\ 3K & 5 \end{vmatrix} = -5K - 0 = -5 \times 10^3$$

$$I = \frac{D_2}{D} = \frac{-5 \times 10^3}{-5 \times 10^6} = 1mA$$

PROCEDURE:

1. The circuit connections are given as per the circuit diagram.
2. Switch ON the power supply.
3. Initially set 5V as input voltage from RPS.
4. The ammeter reading is noted and tabulated.

Table for before interchanging:

V(Volts)	Current(mA)	
	Theoretical	Practical
5		

RESULT:

Thus the reciprocity theorem for the given circuit is verified successfully.

DETERMINATION OF RESONANCE FREQUENCY OF SERIES AND PARALLEL RLC CIRCUITS

EX.NO:5

AIM:

To determine the resonance frequency of series and parallel RLC circuits

APPARATUS REQUIRED:

S.NO	APPARATUS	TYPE	RANGE	QUANTITY
1	Function Generator	AC	(1Hz-3MHz)	1
2	Resistor	AC	600Ω	1
3	Inductor	AC	101.4mH	1
4	Capacitor	AC	0.01mF	1
5	Ammeter	AC	(0-10)mA	1
6	Breadboard	-	-	1
7	Connecting wires	-	-	Few


THEORY:

The resonance of a RLC circuit occurs when the inductive and capacitive reactances are equal in magnitude but cancel each other because they are 180 degrees apart in phase. The sharp minimum in impedance which occurs is useful in tuning applications. The sharpness of the minimum depends on the value of R.

The frequency at which the reactance of the inductance and the capacitance cancel each other is the resonant frequency (or the unity power factor frequency) of this circuit. This occurs at

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

SERIESRESONANCE:

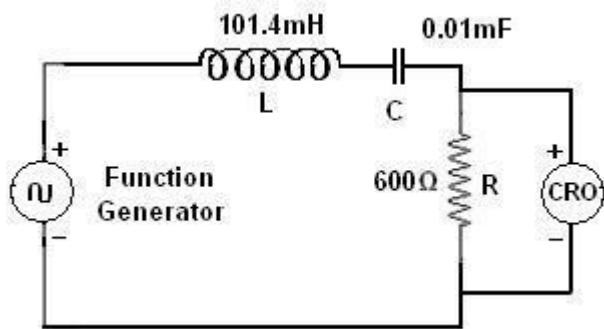

Circuit Diagram for Series Resonant

CALCULATION:

$$R = 600\Omega$$

$$L = 101.4\text{mH}$$

$$C = 0.01\mu\text{F}$$

∴ The resonant frequency is,


$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{101.4 \times 10^{-3} \times 0.01 \times 10^{-6}}} = 5 \text{ KHz}$$

PROCEDURE:

1. The circuit connections are given as per the circuit diagram.
2. Switch ON the power supply.
3. The input is given in the form of sin wave by function generator.
4. The amplitude of the response across the resistor is noted for various frequency ranges.
5. The current is calculated and tabulated.


Table:

S.N o	Frequency (KHz)	Output voltage (Volts)	I= V / R (mA)
1	1		
2	2		
3	2.5		
4	3		
5	4.5		
6	6		
7	7		
8	8		

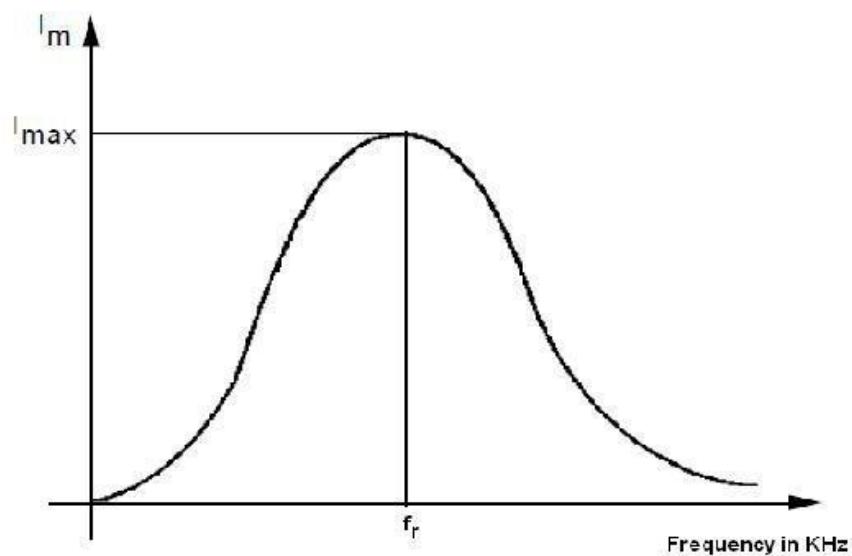

Frequency Response of Series Resonance Circuit

PARALLEL RESONANCE:

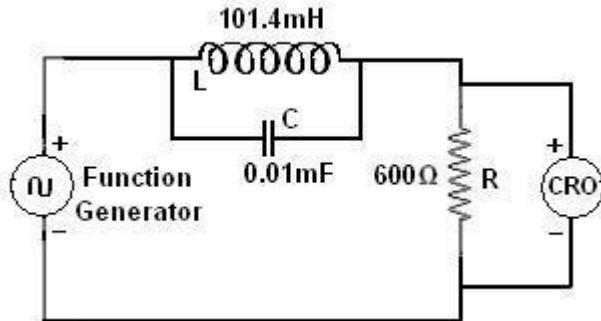

Circuit Diagram for Parallel Resonant

CALCULATION:

$$R = 600\Omega$$

$$L = 101.4\text{mH}$$

$$C = 0.01\mu\text{F}$$

∴ The resonant frequency is,


$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{101.4 \times 10^{-3} \times 0.01 \times 10^{-6}}} = 5\text{ KHz}$$

PROCEDURE:

1. The circuit connections are given as per the circuit diagram.
2. Switch ON the power supply.
3. The input is given in the form of sin wave by function generator.
4. The amplitude of the response across the resistor is noted for various frequency ranges.
5. The current is calculated and tabulated.

Table:

S.No	Frequency (KHz)	Output voltage (Volts)	$I = V / R$ (mA)
1	1		
2	1.8		
3	2.5		
4	3		
5	4		
6	5.2		
7	7		
8	8		

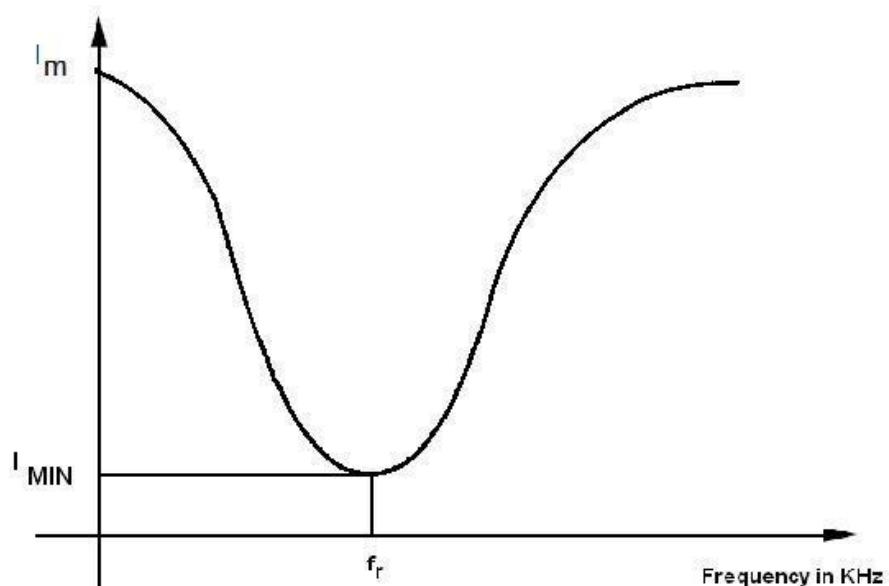

Frequency Response of Parallel Resonance Circuit

RESULT:

Thus the frequency response of series and parallel resonant circuits are analyzed.

TRANSIENT ANALYSIS OF RL AND RC CIRCUITS

EX. NO:

6AIM:

To construct RL & RC transient circuit and to draw the transient curves.

APPARATUS REQUIRED:

S.NO .	NAME OF THE EQUIPMENT	RANGE	TYPE	QTY.
1.	RPS	(0-30)V	DC	1
2.	Ammeter	(0-10)mA	MC	1
3.	Voltmeter	(0-10)V	MC	1
4.	Resistor	10KΩ	-	3
5.	Capacitor	1000μ F	-	1
6.	Breadboard	-	-	1
7.	Connecting Wires	-	Single strand	As required

THEORY:

Electrical devices are controlled by switches which are closed to connect supply to the device, or opened in order to disconnect the supply to the device. The switching operation will change the current and voltage in the device. The purely resistive devices will allow instantaneous change in current and voltage.

An inductive device will not allow sudden change in current and capacitance device will not allow sudden change in voltage. Hence when switching operation is performed in inductive and capacitive devices, the current & voltage in device will take a certain time to change from pre-switching value to steady state value after switching. This phenomenon is known as transient. The study of switching condition in the circuit is called transient analysis. The state of the circuit from instant of switching to attainment of steady state is called transient state. The time duration from the instant of switching till the steady state is called transient period. The current & voltage of circuit elements during transient period is called transient response.


FORMULA:

$$\text{Time constant of RC circuit} = RC$$

PROCEDURE:

- Connections are made as per the circuit diagram.
- Before switching ON the power supply the switch S should be in off position
- Now switch ON the power supply and change the switch to ON position.


CIRCUITDIAGRAM:

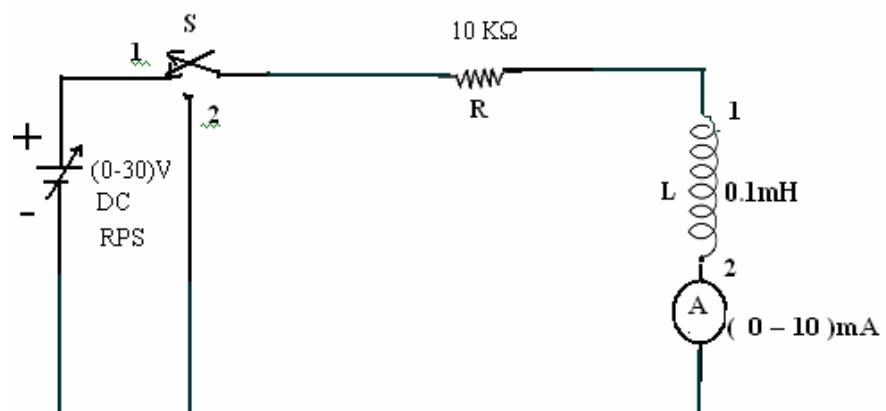

TABULATION:


S.NO.	TIME (msec)	CHARGING CURRENT(IA)	DISCHARGING CURRENT(IA)

MODEL CALCULATION & ANALYSIS:

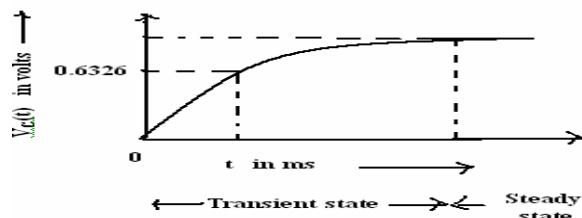


CIRCUITDIAGRAM:RC

CIRCUIT:

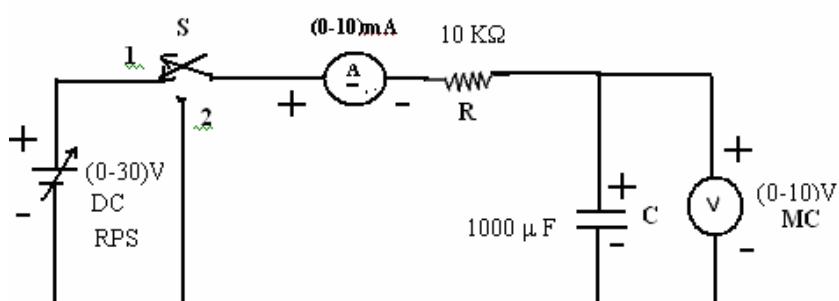


MODELGRAPH:

CHARGING

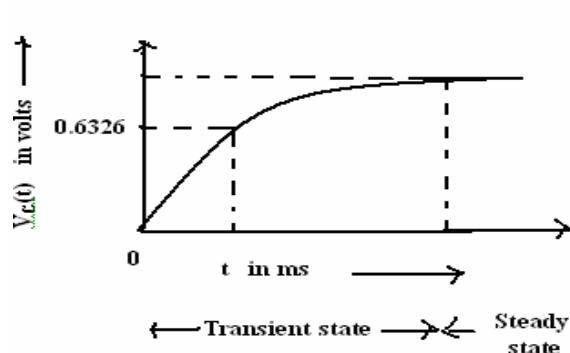

DISCHARGING

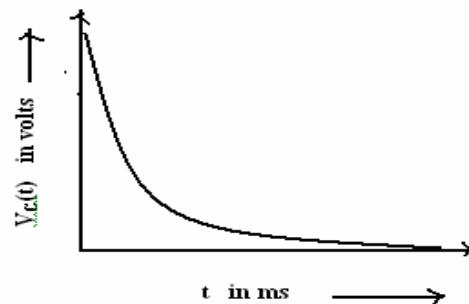

CHARGING:

S.NO.	TIME (msec)	VOLTAGE ACROSS‘ C’ (volts)	CURRENT THROUG H‘C’ (mA)

MODELCALCULATION&ANALYSIS:

TABULATION:

DISCHARGING:

S.NO.	TIME (msec)	VOLTAGE ACROSS‘ C’ (volts)	CURRENT THROUG H‘C’ (mA)

MODEL CALCULATION & ANALYSIS:

RESULT:

Thus the transient response of RL & RC circuit for DC input was verified.