

MAHA BARATHI ENGINEERING COLLEGE

NH-79, Salem-Chennai Highway, A.Vasudevanur, Chinnasalem TK, Kallakurichi Dt – 606 201.

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

Accredited by NAAC and Recognized under section 2(f) & 12(B) status of UGC, New Delhi.

www.mbec.ac.in | 04151-256333, 257333 | mbec123@gmail.com

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Even Semester

(Regulation 2021)



II Year/ IV Semester

EC3462-Linear Integrated Circuits Laboratory

(As per the Anna University Syllabus, Chennai)

TABLE OF CONTENT

Ex.No:1(a)	DESIGN AND ANALYSIS OF CURRENT SERIES FEEDBACK AMPLIFIER
Date:	

AIM:

To design and analyze the current series feedback amplifier and calculate the Bandwidth, Input impedance and Output impedance for with & without feedback amplifier.

EQUIPMENTS REQUIRED:

S.NO	EQUIPMENTS	RANGE	QUANTITY
1	Transistor	BC107	1
2	Resistor	56KΩ, 2.2KΩ, 12KΩ, 470Ω	Each one
3	Capacitor	22μF, 2.2μF, 47μF	Each one
4	CRO	(0-30)MHz	1
5	RPS	(0-30)V	1
6	Function Generator	(0-3)MHz	1
7	Breadboard	-	1
8	Connecting wires	-	As required

THEORY:

A portion of the output signal is taken from the output of the amplifier and is combined with the normal input signal and thereby feedback is accomplished. There are two types of feedback, positive feedback and negative feedback. Feedback increases the stability of an amplifier, increases the bandwidth and reduces distortion and noise. The property of positive feedback is utilized in oscillators. The series connection at the output increases the output resistance. Common emitter amplifier is an example for current series feedback amplifier.

Parameter	With feedback
Input Impedance	Increases
Output Impedance	Increases
Gain	Decreases
Bandwidth	Increases


PROCEDURE:

1. Design the current series feedback amplifier.
2. The connections are made as per the circuit diagram.
3. Set the input voltage to a fixed value. Measure the output voltages for the various input frequencies. Calculate the voltage gain in dB for each input frequency.
4. Plot the graph: Frequency in Hz Vs Gain in dB for the amplifier with feedback.
5. Then the capacitor C_E is included in parallel with R_E to get the amplifier without feedback.
6. The steps (2, 3, and 4) are repeated for an amplifier without feedback.
7. Calculate the input impedance and output impedance values.


CIRCUIT

DIAGRAM: WITHOUT FEEDBACK

EDBACK

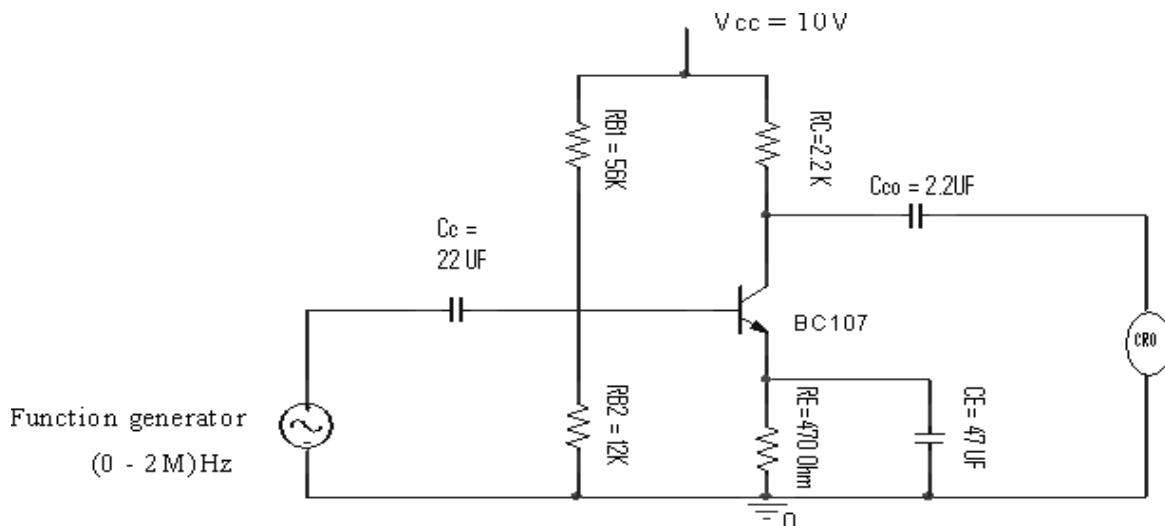

WITH FEEDBACK

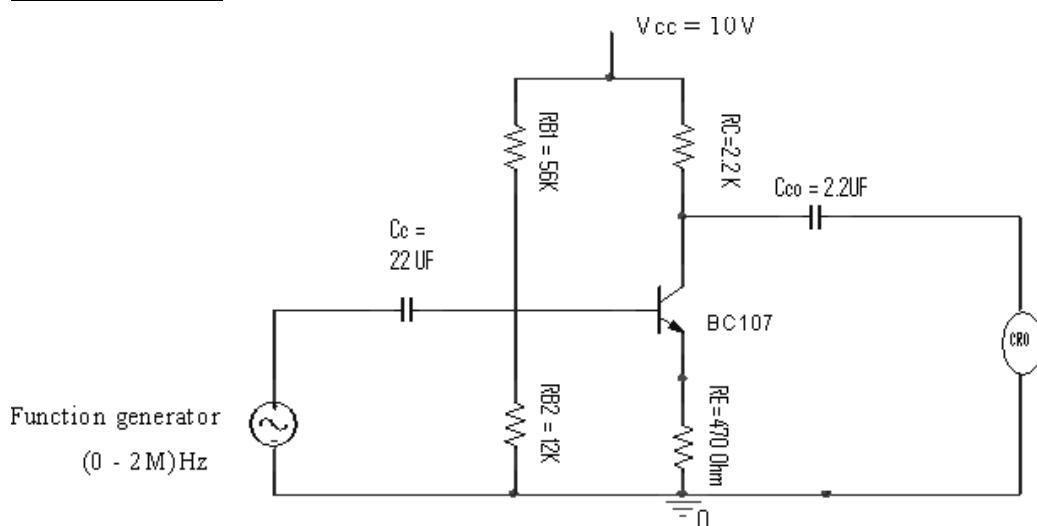

DESIGNPROCEDURE:

Assumptions: $V_{CC}=10\text{V}$, $V_E=V_{CC}/10=1\text{V}$, $V_{CE}=V_{CC}/2=5\text{V}$; $R_L=100\text{ohms}$, $f_L=1\text{KHz}$. Since I_B is very small compare with I_C , $I_E \approx I_C = 2\text{mA}$, $A_V = 30$; $h_{fe} = 120$, $S = 5$, $h_{ie} = 1.56\text{K}\Omega$, $R_{leff} = 234\Omega$, $R_{B1} = 56\text{K}\Omega$, $R_{B2} = 12\text{K}\Omega$, $D = 29$

1. Calculation of R_E :

$$R_E = V_E/I_E = 470\Omega$$

$$\begin{aligned} V_B &= V_{CC} - R_{B1} - R_{B2}V_B \\ &= 1.3\text{V} \end{aligned}$$

2. Calculation of R_C :

$$V_{cc} = I_c R_c + V_{CE} + I_E R_E I_C$$

$$\approx I_E$$

$$R_c = 2.2\text{K}\Omega$$

3. Calculation of R_B :

$$R_B = R_{B1} || R_{B2}$$

$$R_{B1} = 56\text{K}\Omega$$

$$\Omega R_{B2} = 12\text{K}\Omega$$

$$R_B = 9.88\text{K}\Omega$$

4. Calculation of Input impedance Z_i :

$$Z_i = h_{ie} \parallel$$

$$R_B Z_i = 1.34\text{K}\Omega$$

$$\Omega$$

5. Calculation of Output impedance Z_o :

$$Z_0 = R_c = 2\text{K}\Omega$$

Parameter	Without feedback	With Feedback
Input Impedance	$Z_i = R_B // h_{ie} = 1.34\text{K}\Omega$	$Z_{if} = Z_i D = 25.23\text{K}\Omega$
Output Impedance	$Z_o = R_c // R_L = 2\text{K}\Omega$	$Z_{of} = Z_o D = 58\text{K}\Omega$

TABULATION:WITHOUT FEEDBACK:

V_{in}=


S.NO	FrequencyinHz	OutputvoltageinVolts	Voltagegain	Voltagegain in dB

WITHFEEDBACK:

V_{in}=

S.NO	FrequencyinHz	OutputvoltageinVolts	Voltagegain	Voltagegain in dB

MODELGRAPH:

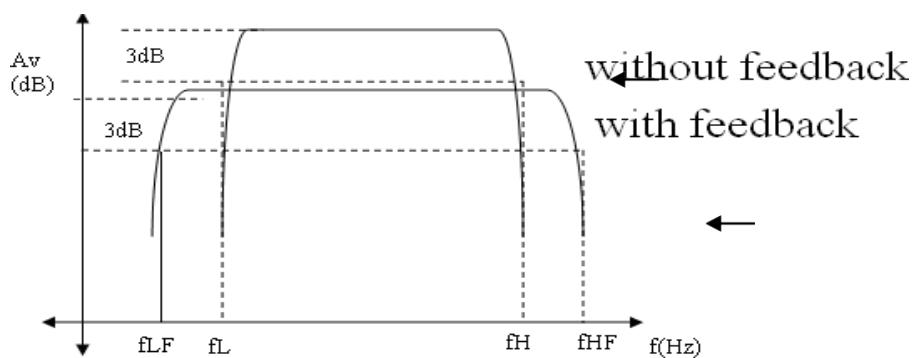

RESULT:

Thus the current series feedback amplifier is designed for without and with feedback.

The circuit is analyzed to get the frequency response and measured the following

parameters LowercutoffFrequency f_L :

UppercutoffFrequency f_H :

Bandwidth :

Input impedance :

Output impedance :

Ex.No:1(b)
Date:

DESIGN AND ANALYSIS OF VOLTAGE SHUNT FEEDBACK AMPLIFIER

AIM

To design and analyze the voltage shunt feedback amplifier and calculate the Bandwidth, Input impedance and Output impedance for with & without feedback amplifier.

EQUIPMENTS REQUIRED:

S.NO	EQUIPMENTS	RANGE	QUANTITY
1	Transistor	BC107	1
2	Resistor	56KΩ, 2.2KΩ, 12KΩ, 470Ω, 1KΩ	Each one
3	Capacitor	22μF, 2.2μF, 47μF, 0.1μF	Each one
4	CRO	(0-30)MHz	1
5	RPS	(0-30)V	1
6	Function Generator	(0-3)MHz	1
7	Breadboard	-	1
8	Connecting wires	-	As required

THEORY:

A portion of the output signal is taken from the output of the amplifier and is combined with the normal input signal and thereby feedback is accomplished. There are two types of feedback, positive feedback and negative feedback. Feedback increases the stability of an amplifier, increases

the bandwidth and reduces distortion and noise. The property of positive feedback is utilized in oscillators. The shunt connection at the output decreases the output resistance. Common emitter amplifier with a resistive feedback from collector to base is an example for voltage shunt feedback amplifier.


Parameter	With feedback
Input Impedance	Decreases
Output Impedance	Decreases
Gain	Decreases
Bandwidth	Increases

PROCEDURE:


1. Design the voltage shunt feedback amplifier.
2. The connections are made as per the circuit diagram.
3. Set the input voltage to a fixed value. Measure the output voltages for the various input frequencies. Calculate the voltage gain in dB for each input frequency.
4. Plot the graph: Frequency in Hz Vs Gain in dB for the amplifier with feedback.
5. Then the capacitor C_f and resistance R_f is removed from the feedback to get the amplifier without feedback.
6. The steps (2,3, and 4) are repeated for an amplifier without feedback.
7. Calculate the input impedance and output impedance values.

CIRCUIT

DIAGRAM: WITHOUT FEEDBACK

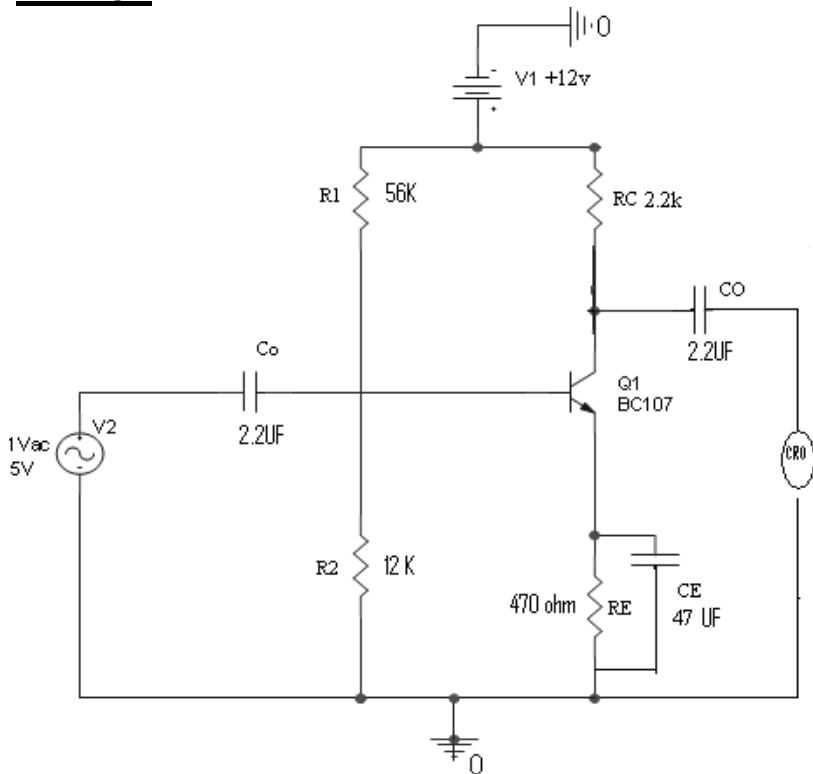

WITHFEEDBACK:

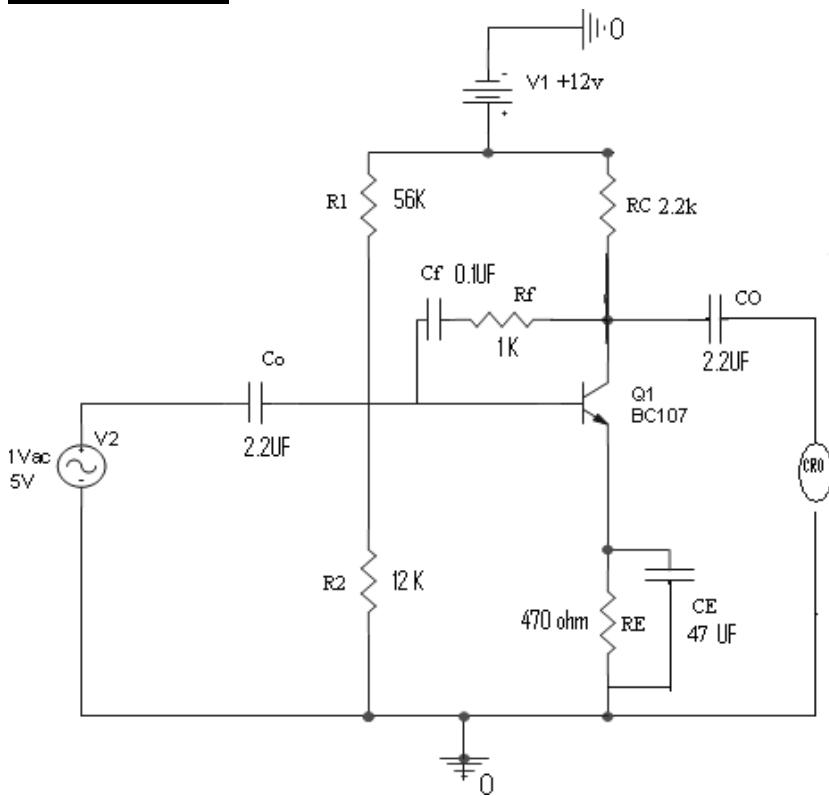

DESIGNPROCEDURE:

Assumptions: $V_{CC}=12\text{v}$, $AV=30$, $f_L=1\text{KHz}$, $S=2$, $I_E=1.2\text{mA}$, $R_L=4.7\text{K}\Omega$, $\beta=0.4$;

1. Calculationof h_{ie} :

$$r_e = 26\text{mV}/I_E$$

$$h_{ie} = h_{fe} r_e$$

2.Caluclationof A_vf

$$A_v = h_{fe} R_c / |R_L|$$

$$h_{ie}$$

$$V_E = V_{CC}/10, V_{CE} = V_{CC}/2$$

3. Calculationof R_c :

$$V_{cc} = I_c R_c + V_{CE} + I_E R_E$$

$$R_C = (V_{cc} - V_{CE} - I_E R_E) / I_c I_C \approx I_E$$

$$V_B = V_{CC} R_2 / (R_1 + R_2)$$

4. Calculationof R_E :

$$R_E = V_E / I_E$$

5. Calculation of R_B :

$$R_B = R_1 \parallel R_2$$

6. Calculation of Input impedance Z_i :

$$R_i = h_{ie} \parallel R_B \parallel R_F$$

7. Calculation of Input impedance Z_0 :

$$R_0 = R_c \parallel R_F$$

8. Calculation of Coupling Capacitors:

$$X_{ci} = R_i / 10$$

$$X_{c0} = R_c \parallel R_L$$

WITH

$$\text{FEEDBACK } D = 1 + A$$

$$\beta A_{VF} = A_v / D$$

$$R_{if} = R_i / D R_{of}$$

$$= R_0 / D$$

Parameter	Without feedback	With Feedback
Input Impedance	$R_i = h_{ie} \parallel R_B \parallel R_F$	$R_{if} = R_i / D$
Output Impedance	$R_0 = R_c \parallel R_F$	$R_{of} = R_0 / D$
Gain	$A_v = h_{fe} R_c \parallel R_L$ _____ H_{ie}	$A_{VF} = A_v / D$

TABULATION:WITHOUT

UTFEEDBACK:

V_{in}=


S.NO	FrequencyinHz	Amplitudein Volts	Voltagegain	Voltagegain in dB

WITHFEEDBACK:

V_{in}=

S.NO	FrequencyinHz	Amplitudein Volts	Voltagegain	Voltagegain in dB

MODELGRAPH:

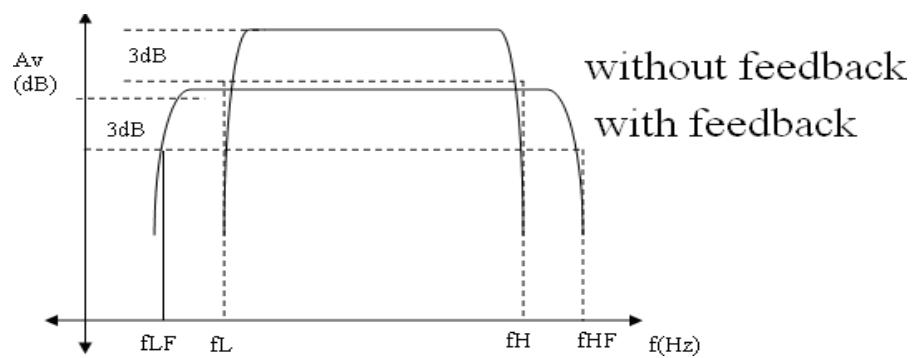

RESULT:

Thus the voltage shunt feedback amplifier is designed for without and with feedback. The circuit is analyzed to get the frequency response and measured the following parameters

Lower cutoff Frequency f_L

:Upper cutoff Frequency

f_H :Bandwidth :

Input impedance :

Output impedance :

Ex.No:2(a)
Date:

DESIGN AND ANALYSIS OF R C PHASE SHIFT OSCILLATOR

AIM:

To design and analyze a RC phase shift oscillator for a given frequency and test the result with the design.

EQUIPMENTS REQUIRED:

S.NO	EQUIPMENTS	RANGE	QUANTITY
1	Transistor	BC107	1
2	Resistor	56K, 12KΩ, 470Ω, 2.2KΩ	Each1
3	Resistor		Each3
4	Capacitor	0.01μF	3
5	CRO	(0-30)MHz	1
6	RPS	(0-30)V	1
7	Breadboard	-	1
8	Connecting wires	-	As required


THEORY:

A common emitter amplifier followed by three sections of RC phase shift network, the output of the last section being returned to the input for a RC phase shift oscillator. In practice the value of R is adjusted such that the phase angle becomes 60° . If the values of R and C are chosen so that for the given frequency the phase shift of each RC section is 60° . Thus such a RC ladder network produces a total phase shift of 180° between its input and output voltages for only the given frequency the total phase shift from the base of the transistor around the circuit and back to the base will be exactly 360° or 0° , thereby satisfying Barkhausen condition for oscillation. The RC phase shift oscillator is suitable for audio frequencies only. Its main drawbacks are that the three capacitors and resistors should be changed simultaneously to change the frequency of oscillation and it is difficult to control the amplitude of oscillation without affecting the frequency of oscillation. It is mainly used in audio frequency transmitter for generating carrier signals.

PROCEDURE:

1. Design the RC phase shift oscillator.
2. The connections are made as per the circuit diagram.
3. Measure the output sine wave form using CRO.
4. The value of frequency is calculated and compared with the design.

CIRCUITDIAGRAM:

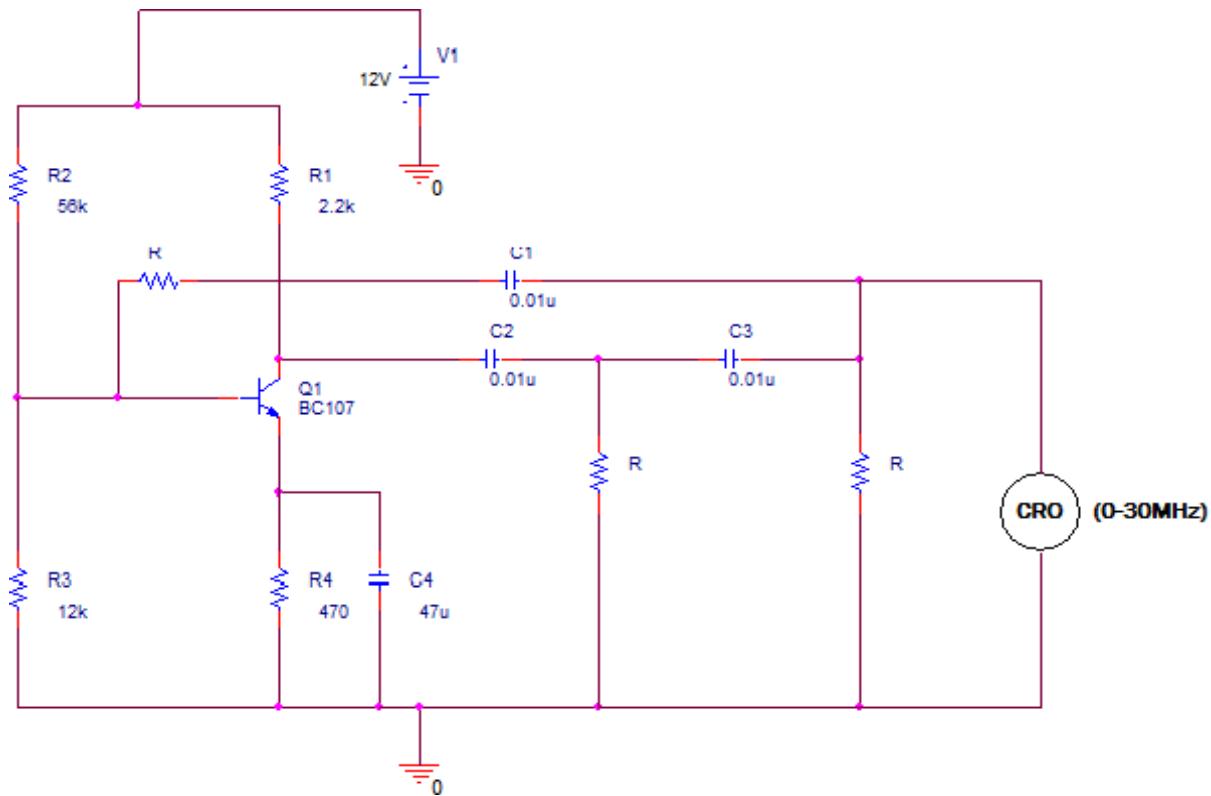

DESIGNPROCEDURE:

Design of a Transistor circuit:

$$V_{CC} = 10V, I_C = 2mA, \beta =$$

$$100I_B = I_C / \beta = 0.02mA$$

$$V_{CE} = V_{CC} / 2 = 5V$$

$$V_{BE} = 10\% \text{ of } V_{CC} = 1.0V$$

$$V_B = V_{RE} + V_{BE} = 1.0 + 0.7 = 1.7V$$

$$R_E = V_{RE} / I_E = 1.0 / (2.02 * 10^{-3}) = 495\Omega = 470$$

$$\Omega R_2 = V_B / (10 * I_B) = 8.5K\Omega = 12K\Omega$$

$$R_1 = [V_{CC} / (10 * I_B)] - R_2 = 50K$$

$$\Omega = 56K\Omega RC = (V_{CC} - V_{CE} - I_E R_E) / I_C = 2.2K\Omega$$

X_{CE} must be equal to one-tenth of value of R_E at the lowest operating frequency. $X_{CE} = R_E / 10 = 47$, $\omega = 2\pi f = 75Hz$

$$\Leftrightarrow 1 / (\omega C_E) = 47$$

$$\Leftrightarrow C_E = 56\mu F =$$

47 μF Choose coupling capacitor = 0.0

1 μF

Design of Tank circuit:

Given frequency = 1 KHZ and assume C =
 $0.01\mu F$ Design Equation: Frequency
 $= 1/(2\pi RC \sqrt{4K+6})$
 $\Rightarrow R = 6.8 K\Omega$

Barkhausen Criterion:

$$K = R_c / R$$

$$= 2.4K / 6.5K$$

$$= 0.32$$


$$h_{fe} = 4K + 23 + 29 / K$$

$$= 114.99$$

TABULATION:

S.No	Capacitor	Resistor	Theoretical frequency in KHz	Amplitude in Volts	Time period in ms	Observed frequency in KHz
1	0.01uF		1K			
2	0.01uF		1.5K			
3	0.01uF		2K			
4	0.01uF		2.5K			

MODELGRAPH:

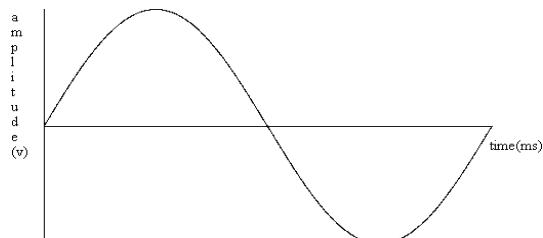

RESULT:

Thus the RC phase shift oscillator is designed and analyzed as per the design.

Designed frequency

= Obtained frequency

=

Ex.No:2(b)
Date:

DESIGN AND ANALYSIS OF WEIN BRIDGE OSCILLATOR.

AIM:

To design and analyze a wein bridge oscillator for a given frequency and test the result with the design.

EQUIPMENTS REQUIRED:

S.NO	EQUIPMENTS	RANGE	QUANTITY
1	Transistor	BC107	1
2	Resistor	470 Ω	1
3	Resistor	56KΩ, 12KΩ, 1KΩ, 1.5KΩ 1KΩ	Each 2
4	Resistor	4KΩ	1
5	Capacitor	0.1 μF, 10 μF	Each 2
6	CRO	(0-30) MHz	1
7	RPS	(0-30) V	1
8	Breadboard	-	1
9	Connecting wires	-	As required

THEORY:

Wein bridge oscillator is an audio frequency RC oscillator. The amplifier used in wein bridge oscillator is non inverting type. Here two common emitter amplifier is cascaded to produce a phase


shift of 0. Therefore the feedback network need not provide any phase shift. By changing the value of R and C in frequency sensitive arm we can change the output signal frequency. To generate low frequency audio signal wein bridge oscillators is used in signal generators.

$$\text{Frequency of oscillation} = 1 / (2\pi RC\sqrt{6})$$

PROCEDURE:

1. Design the wein bridge oscillator as per the design.
2. The connections are made as per the circuit diagram.
3. Measure the output sine wave form using CRO.
4. The value of frequency is calculated and compared with the design

CIRCUITDIAGRAM:

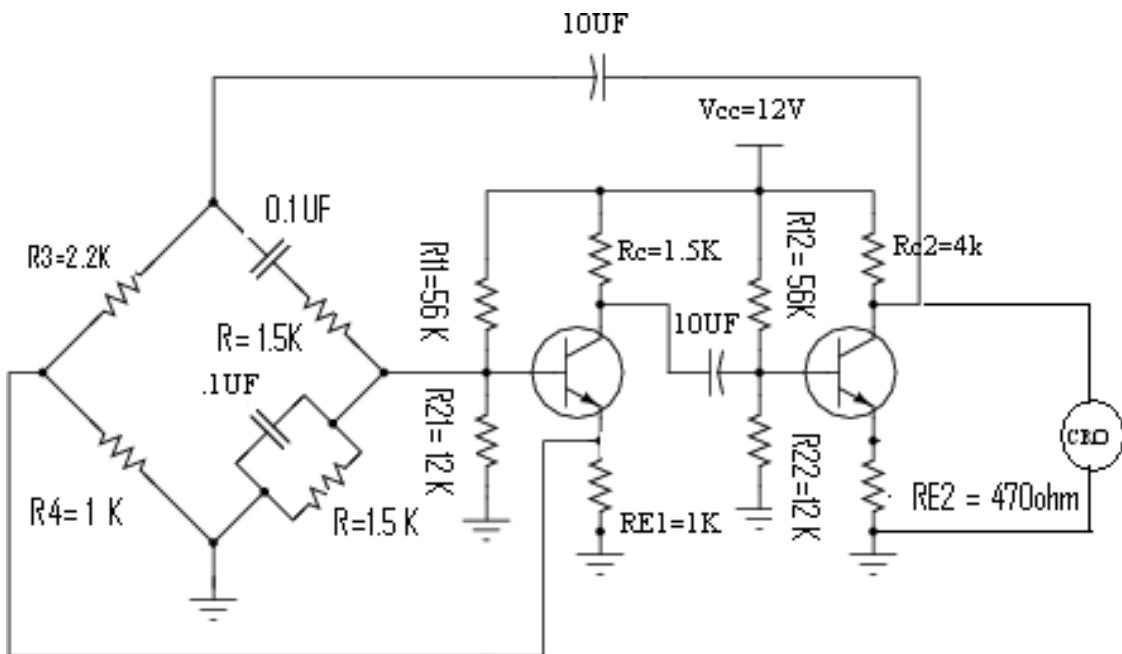

DESIGNPROCEDURE:

DesignofaTransistorcircuit1:

Assume $V_{cc}=12V$, $I_c=4mA = I_E$, $V_{CE}=V_{CC}/2=6V$, $V_E=V_{CC}/10$,

$$R_{11}=56K\Omega$$

$$Z_{parallel} = R_c / X_C = =$$

$$9.42\Omega Z_{series} = R + X_C ==$$

$$1.6K\Omega Z_f=1.61K\Omega$$

To find R_{E1} :

$$R_{E1}=V_E/I_E=1K\Omega$$

To find R_{C1}

$$R_{C1}=V_{CC}/2I_C=1.5K\Omega$$

To find R_{12}

$$R_{11} || R_{12} > 10Z_f \quad R_{12}=56K\Omega$$

DesignofaTransistorcircuit2:

Assume $V_{cc}=12V$, $I_c=1.5mA = I_E$, $V_{CE}=V_{CC}/2=6V$, $V_E=V_{CC}/10=1.2V$, $R_{22}=12K$

To find R_{E2}

$$R_{E2} = V_E/I_E = 470\Omega$$

To find R_{C2}

$$R_{C2} = V_{CC}/2I_C = 4K\Omega$$

$$V_B = V_{BE} + V_E = 1.9V$$

$$V_B = V_{CC}(R_{B2}/(R_{22}+R_{21}))$$

To find R_{21}

$$R_{21} + R_{22} > 10Z_F$$

$$R_{21} = 12K\Omega$$

Design of Tank circuit:

Assume: $f = 1 \text{ KHz}$, $C = 0.1\mu\text{F}$

$$F = 1/2\pi RCR$$

$$= 1.5K\Omega$$


Barkhausen Criterion:

$$\text{Assume } R_4 = 1K\Omega$$

$$R_3/R_4 = 2; R_3 = 2K\Omega$$

TABULATION:

S.No	Amplitude in Volts	Time period in ms	Theoretical frequency in KHz	Observed frequency in KHz

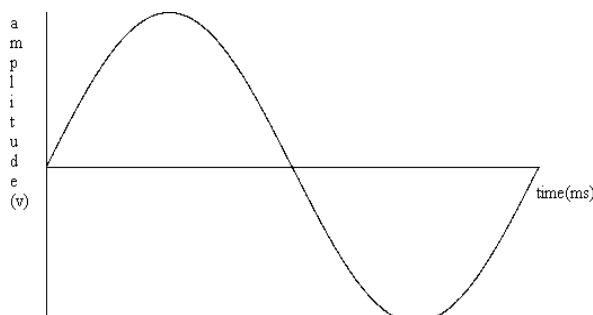MODEL GRAPH:

RESULT:

Thus the Wein bridge oscillator is designed and analyzed as per the design.

Designed frequency

= Obtained frequency =

Ex.No:3(a)	
Date:	

DESIGN AND ANALYSIS OF HARTLEY OSCILLATOR

AIM:

To design and analyze a Hartley oscillator for a given frequency and test the result with the design.

EQUIPMENTS REQUIRED:

S.NO	EQUIPMENTS	RANGE	QUANTITY
1	Transistor	BC107	1
2	Resistor	56KΩ, 2.2KΩ, 12KΩ, 470Ω	Each one
3	Capacitor	22μF, 2.2μF, 47μF, 0.01μF	Each one
4	Inductor	mH	2
5	CRO	(0-30)MHz	1
6	RPS	(0-30)V	1
7	Breadboard	-	1
8	Connecting wires	-	As required

THEORY:


When the supply voltage +V_{cc} is switched on, a transient current is produced in the tank circuit and consequently damped harmonic oscillations are set up in the circuit. The oscillatory current in the tank circuit produces ac voltages across L₁ and L₂. As terminal 3 is earthed it will beat zero potential. If terminal 1 is at positive potential with respect to 3 at any instant, terminal 2 will be a negative potential with respect to 3 at the same instant. Thus the phase difference between the terminals 1 and 2 is always

180°. In the CE mode, the transistor provides the phase difference of 180° between the input and output. Therefore the total phase shift is 360°. Thus at the frequency determinant for the tank circuit, the necessary condition for sustained oscillations is satisfied. If the feedback is adjusted so that the loop gain Aβ = 1, the circuit acts as an oscillator. In radio frequency transmitter to generate high frequency carrier signals LC oscillators are used.

PROCEDURE:

1. Design the Hartley oscillator as per the design procedure.
2. The connections are made as per the circuit diagram.
3. Measure the output sine wave form using CRO.
4. The value of frequency is calculated and compared with the design

CIRCUIT DIAGRAM:

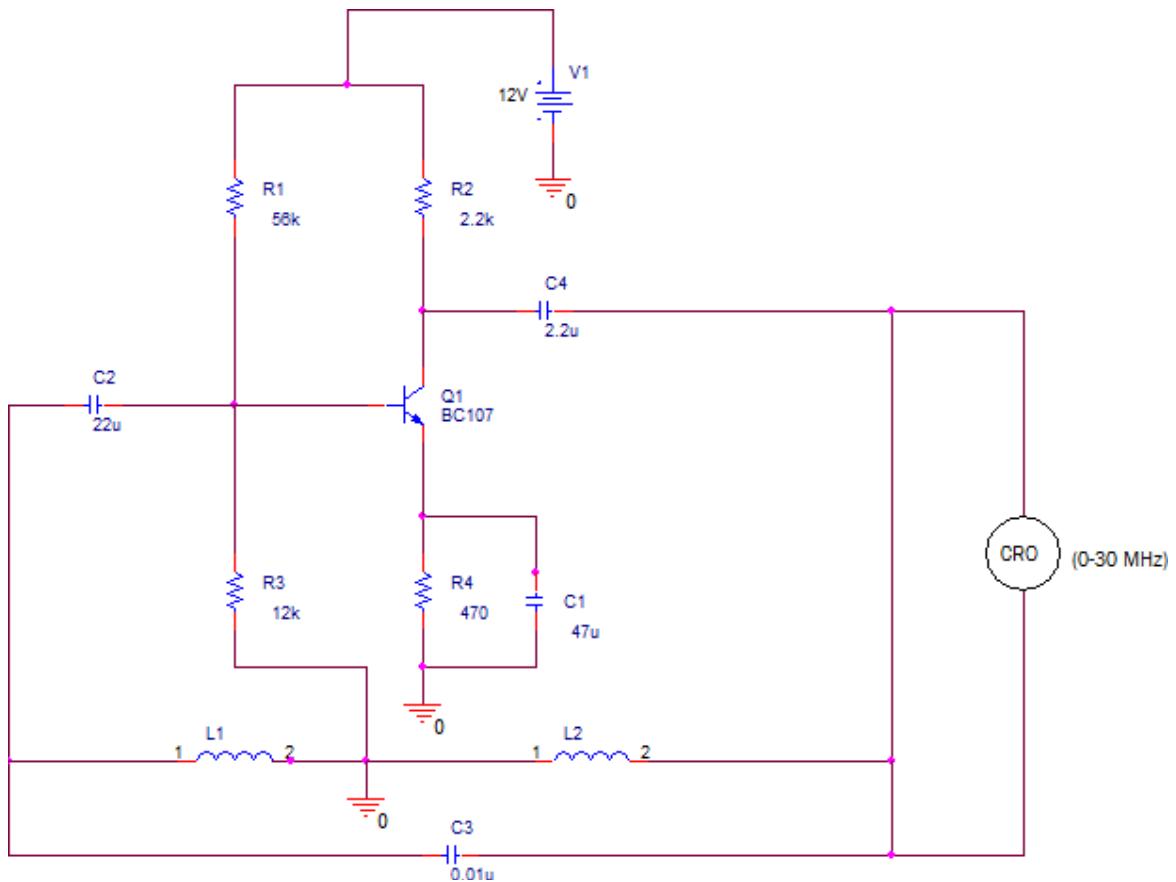

DESIGNPROCEDURE:

Design of Transistor circuit:

Assume $V_{cc} = 10V$, $I_c = 4mA = I_E$, $V_{CE} = V_{CC}/2 = 5V$, $V_E = V_{CC}/10$, $R_E = V_E / I_E = 470\Omega$

$$R_C = V_{CC} - V_{CE} - V_E$$

=
2.2KΩI_C

$$V_2 = V_{BE} + V_E = 1.7V$$

$$1+V_2=10.1VR_1$$

$$=V_1/10^*I_B=56K\Omega R_2=$$

$$V_2/9 * I_B = 12 \text{ k}\Omega$$

$$R_B = R_1 \parallel R_2 = 20.78\text{ k}\Omega F_0 =$$

10KHz

$$X_{CE}=R_E/10=47$$

$$C_E = 10/2 * F_O * R_E = 47 \mu F$$

Design of Tankcircuit:

Assume f = 30 KHz and C = 0.01 μ F Frequency of oscillation f = 1/(2 π \sqrt{LC}) Then L = 6 mH;

$$L = L_1 + L_2$$

$$\text{Let } L_1 = L_2$$

$$L_1 = L/2 = 3 \text{ mH}$$

$$L_1 = L_2 = 3 \text{ mH}$$

Barkhausen Criterion:


$$h_{fe} = L_1/L_2$$

$$= 3 \text{ mH}/3 \text{ mH} = 1$$

TABULATION:

S.No	Capacitor	Inductor ($L_1 = L_2$)	Theoretical frequency in KHz	Amplitude in Volts	Time period in ms	Observed frequency in KHz
1	0.01 μ F		40K			
2	0.01 μ F		10K			
3	0.01 μ F		20K			
4	0.01 μ F		30K			

MODELGRAPH:

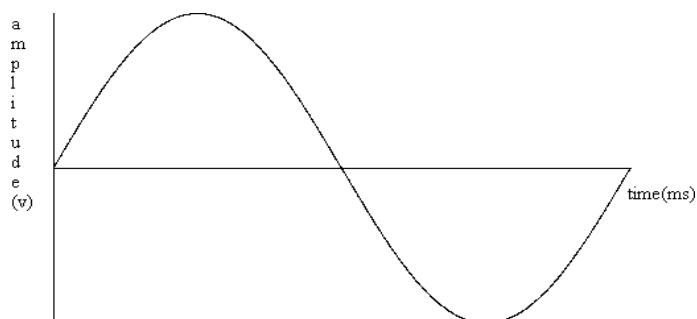

RESULT:

Thus the Hartley oscillator is designed and analyzed as per the design.

Designed frequency

= Obtained frequency =

Ex.No:3(b)
Date:

DESIGN AND ANALYSIS OF COLPITTS OSCILLATOR

AIM:

To design and construct a Colpitts oscillator for a given frequency and test the result with the design.

EQUIPMENTS REQUIRED:

S.NO	EQUIPMENTS	RANGE	QUANTITY
1	Transistor	BC107	1
2	Resistor	56KΩ, 2.2KΩ, 12KΩ, 470Ω	Each one
3	Capacitor	22μF, 2.2μF, 47μF, 0.01μF 2.2μF-1, 22μF-1, 0.01μF- 247μF- 1	
4	Inductor	mH	1
5	CRO	(0-30)MHz	1
6	RPS	(0-30)V	1
7	Breadboard	-	1
8	Connecting wires	-	As required


THEORY:

The feedback network consisting of inductors L and capacitors C₁ and C₂ determines the frequency of the oscillator. When the supply voltage +V_{cc} is switched on, a transient current is produced in the tank circuit and consequently damped harmonic oscillations are set up in the circuit. The oscillatory current in the tank circuit produces ac voltages across C₁ and C₂. As terminal 3 is earthed it will be at zero potential. If terminal 1 is at positive potential with respect to 3 at any instant, terminal 2 will be at negative potential with respect to 3 at the same instant. Thus the phase difference between the terminals 1 and 2 is always 180°. In the CE mode, the transistor provides the phase difference of 180° between the input and output. Therefore the total phase shift is 360°. Thus at the frequency determinant for the tank circuit, the necessary condition for sustained oscillations is satisfied. If the feedback is adjusted so that the loop gain Aβ = 1 the circuit acts as an oscillator. In radio frequency transmitter to generate high frequency carrier signals LC oscillators are used.

PROCEDURE:

1. Design the Colpitts oscillator as per the design procedure.
2. The connections are made as per the circuit diagram.
3. Measure the output sine wave form using CRO.
4. The value of frequency is calculated and compared with the design.

CIRCUITDIAGRAM:

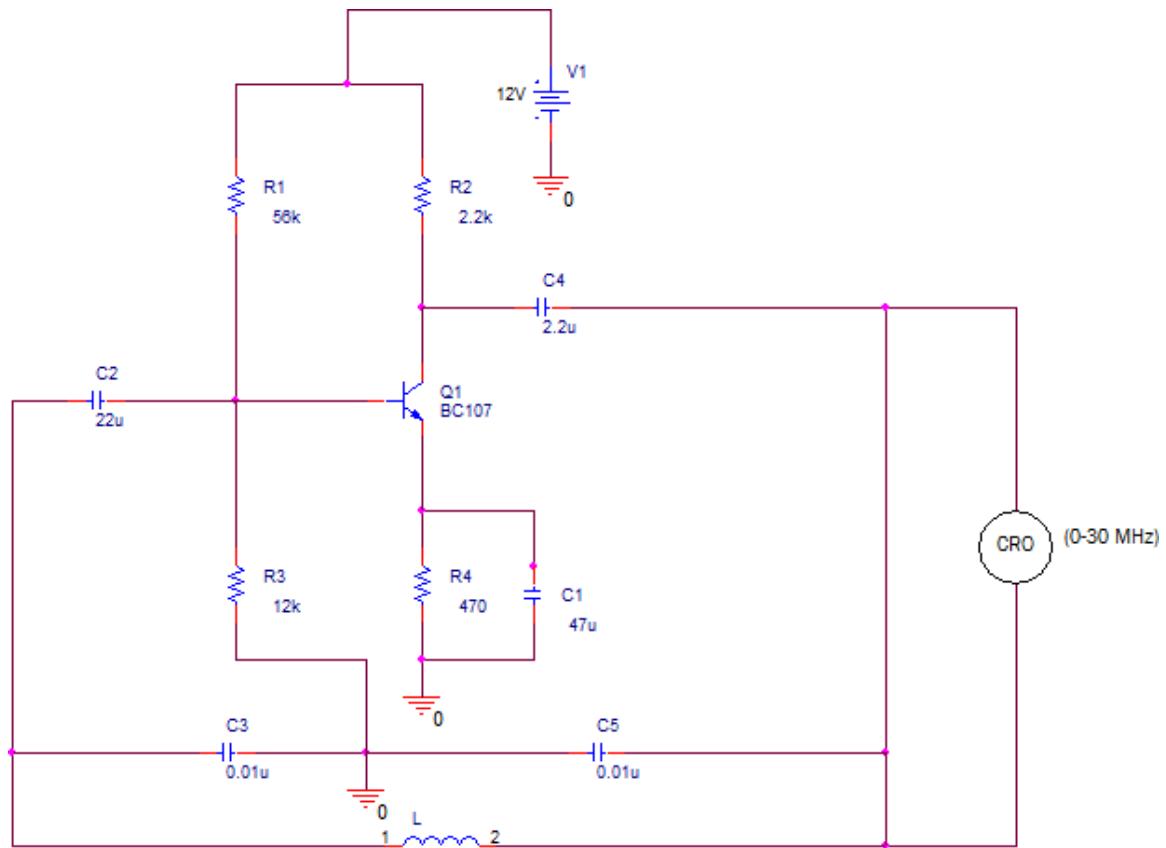

DESIGNPROCEDURE:

Assume $f = 30$ KHz and $L = 5\text{mH}$,

$$C = 5.6\text{nF} \quad \text{Frequency of oscillation } f = 1 / (2\pi\sqrt{LC})$$

$$\text{And } C = C_1 C_2 / (C_1 + C_2)$$

$$\text{Let } C_1 = 0.01\mu\text{F}$$

$$\Rightarrow C_2 = 0.01\mu\text{F}$$

BarkhausenCriterion:


$$h_{fe} = C_1 / C_2$$

$$= 0.01\mu\text{F} / 0.01\mu\text{F} = 1$$

TABULATION:

S.No	Capacitor (C ₁ =C ₂)	Inductor L	Theoretical frequency inKHz	Amplitude inVolts	Time period inms	Observed frequency inKHz
1	0.01uF		40K			
2	0.01uF		10K			
3	0.01uF		20K			
4	0.01uF		30K			

MODELGRAPH:

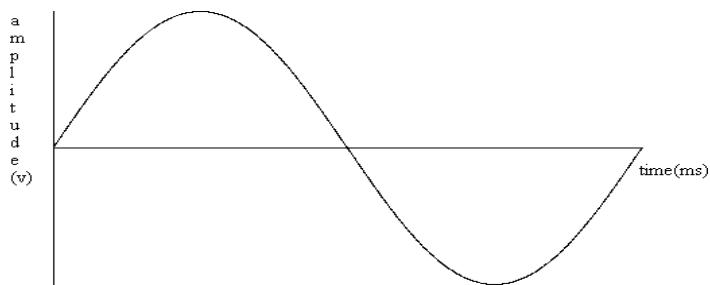

RESULT:

Thus the Colpitts oscillator is designed and analyzed as per the design.

Designed frequency

= Obtained frequency =

Ex.No:4	DESIGN AND ANALYSIS OF RC INTEGRATOR & DIFFERENTIATOR
Date:	

AIM:

To design and analyze the RC integrator, differentiator circuits.

EQUIPMENTS REQUIRED:

S.NO	EQUIPMENTS	RANGE	QUANTITY
1	Resistor	1KΩ	1
2	Capacitor	0.1uF	1
3	CRO	(0-30)MHz	1
4	Function generator	(0-3)MHz	1
5	Breadboard	-	1
6	Connecting wires	-	As required

THEORY:

INTEGRATOR:

For a low pass RC circuit, if the time constant is very large as compared to the time required by the input signal to make an appreciable change, the circuit acts as an integrator. Under this case, the drop across C is negligible compared to drop across R. Thus the entire input $V_i(t)$ can be assumed to be appearing across R. Then the current i is given by, $V_r = V_i = iR$; $i = V_i / R$

DIFFERENTIATOR:

For a high pass RC circuit, if time constant is very small as compared to the time required by the input signal to make an appreciable change the circuit acts as a differentiator.

$$i = C \left(\frac{dV_c}{dt} \right)$$

$$/$$

$$dt) V_o = i$$


$$R$$

$$V_o = RC \left(\frac{dV_i}{dt} \right)$$

PROCEDURE:

1. The circuit connections are made as per the circuit diagram Integrator.
2. Apply the square wave as a input signal to the circuit.
3. The time period and amplitude of the output wave is noted from CRO and the waveform is drawn in a graph.
4. Interchange the resistor and capacitor position to get Differentiator circuit, then perform the steps 1, 2, 3.


INTEGRATOR:

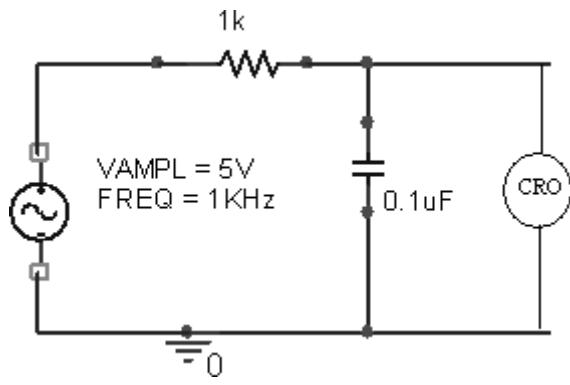


TABULATION:

S.No	Amplitude in V	Time period in ms

MODELGRAPH:

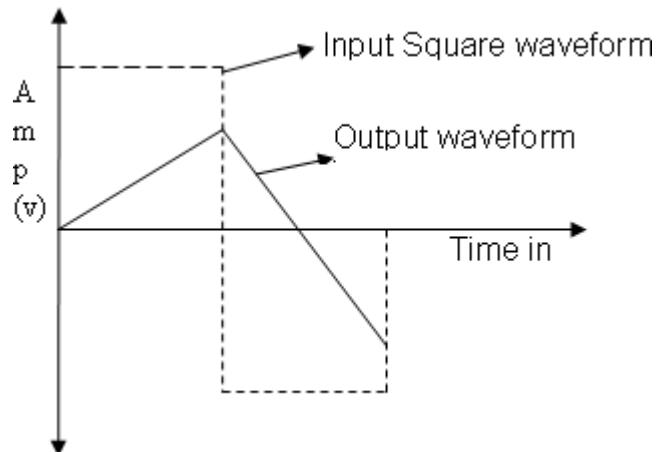


DIFFERENTIATOR:

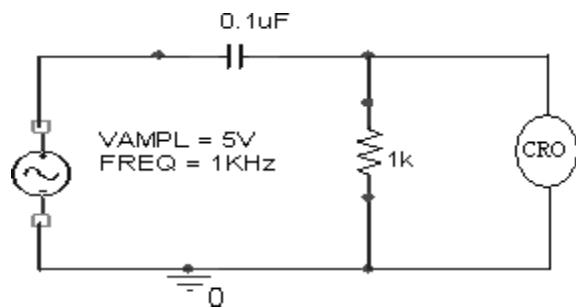

TABULATION:

S.No	Amplitude in V	Time period in ms

MODELGRAPH:

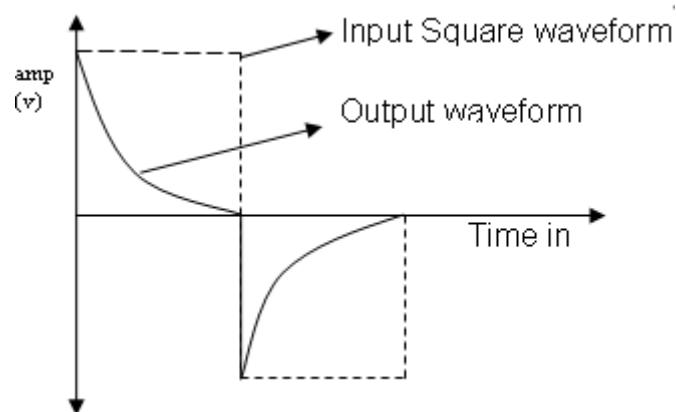

RESULT:

Ex.No:5	
Date:	

DESIGN AND ANALYSIS OF CLIPPERS & CLAMPERS

AIM:

To design and analyze the clippers, clampers circuits.

EQUIPMENTS REQUIRED:

S.NO	EQUIPMENTS	RANGE	QUANTITY
1	Diode	IN4007	1
2	Resistor	1K	1
3	Capacitor	0.1uF	1
4	CRO	(0-30)MHz	1
5	RPS	(0-30)V	1
6	Breadboard	-	1
7	Connecting wires	-	As required

THEORY:

CLIPPER:

Clipper is a circuit which is used to clip off unwanted portion of the waveform, without distorting the remaining part of the waveform. When the diode is connected in series with the load, such a circuit is called a series clipper. The clipper level is determined by the reference voltage V_{ref} and could be obtained by the supply voltage.

When the supply voltage is positive, the circuit is said to be positive reference clipper.

CLAMPER:

The clamper which is used to add a dc level as per the requirements to the ac output signal is called clamps. The capacitor, diode and resistors are the 3 basic elements of a clamper circuit. They are also called as dc inserter circuits or dc resonators. They are positive and negative clamps depending on whether positive or negative dc shift is introduced. A positive clamper adds a positive level to the ac output. During the positive half cycle of V_i , the diode is reverse biased and the capacitor starts discharge. During the negative half cycle, the diode gets forward biased and the capacitor charges to maximum level V_m . A negative clamper adds a negative level to the ac output.


PROCEDURE:

1. The circuit connections are made as per the circuit diagram.
2. Apply the sine wave as an input signal to the circuit.

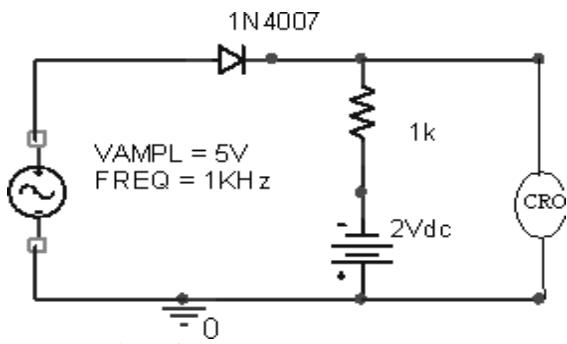3. The time period and amplitude of the output wave is noted from CRO and the waveform is drawn in a graph.
4. Repeat the above procedures for all the circuit diagram drawn in a graph.
5. Repeat the above procedures for all the circuit diagram.

SERIESCLIPPERS:


Negative clipper with negative reference:




TABULATION:

S.No	Amplitude in V	Time period in ms

MODELGRAPH:

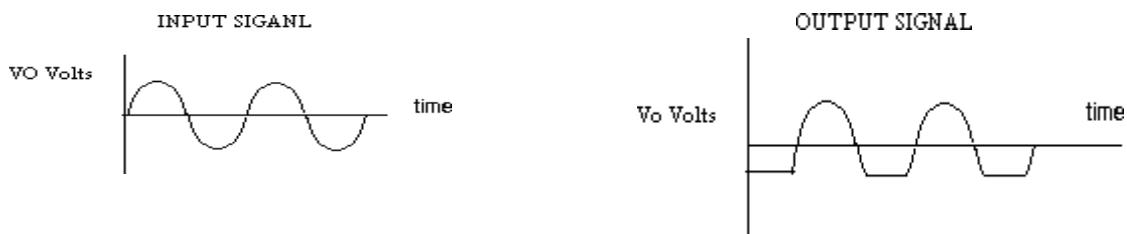

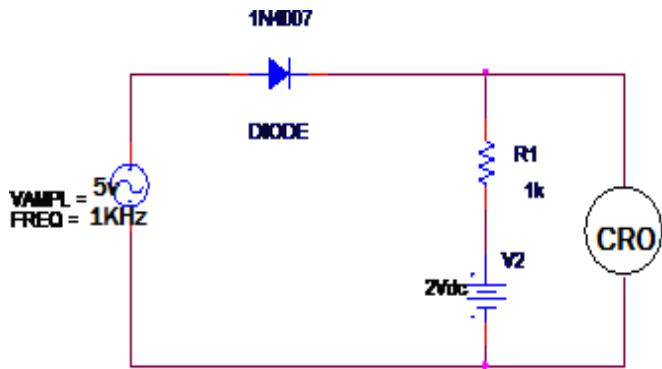
Negative clipper with positive reference:



TABULATION:


S.No	Amplitude in V	Time period in ms

MODELGRAPH:

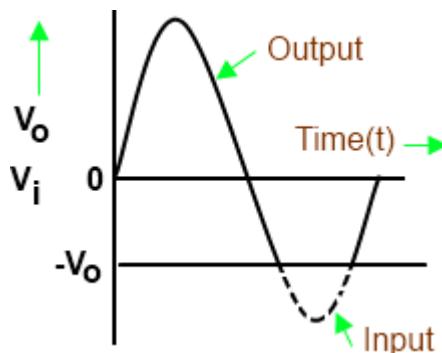

PARALLELCLIPPERS:

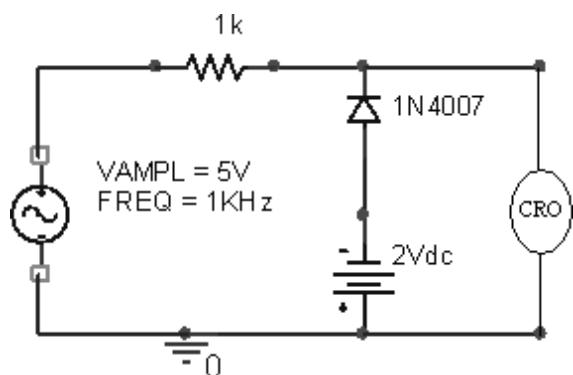
Negative clipper with negative reference:




TABULATION:

S.No	Amplitude in V	Time period in ms

MODELGRAPH:

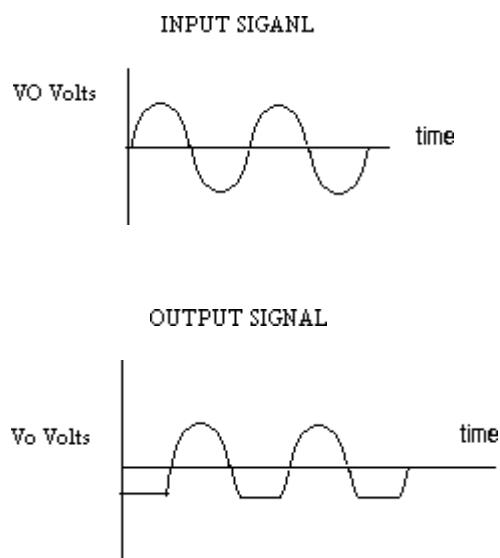

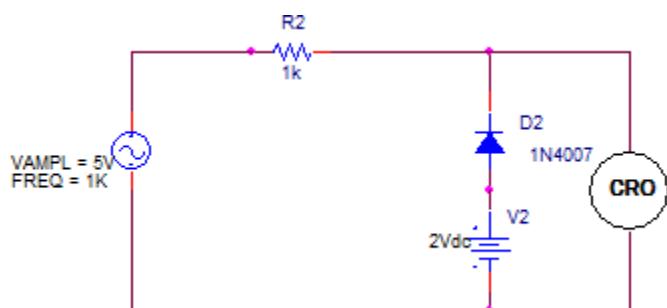
Negative clipper with positive reference:



TABULATION:

S.No	Amplitude in V	Time period in ms


MODELGRAPH

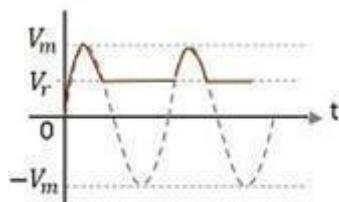

Practical Output
Waveform

CLAMPER:


Positiveclamper:

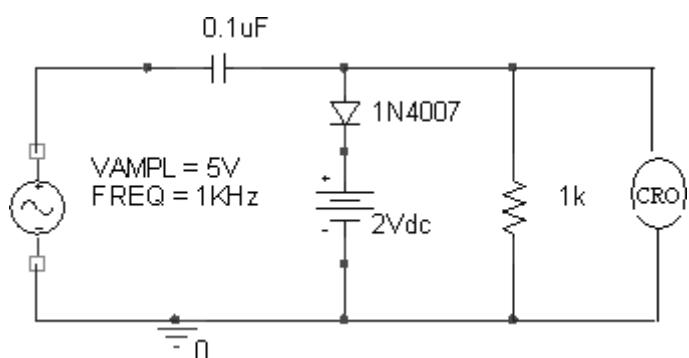


TABULATION:

S.No	Amplitude in V	Time period in ms

MODELGRAPH:

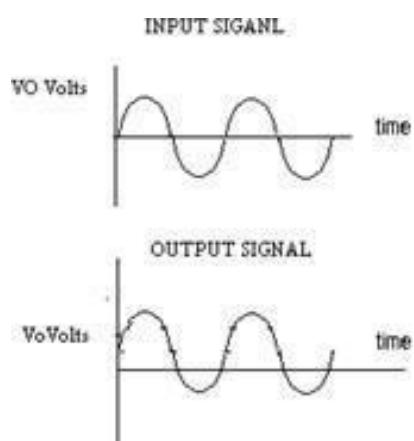

NegativeClamper:

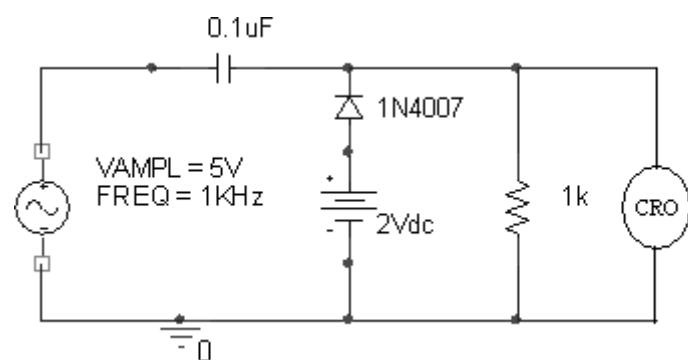


TABULATION:


S.No	Amplitude in V	Time period in ms

MODELGRAPH:

INPUT SIGNAL

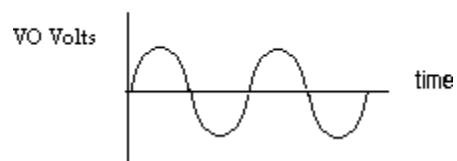

OUTPUT SIGNAL

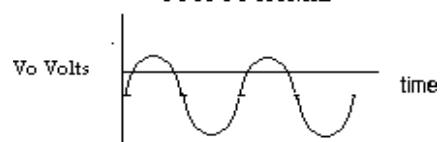

RESULT:

Date:

Aim: To design an instrumentation amplifier and obtain the output for various gain.

Apparatus Required:

S.NO.	COMPONENTS NAME	SPECIFICATION & RANGE	QUANTITY
1.	Bread board	-	1
2.	Opamp	IC741	3
3.	Function generator	3MHz	2
4.	CRO	30MHz	1
5.	Dual power supply	+12/-12V	1
6.	Resistors		Each 1
7.	Connecting wires	Single strand	As required

Theory:

Instrumentation amplifier is a kind of differential amplifier with additional input buffer stages. The addition of input buffer stages makes it easy to match (impedance matching) the amplifier with the preceding stage. Instrumentation are commonly used in industrial test and measurement application. The instrumentation amplifier also has some useful features like low offset voltage, high CMRR (Common mode rejection ratio), high input resistance, high gain etc.


The two non-inverting amplifiers form a differential input stage acting as buffer amplifiers with a gain of $1 + 2R_2/R_1$ for differential input signals and unity gain for common mode input signals. Since amplifiers A1 and A2 are closed loop negative feedback amplifiers, we can expect the voltage at V_a to be equal to the input voltage V₁. Likewise, the voltage at V_b to be equal to the value at V₂.

As the op-amps take no current at their input terminals (virtual earth), the same current must flow through the three resistor network of R₂, R₁ and R₂ connected across the op-amp outputs. This means that the voltage on the upper end of R₁ will be equal to V₁ and the voltage at the lower end of R₁ to be equal to V₂.

The voltage output from the differential op-amp A₃ acting as a subtractor, is simply the difference between its two inputs (V₂ - V₁) and which is amplified by the gain of A₃ which may be one, unity, (assuming that R₃ = R₄). Then we have a general expression for overall voltage gain of the instrumentation amplifier circuit as:

$$out = V - \frac{[1 + \frac{2R_2}{R_1}]\frac{R_4}{R_3}}{R_1 R_3}$$

Instrumentation Amplifier Circuit:

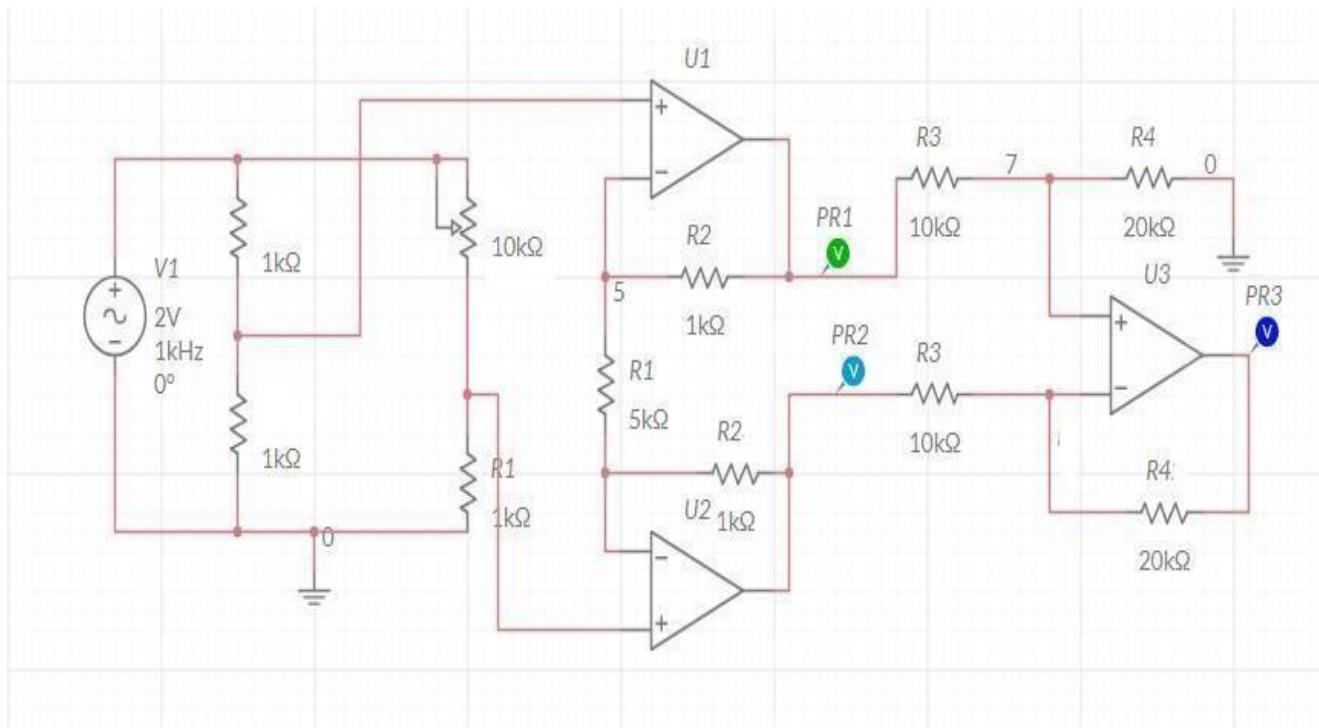

Procedure:


1. Connections are given as per the circuit diagram.
2. Input signal is connected to the circuit from the signal generator.
3. The input and output signals of the circuit observed from the dual channels 1 and 2 of the CRO.
4. Suitable voltage sensitivity and time-base on CRO is selected.
5. Change the gain setting resistor value and observe the output.

Design:

Tabulation:

Input /Output	Theoretical			Practical		
	Amplitude	Time				
Input						
Output	V1	V2	Vo	V1	V2	Vo

Output:

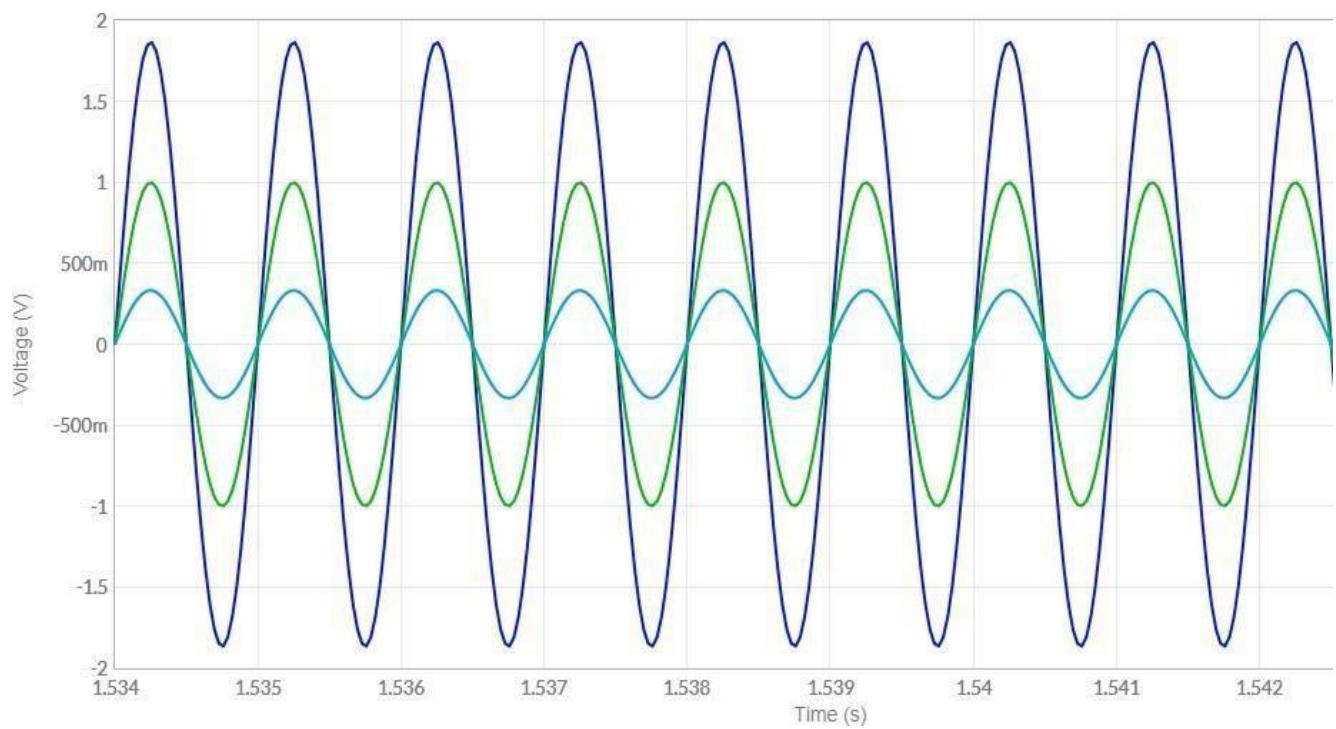

Result:

Thus the instrumentation amplifier was designed and verified.

Exp.No:7 ActiveLowPass,HighPassandBandPassFilters

Date:

Aim:

To design Low pass, High pass and Band pass active filters using Op-amp and obtain frequency response.

Apparatus Required:

S.NO.	COMPONENTS NAME	SPECIFICATION & RANGE	QUANTITY
1.	Bread board	-	1
2.	Op-amp	IC741	1
3.	CRO	30MHz	1
4.	Dual Powersupply	+12/-12V	1
5.	Capacitor		Each1
6.	Resistors		Each1
7.	Function generator	3 MHz	1
8.	Connecting wires	Single strand	As required

Theory:

A filter is often used in electronic circuits to block (or allow) a select frequency to the circuit. A op-amp is used to design filters, so it is called Active filters. There are four types of active filters like Lowpass, High pass, band pass and band stop. A low pass filter is used in circuits that only allow low frequencies to pass through (below the cutoff frequency). It is often used to block high frequencies and AC current in a circuit. A high pass filter is used in circuits that only require high frequencies to operate (above the cut off frequency). It blocks most low frequencies & DC component. A band pass filter is a combination of a high pass and a low pass filter. It allows only a select range of frequencies to pass through. It is designed such away that the cutoff frequency of the low pass filter is higher than the cutoff frequency of the high pass filter, hence allowing only a select range of the frequencies to pass through.

Procedure:


1. Connections are given as per the circuit diagram.
2. Input signal is connected to the circuit from the signal generator.
3. The input and output signals of the filter channels 1 and 2 of the CRO are reconnected.
4. Suitable voltage sensitivity and time-base on CRO is selected.
5. The correct polarity is checked.
6. The above steps are repeated for second order filter.

DesignLowPassFilter:


Design Second order Butterworth LowPassfilter having uppercutofffrequency 1KHz anddetermineitsfrequencyresponse.

The following steps are used for the design of active LPF.


1. The value of high cut off frequency f_H is chosen.
2. The value of capacitor C is selected such that its value is $\leq 1 \mu F$.
3. By knowing the values of f_H and C , the value of R can be calculated using
$$f = \frac{1}{2\pi RC}$$
4. Finally the values of R_1 and R_f are selected depending on the designed passband gain by using
$$A = 1 + \left| \frac{R}{f} \right|$$

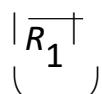

LowPassfilterCircuit:

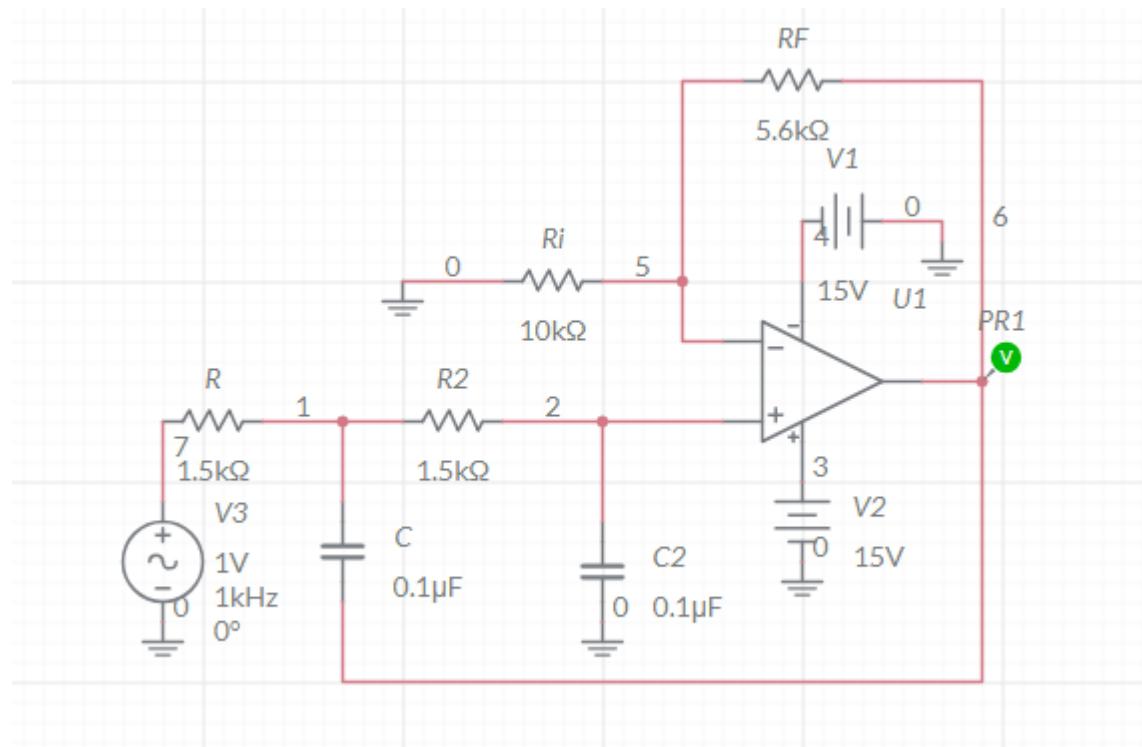

Output:

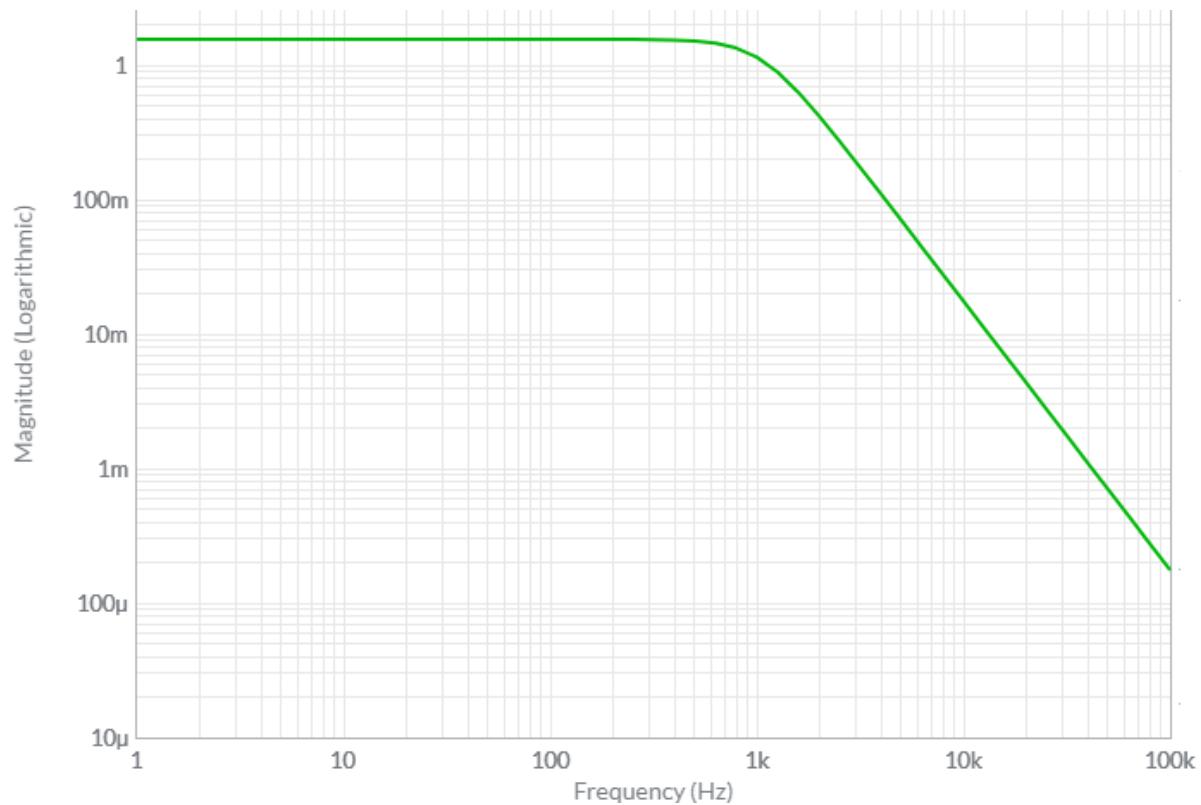

LowPassFilterTabulation:

SecondorderHighPassFilter:

The high pass filter is the complement of the low pass filter. Thus the high pass filter can be obtained by interchanging R and C in the circuit of low pass configuration. A high pass filter allows only frequencies above a certain break point to pass through and after terminates the low frequency components. The range of frequencies beyond its lower cutoff frequency f_L is called stopband.

Design:-

$$f_L = 1 \text{ KHz}, C = 0.1 \mu F, Gain, Av = 2$$

$$f_L = \frac{1}{2\pi \sqrt{R_2 R_3 C_2 C_3}}$$

$$\begin{aligned} Let R_2 &= R_3 = RC_2 = C \\ &C_3 = C \end{aligned}$$


$$R_2 = R_3 = \frac{1}{2\pi f L C}$$

$$R_2 = R_3 = 1.5 k\Omega$$


$$A = 1 + \frac{R_f}{R_1} = 2$$

$$\therefore R_f = R_1 = 10 k\Omega \text{ (given)}$$

SecondorderHighPassFilterCircuit:

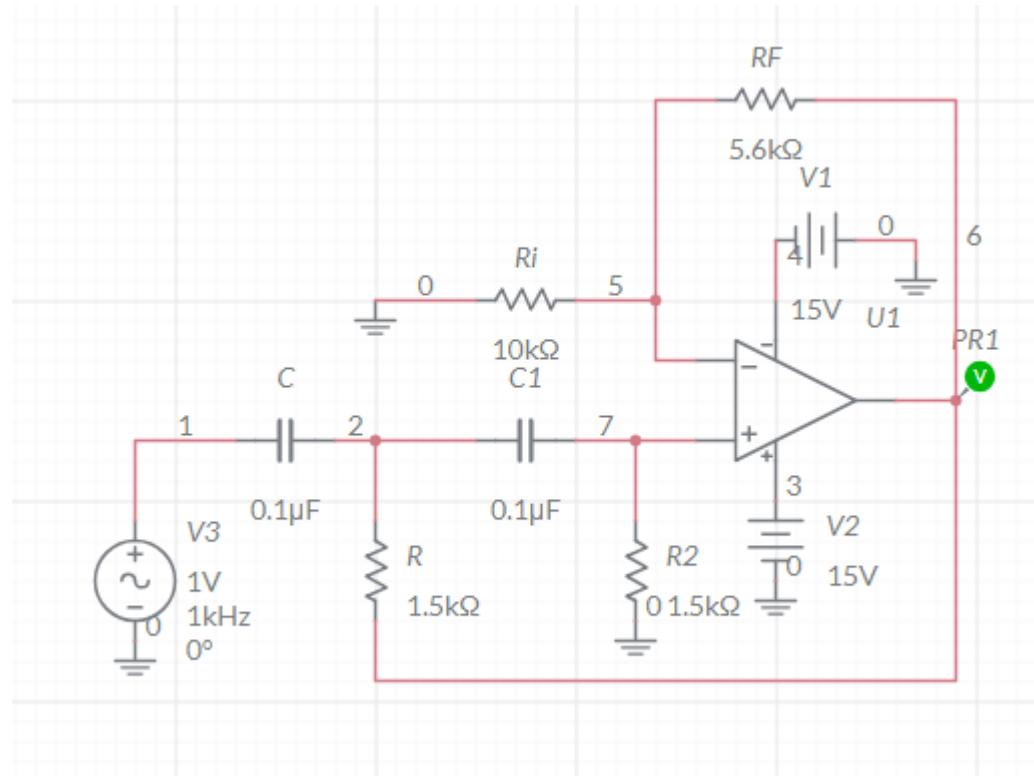

Output:

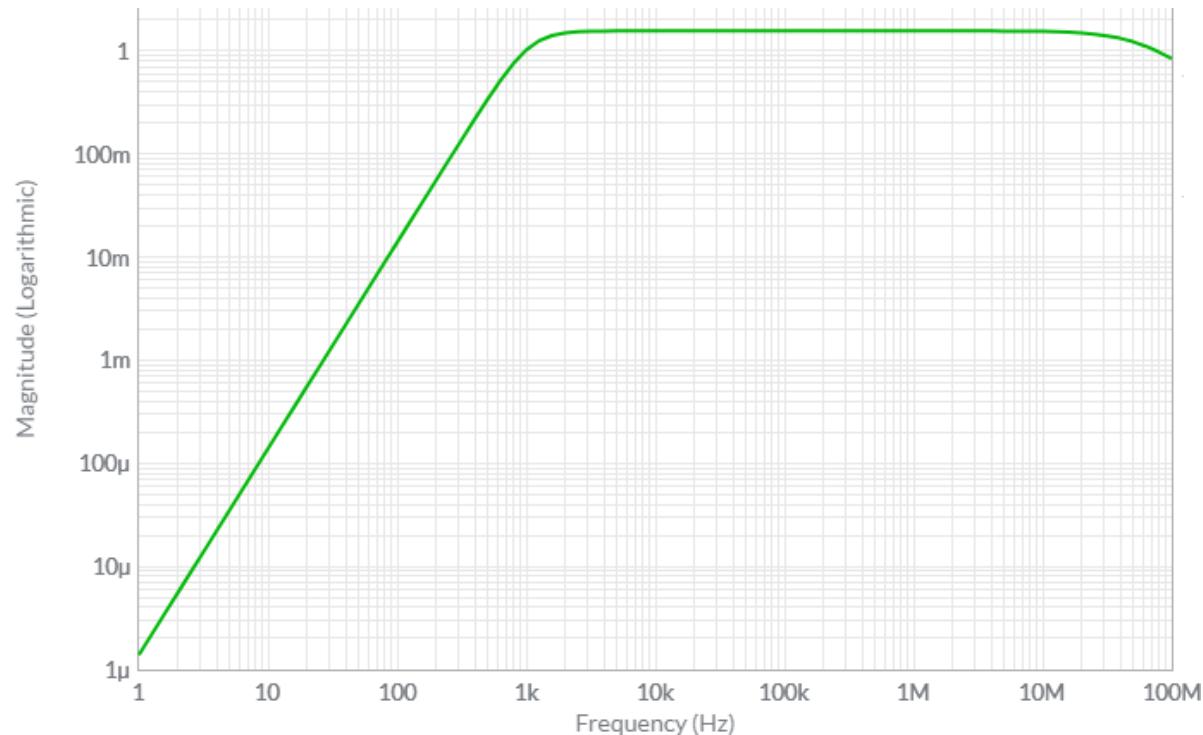

HighPassFilterTabulation:

BPF:-


The BPF is the combination of high and low pass filters and this allows a specified range of frequencies to pass through. It has two stop bands in range of frequencies between 0 to f_L and beyond f_H . The band b/w f_L and f_H is called pass band. Hence its bandwidth is $(f_H - f_L)$. This filter has a maximum gain at the resonant frequency (f_r) which is defined as

$$f_r = \sqrt{f_H f_L}$$


The figure of merit (or) quality factor Q is given by

$$Q = \frac{f_r}{\frac{f_r}{f_H - f_L}} = \frac{f_r}{BW}$$

BandPassFilterCircuit:

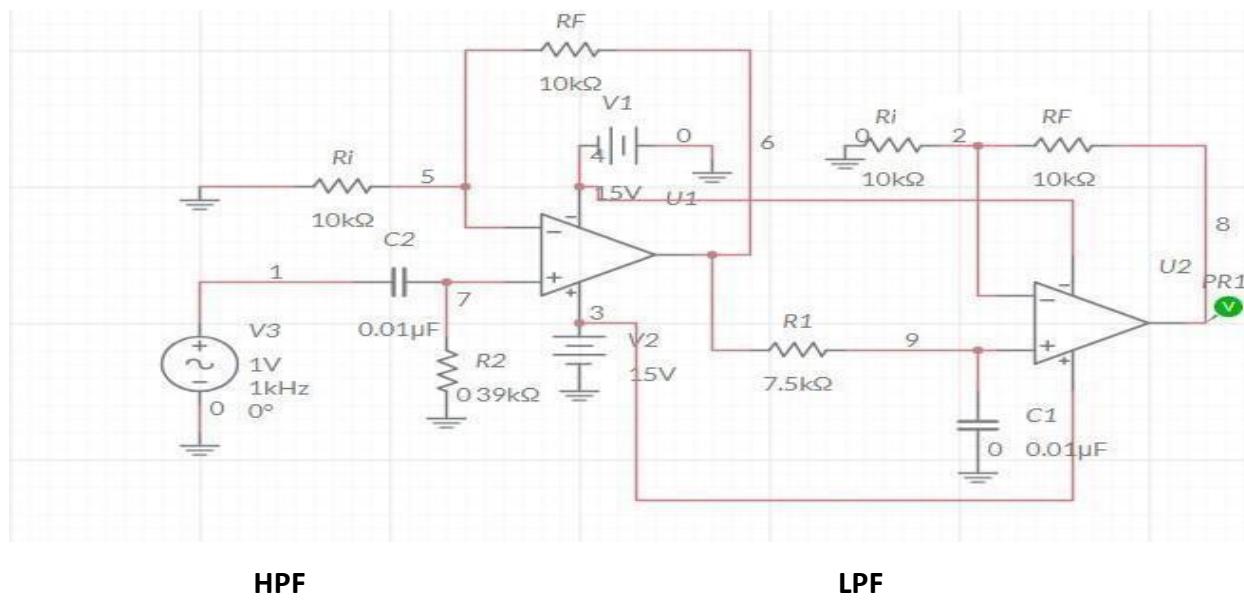

Output:

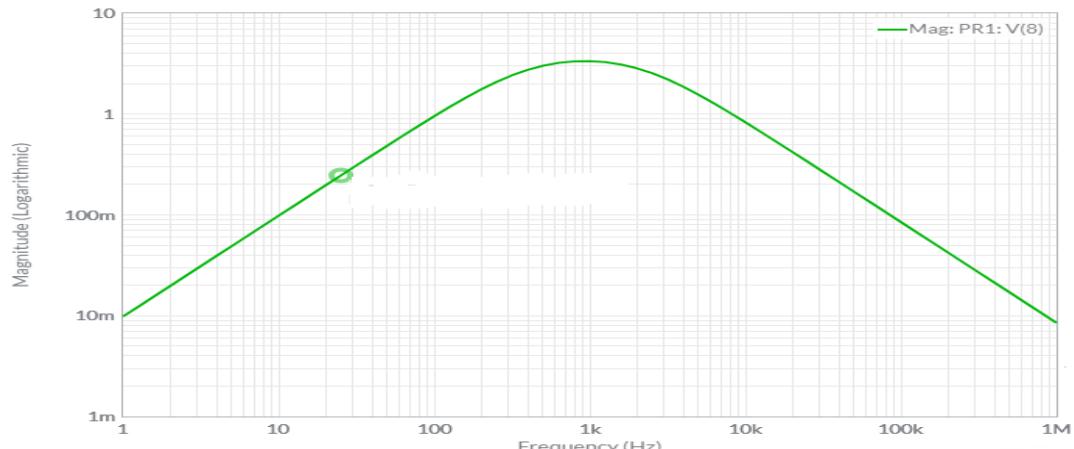

Result:

The circuit was designed and their frequency responses were replotted.

Lowpassfilter:

The upper cutoff frequency (Designed)= KHz.

The upper cutoff frequency (Obtained)= KHz.

Highpassfilter:

The lower cutoff frequency (Designed)= KHz.

The lower cutoff frequency (Obtained) = KHz.

Bandpass filter:

Centre Frequency = KHz.

Quality Factor =

Ex.No: 8

PLL characteristics and its uses as Frequency Multiplier, Clock synchronization.

e:

Aim:


- 1. To study the PLL characteristics.**
- 2. To use PLL as frequency multiplier and clock synchronization.**

Apparatus Required:

S.NO.	EQUIPMENTS & COMPONENTS	SPECIFICATION	QUANTITY
1.	Bread board	-	1
2.	IC	IC565, IC7490	1
3.	Resistors	20K, 2K, 10K, 4.7K	Each 1
	Capacitor	0.001μF, 10μF, 0.01μF	Each 1
4.	Function generator	3 MHz	1
5.	CRO	30MHz	1
6.	Dual power supply	+6/-6V	1
7.	Connecting wires	Single strand	10 wires

Theory:

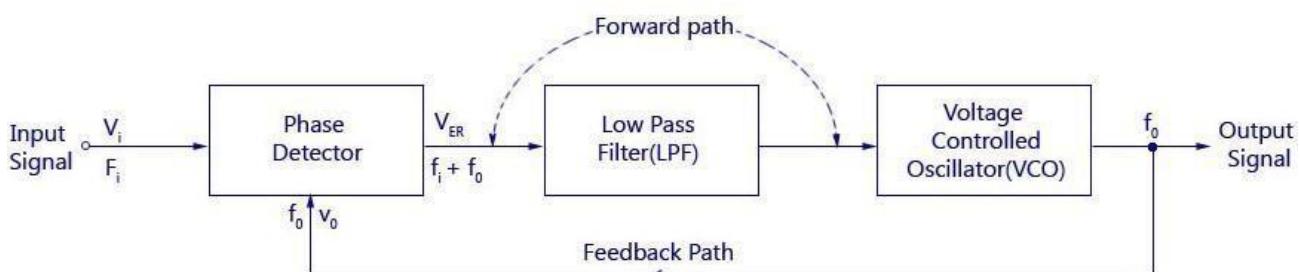
The PLL IC 565 is usable over the frequency range 0.1 Hz to 500 kHz. It has highly stable centre frequency and is able to achieve very linear FM detection. The output of VCO is capable of producing TTL compatible square wave. The dual supply is in the range of ±6V to ±12V. The IC can also be operated from single supply in the range 12V to 24V.



The phase locked loop consists of a phase detector, a voltage control oscillator and, in between them, a low pass filter is fixed. The input signal „Vi“ with an input frequency „Fi“ is conceded by a phase detector. Basically the phase detector is a comparator which compares the input frequency through the

feedback frequency f_o . The output of the phase detector is $(f_i + f_o)$ which is a DC voltage. The output of the phase detector, i.e., DC voltage is input to the lowpass filter (LPF); it removes the high-frequency noise and produces a steady DC level, i.e., $F_i - F_o$. The V_f is also a dynamic characteristic of the PLL.

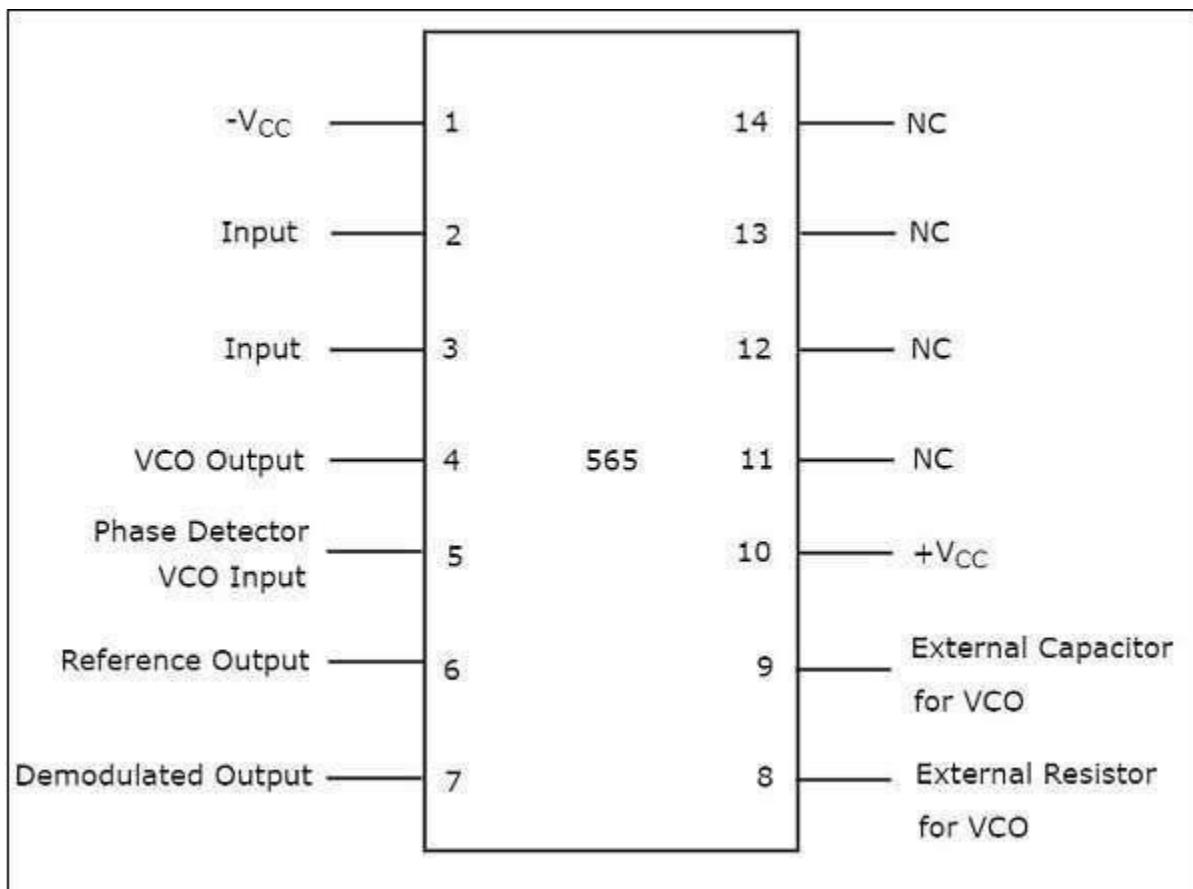The following figure shows the pin-out and the internal blocks schematic of PLLICLM565.



Design:

Center frequency or VCO frequency

$$f_{out} = \frac{1.2}{4RC} \text{ Hz}$$

$$Lockinrange = f = \pm 8 \text{ Hz} ; \quad V = V^+ - (V^-)$$

$$L \quad V$$

$$Capture range = f = \pm \left[\frac{f_L}{2\pi \times 3.6 \times 10^3 \times C_2} \right]^2 -$$

PLL used as Frequency Multiplier:

Design:


Let $V_+ = 10V$ and $V_- = -10V$

Let the input frequency be 1Khz, and the output frequency 5Khz, VCO should run at 5Khz frequency, $f_o = (1.2/4 \cdot R_1 \cdot C_1) = 5\text{Khz}$

Take $C_1 = 0.01\mu\text{F}$ Then $R_1 = 6\text{K}$ Take

$C_2 = 10\mu\text{F}$ and $C_3 = 0.001\mu\text{F}$

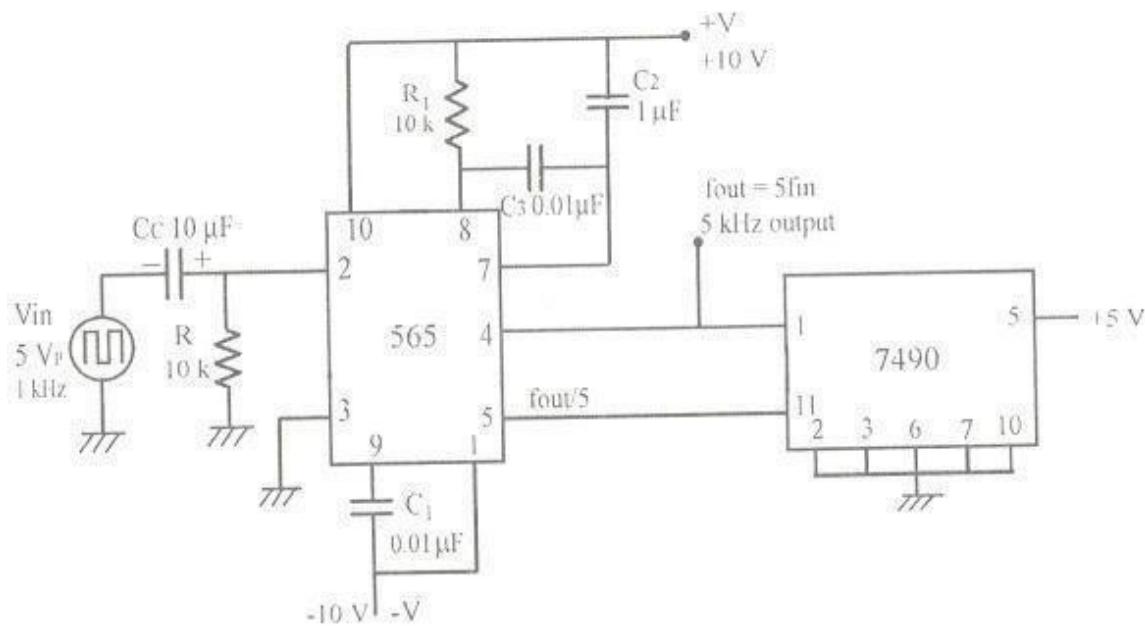
use $C_c = 10\mu\text{F}$ and $R = 10\text{k}$ for accoupling of input signal



Procedure:

- Check the component using multimeter
- setup the circuit stage by stage on the breadboard
- verify the working of circuit separately.
- complete the circuit and apply 5Vp-p, 1Khz square wave
- observe the multiplied frequency output on the CRO
- plot the output waveform on the graph sheet

Output waveform:

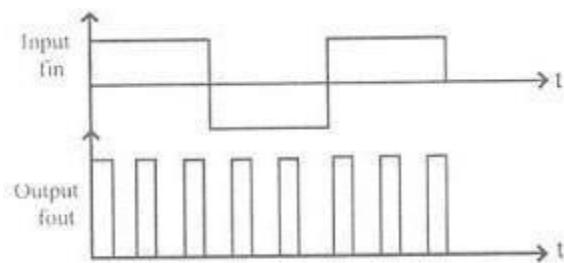

Result:

Thus, the PLL circuit was assembled successfully.

Ex.No:9

R-2RLadderTypeD-AConverter using Op-amp.

Date:

Aim:

To design R-2R Ladder Type D-A Converter using Op-amp and observe the output.

Apparatus required:

S.NO.	EQUIPMENTS & COMPONENTS	SPECIFICATION	QUANTITY
1.	Bread board	-	1
2.	Op-amp	IC741	1
3.	Resistors	2.5K	5
4.	Function generator	3 MHz	1
5.	CRO	30MHz	1
6.	Dual power supply	+6/-6V	1
7.	Connecting wires	Single strand	10 wires

Theory:


A digital-to-analog converter (DAC, D/A, D2A or D-to-A) is a circuit that converts digital data (usually binary) into an analog signal (current or voltage). One important specification of a DAC is its resolution. It can be defined by the numbers of bits or its step size. Wide range of resistors used Weighted Resistor type DAC. This can be avoided by using R-2R ladder type DAC where only two values of resistors are required.

Basic Block diagram of DAC.

The output voltage of DAC;


$$V_0 = (d_1 2^{-1} + d_2 2^{-2} + \dots + d_n 2^{-n})$$

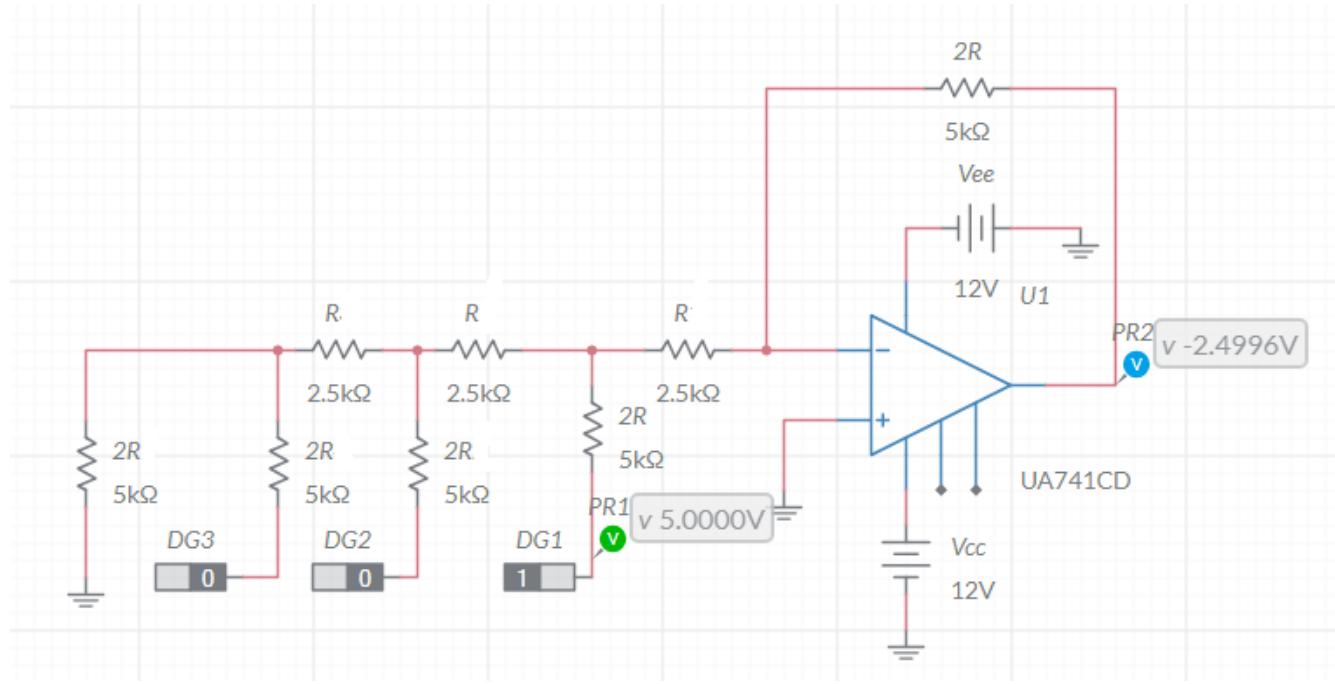To design 3 bit R-2R Digital to Analog converter to convert analog voltage of binary bit 100.



Theoretical Calculation:

If binary bit011 :

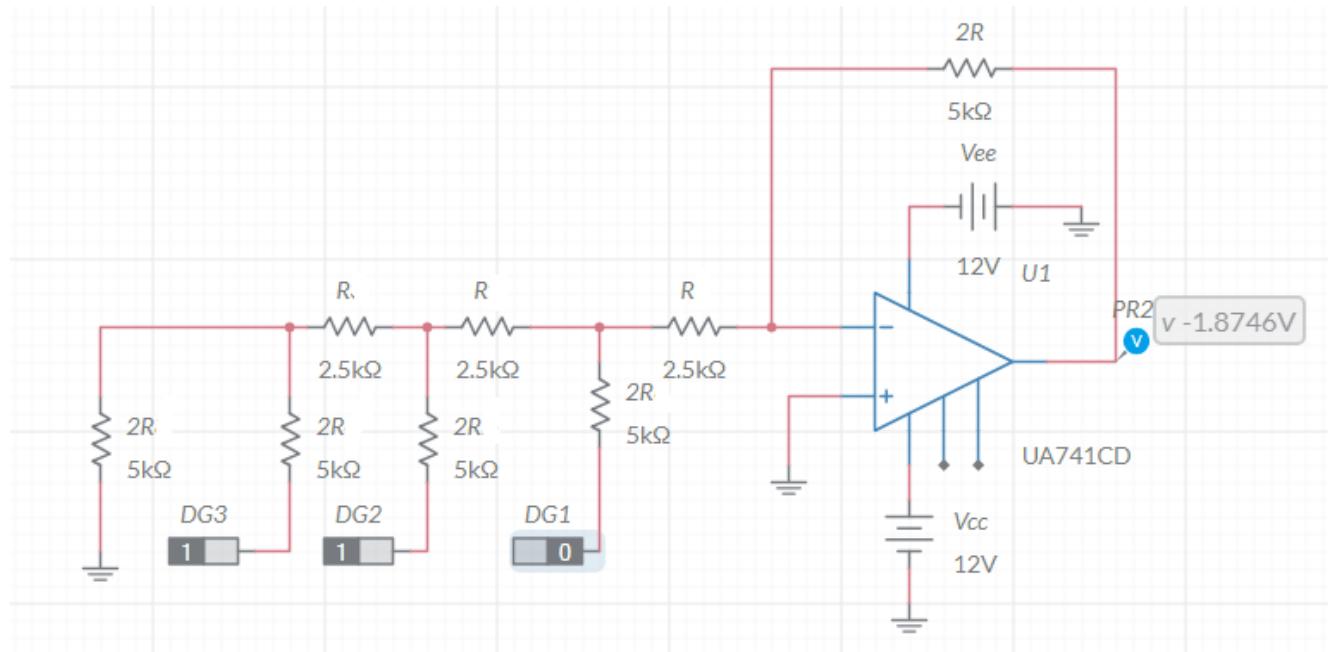

Tabulation:

$$V_{ref} = -5V$$

d1	d2	d3	Theoretical V0	Practical V0
0	0	0		
0	0	1		
0	1	1		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Procedure:

- Check the component using multimeter.
- Setup the circuit stage by stage on the breadboard
- Verify the working of circuit separately.
- Complete the circuit and apply $-5V$ ref if bit=1.
- Observe the output using multimeter.
- Plot the output waveform on the graph sheet.

Result:

Thus the R-2RLadder type using op-amp were designed and its output waveform were plotted

Ex.No:1	TUNED COLLECTOR OSCILLATOR
Date:	

AIM

To construct and simulate the Tuned collector oscillator by using gspice.


SOFTWARE USED

ORCAD 16.0


PROCEDURE

1. ORCAD-capture
2. Maximize the session log.
3. In file, open a new project and give the name to the project and choose analog or mixed A/B and specify the location say D:/ECEII
4. Create a blank project.
5. Click inside the window once and the tool bar appears.
6. Choose place part-add library-select a component in the library and select all the components -click open to add all the components.
7. Choose the components from the library and place in the worksheet.
8. Give connection using wire and properly ground the circuit.
9. Save the project and simulate it.
10. Place the marker at the points wherever the waveforms are to be viewed.
11. Click the option RUN and the output will be displayed.
12. If there are errors, correct and simulate it.
13. To view the waveform separately in plot-add plot to window-cut and paste the required waveforms.
14. The required input and output waveforms are taken printout.

CIRCUITDAIGRAM:
TUNEDCOLLECTOROSCILLATOR

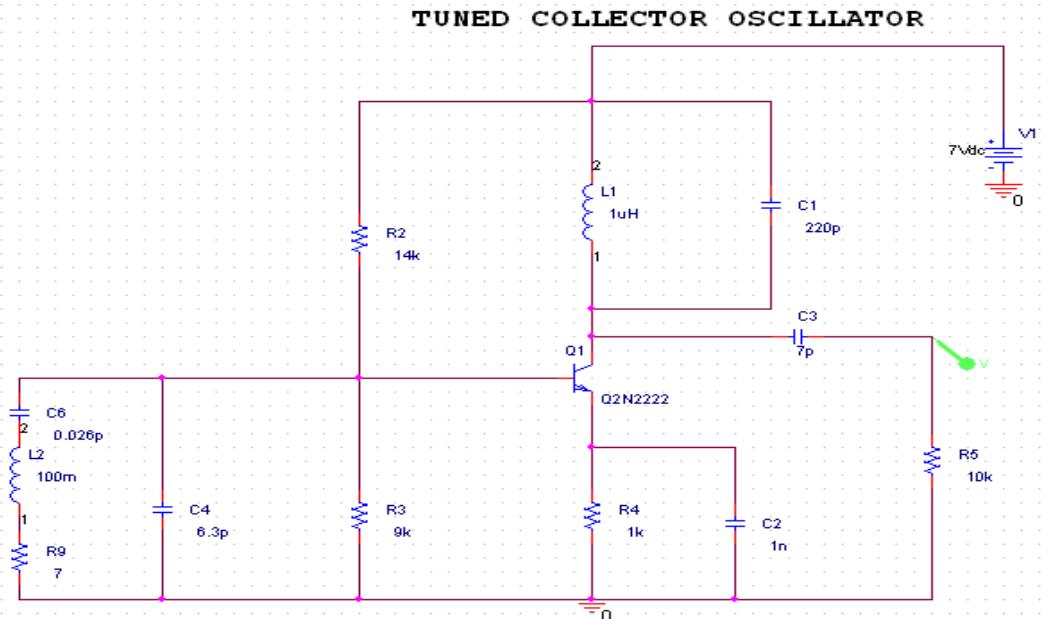

OUTPUTWAVEFORM:

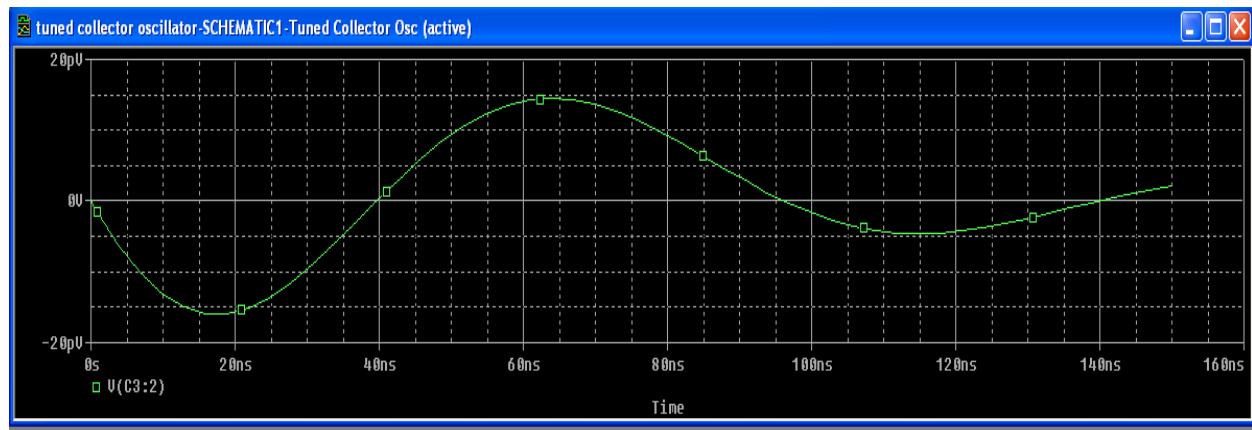

RESULT:

Ex.No:2	TWIN-TOSCILLATOR/WEINBRIDGEOSCILLATOR
Date:	

AIM

To construct and stimulate a Twin-Toscillator and Weinbridge oscillator using pspice.


SOFTWARE USED

ORCAD16.0


PROCEDURE

1. ORCAD-capture
2. Maximizes the session log.
3. In file, open a new project and give the name to the project and choose analog or mixed A/B and specify the location say D:/ECEII
4. Create a blank project.
5. Click inside the window once and the tool bar appears.
6. Choose place part-add library - select a component in the library and select all the components - click open to add all the components.
7. Choose the components from the library and place in the worksheet.
8. Give connection using wire and properly ground the circuit.
9. Save the project and simulate it.
10. Place the marker at the points wherever the waveforms are to be reviewed.
11. Click the option RUN and the output will be displayed.
12. If there are errors, correct and simulate it.
13. To view the waveform separately in plot-add plot to window-cut and paste the required waveforms.
14. The required input and output waveforms are taken printout.


CIRCUITDIAGRAM:

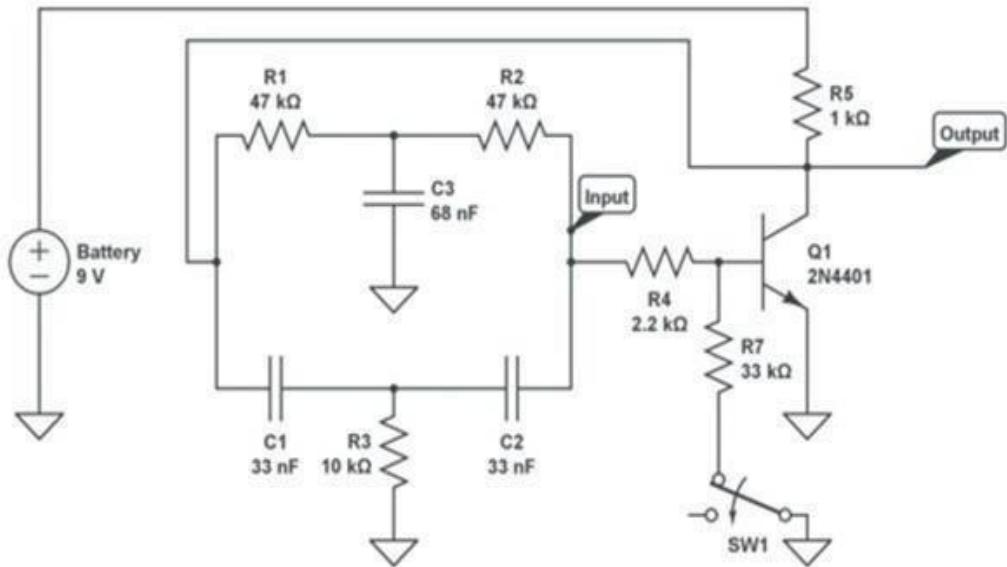


MODELGRAPH:

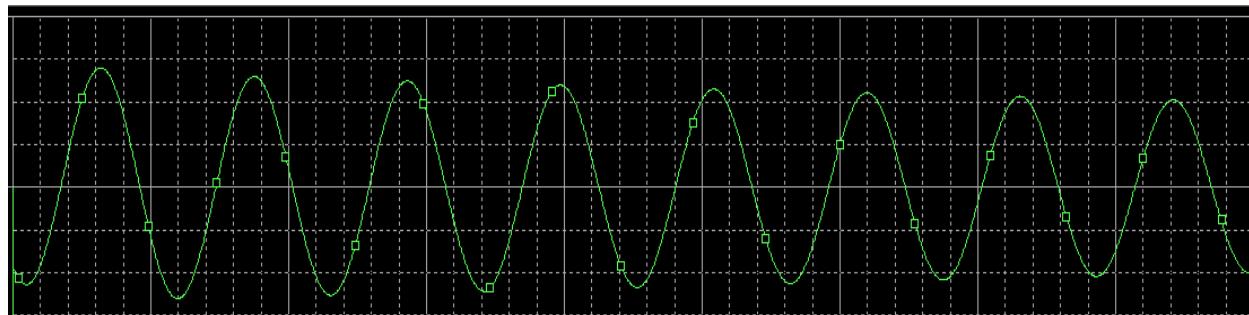

CIRCUITDIAGRAM:

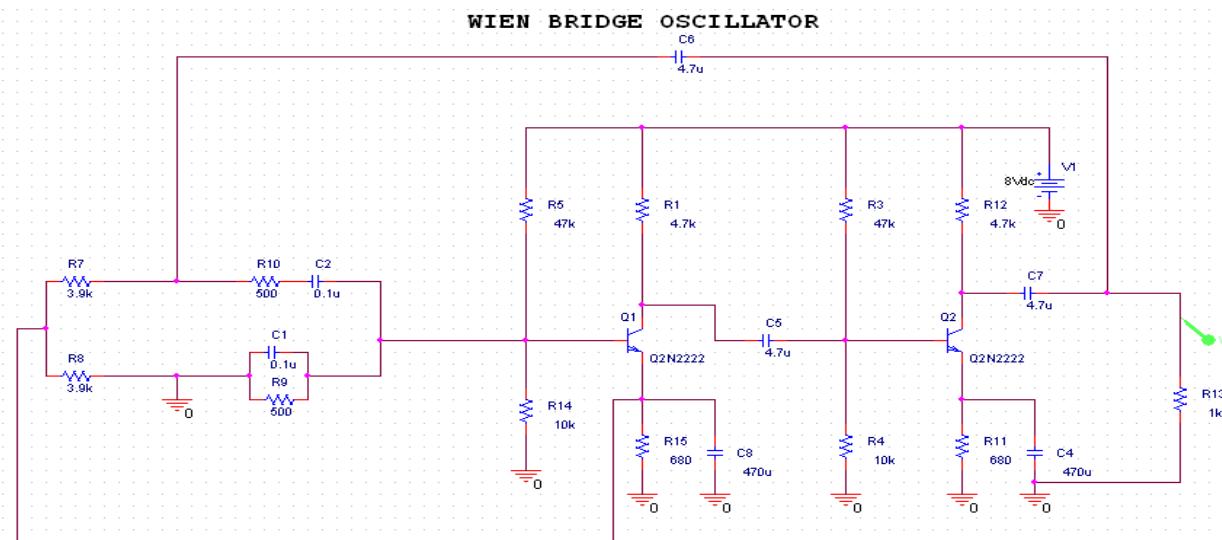

MODELGRAPH:

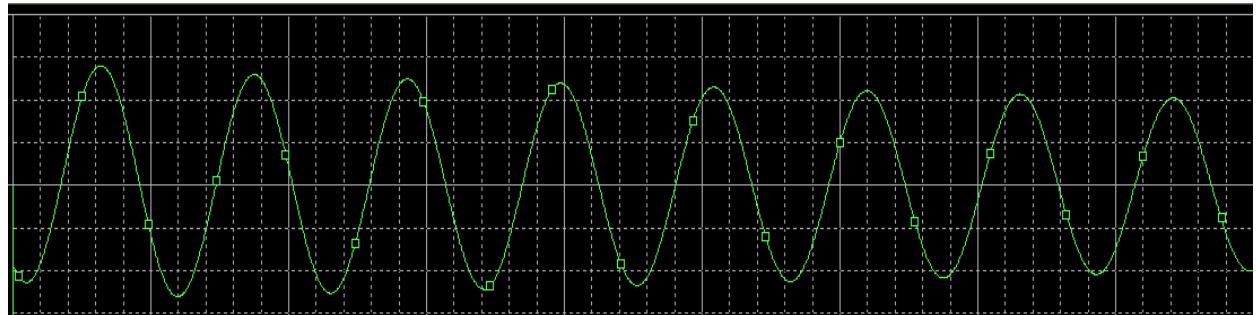

RESULT:

Ex.No:3	DOUBLE AND STAGGER TUNED AMPLIFIERS
Date:	

AIM

To construct and simulate a Double and Stagger tuned amplifiers using pspice.


SOFTWARE USED

ORCAD 16.0


PROCEDURE:

1. ORCAD-capture
2. Maximizes the session log.
3. In file, open a new project and give the name to the project and choose analog or mixed A/B and specify the location say D:/ECEII
4. Create a blank project.
5. Click inside the window once and the tool bar appears.
6. Choose place part-add library- select a component in the library and select all the components - click open to add all the components.
7. Choose the components from the library and place in the worksheet.
8. Give connection using wire and properly ground the circuit.
9. Save the project and simulate it.
10. Place the marker at the points wherever the waveforms are to be reviewed.
11. Click the option RUN and the output will be displayed.
12. If there are errors, correct and simulate it.
13. To view the waveform separately in plot-add plot to window-cut and paste the required waveforms.
14. The required input and output waveforms are taken printout.

DOUBLE TUNED AMPLIFIER

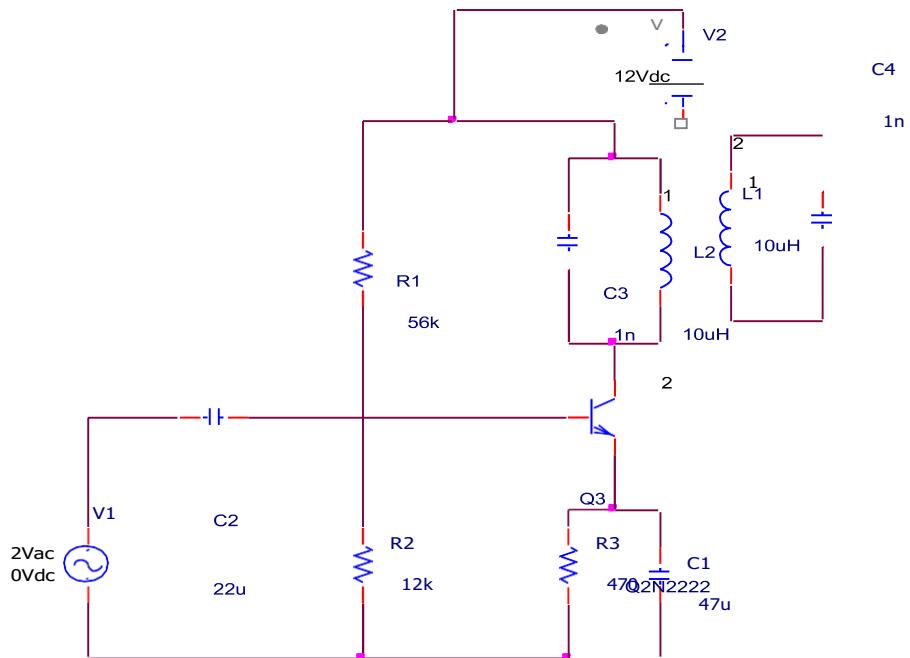


OUTPUT WAVEFORM

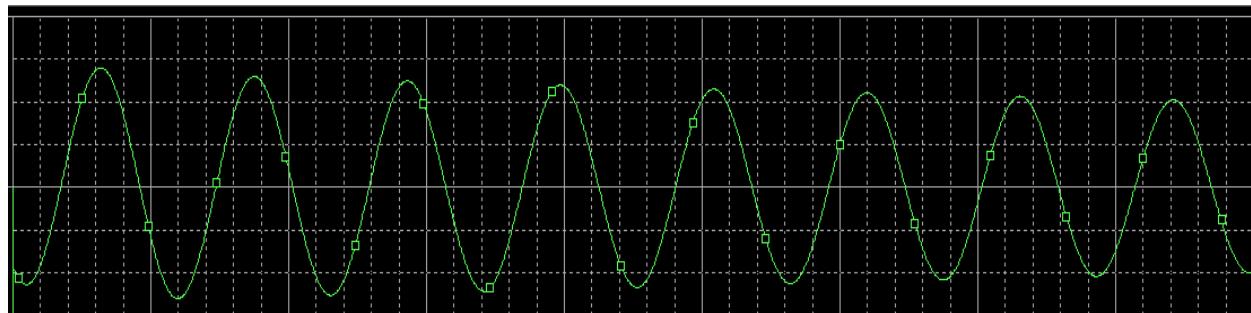


CIRCUITDIAGRAM:

STAGGER TUNED AMPLIFIER

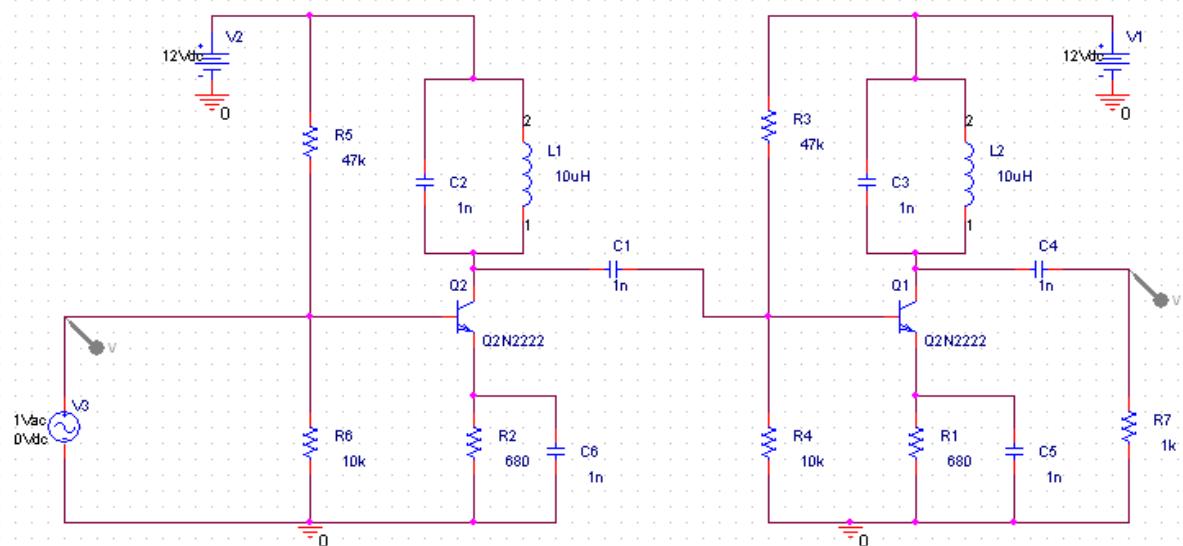

OUTPUTWAVEFORM:

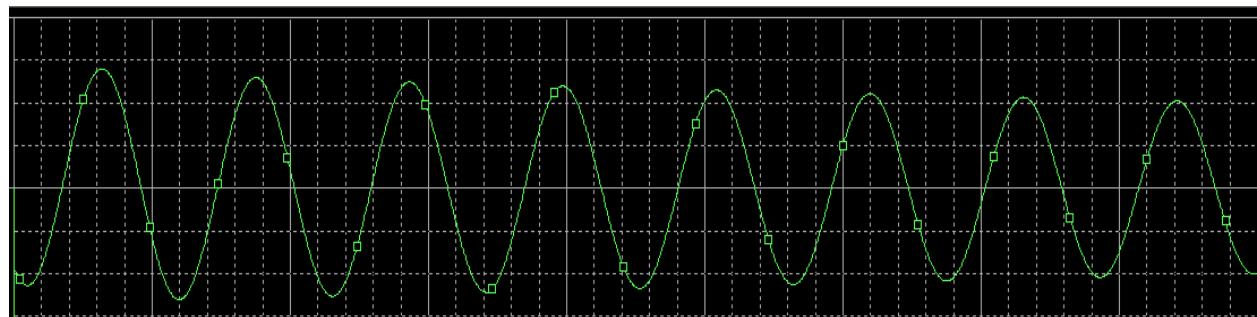

RESULT:

Ex.No:4	BISTABLEMULTIVIBRATOR
Date:	

AIM

To construct and simulate the Bistable multivibrator by using pspice.


SOFTWARE USED

ORCAD16.0


PROCEDURE

1. ORCAD-capture
2. Maximizes the session log.
3. In file, open a new project and give the name to the project and choose analog or mixed A/B and specify the location say D:/ECEII
4. Create a blank project.
5. Click inside the window once and the tool bar appears.
6. Choose place part-add library- select a component in the library and select all the components - click open to add all the components.
7. Choose the components from the library and place in the worksheet.
8. Give connection using wire and properly ground the circuit.
9. Save the project and simulate it.
10. Place the marker at the points wherever the waveforms are to be reviewed.
11. Click the option RUN and the output will be displayed.
12. If there are errors, correct and simulate it.
13. To view the waveform separately in plot-add plot to window-cut and paste the required waveforms.
14. The required input and output waveforms are taken printout.

CIRCUITDIAGRAM:

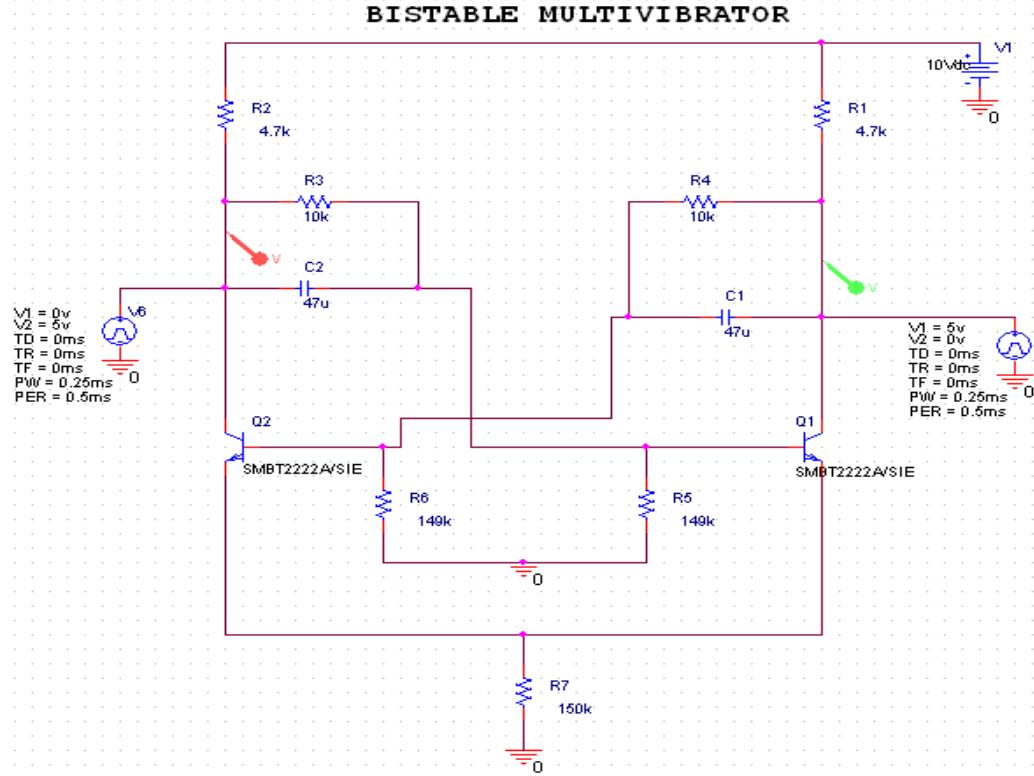

OUTPUTWAVEFORM:

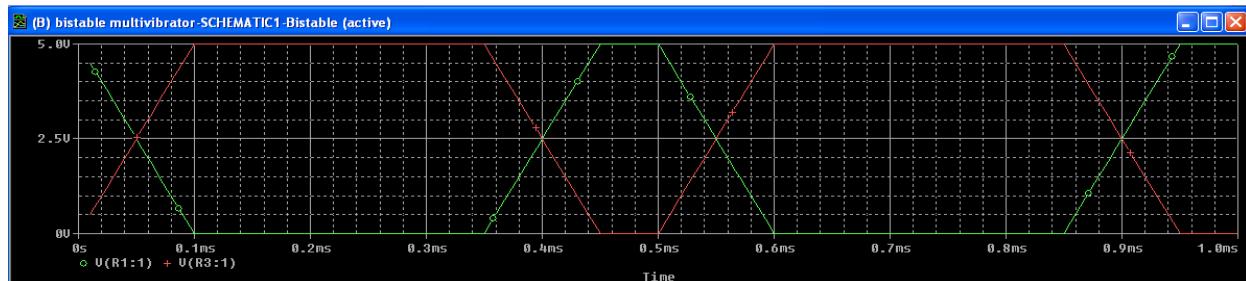

RESULT:

Ex.No:5	SCHMITTTRIGGERCIRCUITWITHPREDICTABLEH YSTERESIS
Date:	

AIM

To construct and simulate Schmitt trigger circuit by using pspice.


SOFTWARE USED

ORCAD16.0


PROCEDURE

1. ORCAD-capture
2. Maximizes the session log.
3. In file, open a new project and give the name to the project and choose analog or mixed A/B and specify the location say D:/ECEII
4. Create a blank project.
5. Click inside the window once and the tool bar appears.
6. Choose place part-add library-select a component in the library and select all the components -click open to add all the components.
7. Choose the components from the library and place in the worksheet.
8. Give connection using wire and properly ground the circuit.
9. Save the project and simulate it.
10. Place the marker at the points wherever the waveforms are to be reviewed.
11. Click the option RUN and the output will be displayed.
12. If there are errors, correct and simulate it.
13. To view the waveform separately in plot-add plot to window-cut and paste the required waveforms.
14. The required input and output waveforms are taken printout.

CIRCUITDIAGRAM

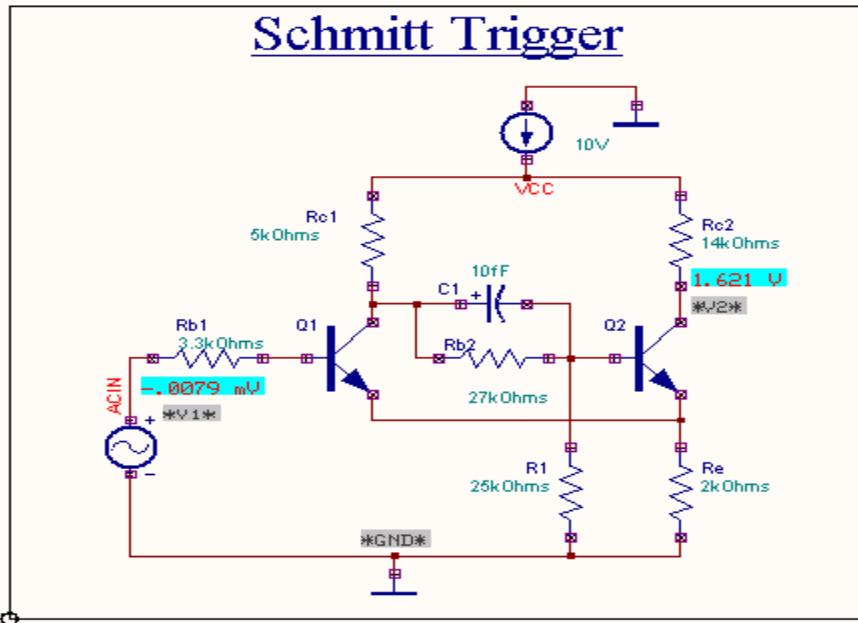

OUTPUTWAVEFORM

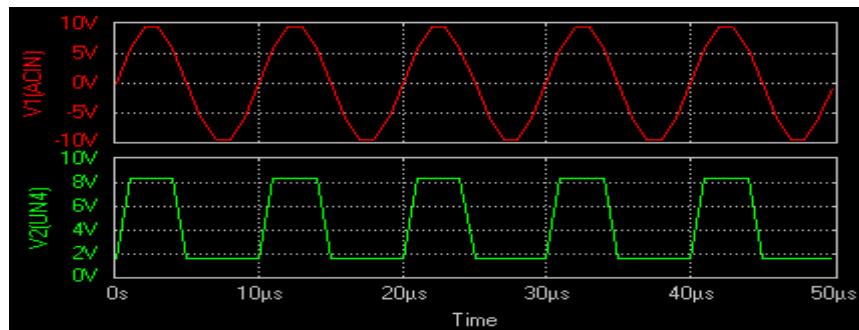

RESULT:

Ex.No:6	
Date:	

ANALYSIS OF POWER AMPLIFIERS

AIM

To construct and simulate power amplifier circuit by using pspice.


SOFTWARE USED

ORCAD 16.0

PROCEDURE

1. ORCAD-capture
2. Maximizes the session log.
3. In file, open a new project and give the name to the project and choose analog or mixed A/B and specify the location say D:/ECEII
4. Create a blank project.
5. Click inside the window once and the tool bar appears.
6. Choose place part-add library-select a component in the library and select all the components -click open to add all the components.
7. Choose the components from the library and place in the worksheet.
8. Give connection using wire and properly ground the circuit.
9. Save the project and simulate it.
10. Place the marker at the points wherever the waveforms are to be reviewed.
11. Click the option RUN and the output will be displayed.
12. If there are errors, correct and simulate it.
13. To view the waveform separately in plot-add plot to window-cut and paste the required waveforms.
14. The required input and output waveforms are taken printout.

CIRCUITDIAGRAM

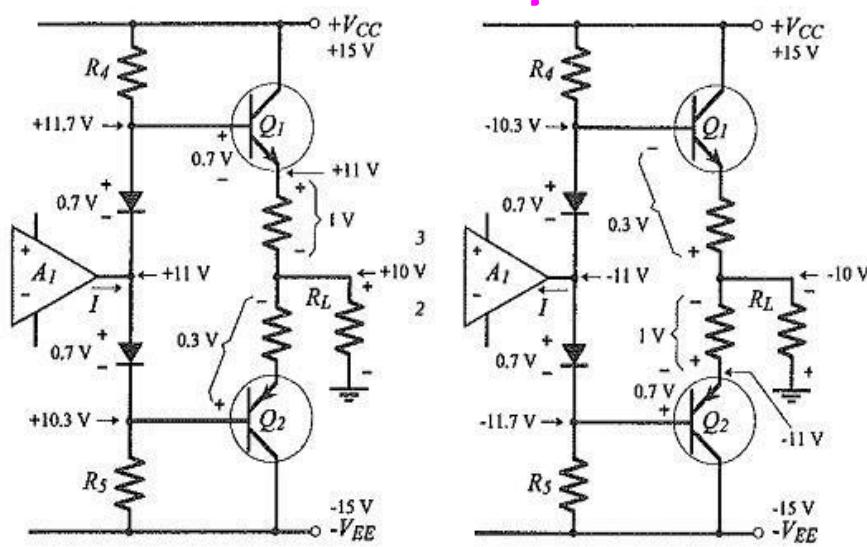


(a) Voltage levels when $V_o = +10\text{ V}$

(b) Voltage levels when $V_o = -10\text{ V}$

Figure 18-40
Output stage voltage levels for peak output voltages of $\pm 10\text{ V}$.

OUTPUTWAVEFORM

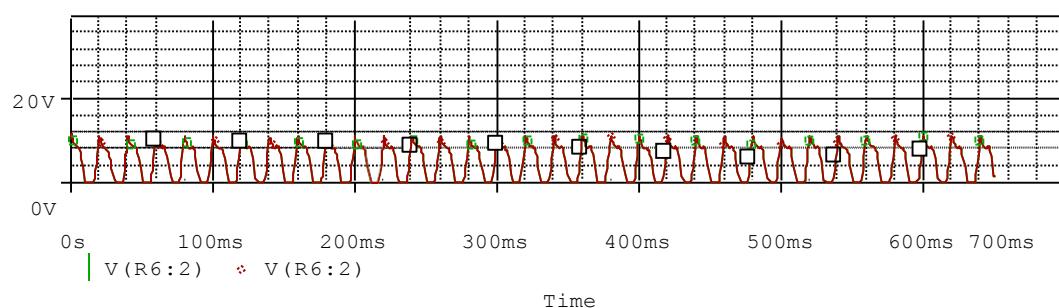

RESULT:

