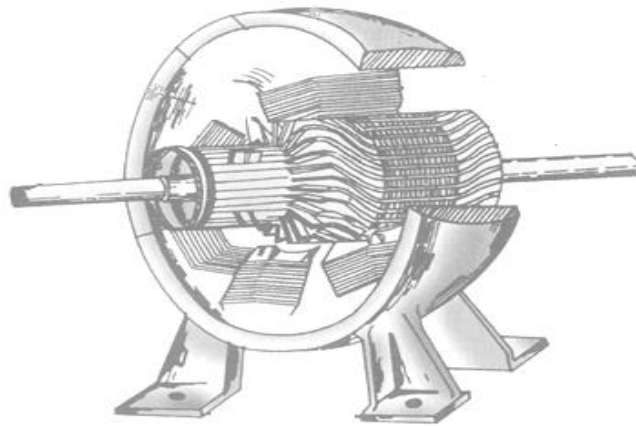




**MAHA BARATHI ENGINEERING  
COLLEGE, CHINNASALEM**  
**DEPARTMENT OF EEE**



**Electrical machines - I**  
**Lab manual**

1. Open circuit and load characteristics of separately and self excited DC shunt generators.
2. Load characteristics of DC compound generator with differential and cumulative connection.
3. Load characteristics of DC shunt and compound Motor.
4. Load characteristics of DC series motor.
5. Swinburne's test and speed control of DC shunt motor.
6. Hopkinson's test on DC motor - generator set.
7. Load test on single-phase transformer and three phase transformer connections.
8. Open circuit and short circuit tests on single phase transformer.
9. Sumner's test on transformers.
10. Separation of no-load losses in single phase transformer.
11. Study of starters and three phase transformer connections.


**T  
O  
T  
A  
L  
:**

# EE6411-Electrical machines - I

## LIST OF EXPERIMENTS

S.NO	DATE	TITLE	PAGE NO	MARKS
1		(a) OPEN CIRCUIT AND LOAD CHARACTERISTICS OF SEPARATELY EXCITED D.C SHUNT GENERATOR (b) OPEN CIRCUIT AND LOAD CHARACTERISTICS OF SELF EXCITED D.C SHUNT GENERATOR		
2		LOAD CHARACTERISTICS OF DC COMPOUND GENERATOR WITH DIFFERENTIAL AND CUMULATIVE CONNECTION		
3		(a) LOAD CHARACTERISTICS OF DC SHUNT MOTOR (b) LOAD CHARACTERISTICS OF DC COMPOUND MOTOR.		
4		LOAD CHARACTERISTICS OF DC SERIES MOTOR.		
5		(i) SPEED CONTROL OF D.C. SHUNT MOTOR (ii) SWINBURNE'S TEST		
6		HOPKINSON'S TEST ON DC MOTOR - GENERATOR SET.		
7		(i) LOAD TEST ON SINGLE-PHASE TRANSFORMER (ii) STUDY OF THREE PHASE TRANSFORMER CONNECTIONS.		
8		OPEN CIRCUIT AND SHORT CIRCUIT TESTS ON SINGLE PHASE TRANSFORMER.		
9		SUMPNER'S TEST ON TRANSFORMERS.		
10		SEPARATION OF NO-LOAD LOSSES IN SINGLE PHASE TRANSFORMER.		

**CIRCUIT DIAGRAM FOR OC TEST:**

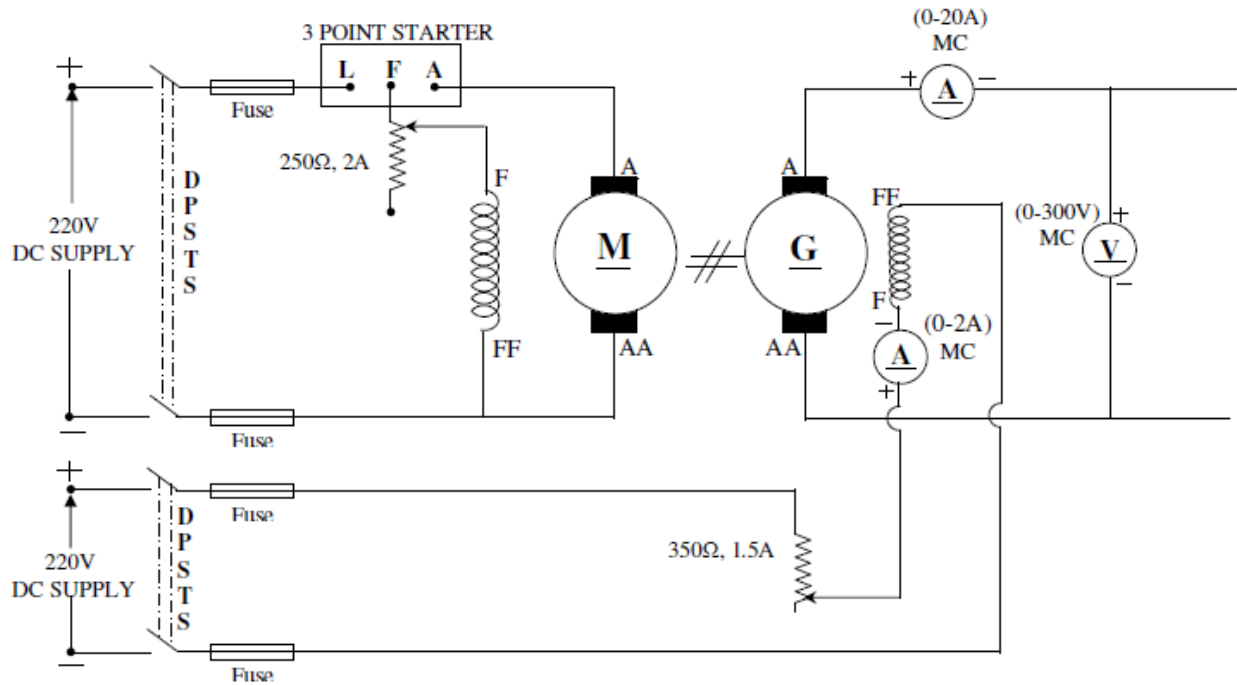

**TABULATION:**

S.No	$I_f$ (in Amps)	$E_g$ (in volts)

EXP NO :1(a)

DATE:

**OPEN CIRCUIT AND LOAD CHARACTERISTICS OF D.C  
SEPERATELY EXCITED SHUNT GENERATOR**

**AIM:**

To conduct open circuit and load test on a given separately excited D.C shunt generator and to obtain the characteristics.

**APPARATUS REQUIRED:**

Sl.No	Name of the apparatus	Type	Range	Quantity
1	Voltmeter	(0-300) V	M.C	1
2	Ammeter	(0-10) A (0-2) A	M.C M.C	1 1
3	Tachometer		Analog	1
4	Rheostat	230 ohm,1.7A	Wire wound	2
5	single phase Resistive load	5kw	---	1
6	Connecting wires	--	---	As required

**PROCEDURE:**


Open circuit test :

- 1) To give the connection as per the circuit diagram.
- 2) Switch on the MCB.
- 3) To start the motor by using 3-point starter.
- 4) Then set the motor (prime mover) speed is equal to synchronous speed by adjusting the motor field rheostat.
- 5) To kept open position in generator side DPSTS.
- 6) Note down the voltmeter reading at  $I_f$  is zero.
- 7) Then apply the field current and adjust the generator field rheostat in step by step also note down the ammeter and voltmeter reading in each step.
- 8) Then switched off the prime mover by using MCB.

Load test :

- 1) To give the connection as per the circuit diagram.
- 2) Switch on the MCB.
- 3) To start the motor (prime mover) by using 3-point starter.
- 4) Then set the motor (prime mover) speed is equal to synchronous speed by adjusting the motor field rheostat.

**CIRCUIT DIAGRAM FOR LOAD TEST:**

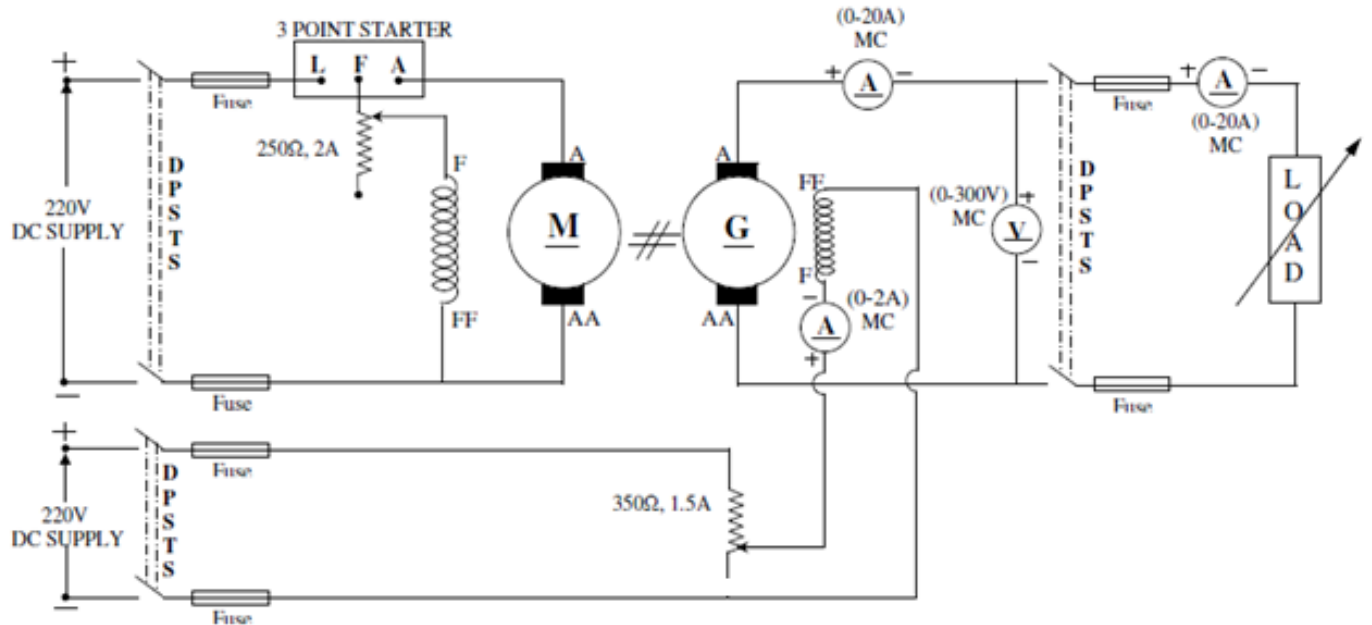

**TABULATION:**

Armature resistance  $R_a =$

S.NO	Load Voltage ( $V_L$ )	Field Current ( $I_f$ )	Load Current ( $I_L$ )	$I_a = I_L$	$E_g = V_L + I_a R_a$

- 5) Set the terminal voltage in generator side in rated by adjusting the generator field rheostat.
- 6) Switch on the generator side DPSTS.
- 7) Then apply the load in step by step also note down the ammeter and voltmeter reading in each step.
- 8) Then switched off the prime mover by using MCB.

**FORMULA USED:**

Open circuit test:

$$\text{Field resistance } R_F = \Delta_{E1} / I_{F1} = E_1 - E_o / I_{F1}$$

$$\text{Critical field resistance } R_c = \Delta_{E2} / I_{F2}$$

Load Test:

$$I_a = I_L \quad E_g = V_L + I_a R_a$$

## MODEL GRAPH:


### Open circuit test

- Field current Vs Open circuit voltage (If Vs Eg)


### Load test:

- Armature current Vs Generated voltage (Internal Characteristics) ( $I_a$  Vs  $E_g$ )
- Load current Vs Load voltage (External Characteristics) ( $I_L$  Vs  $V_L$ )

### **Open circuit test:**

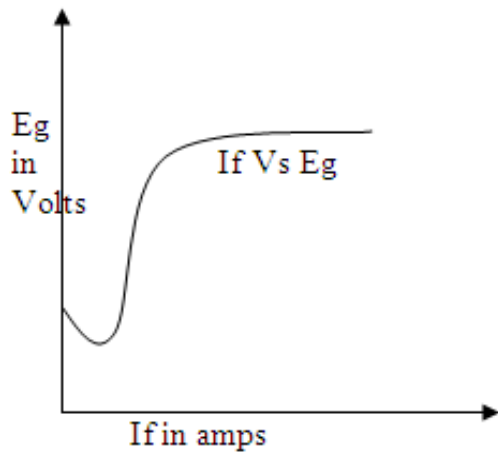


### **Load test:**

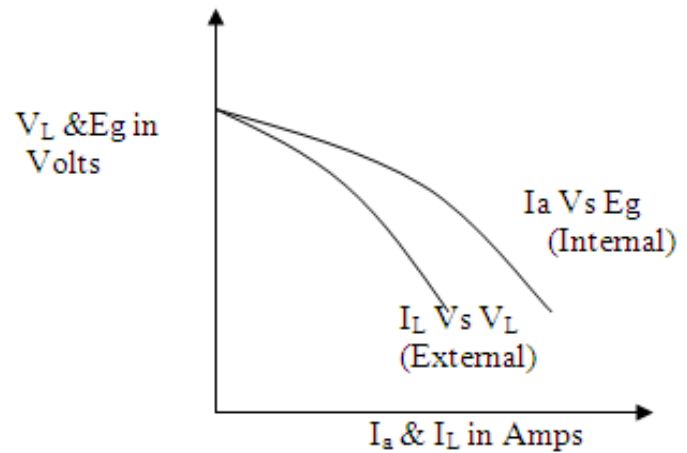



**RESULT:**

**CIRCUIT DIAGRAM FOR OC TEST:**

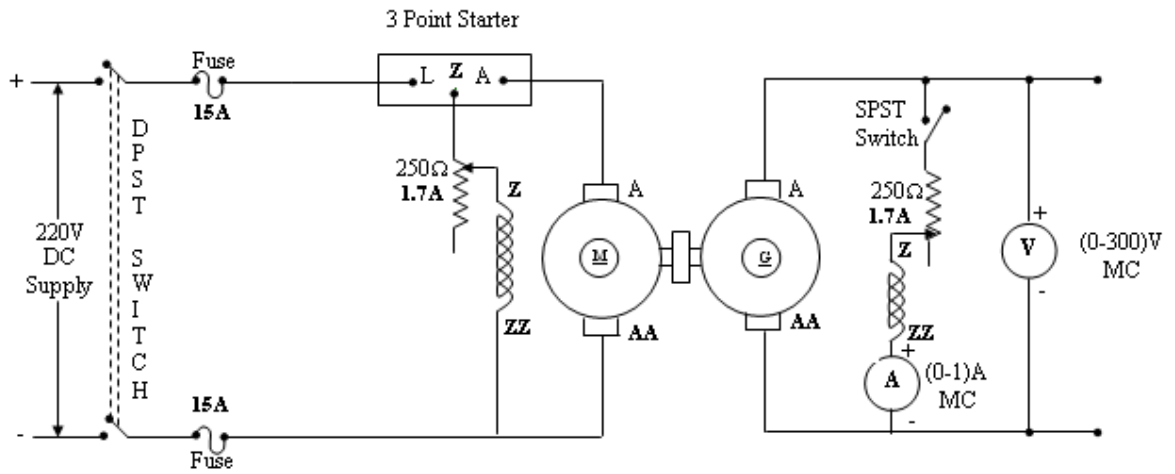

**FUSE RATING:**

125% of rated current

**NAME PLATE DETAILS:**

	<b><u>Motor</u></b>	<b><u>Generator</u></b>
Rated Voltage :	220V	220V
Rated Current :		
Rated Power :		
Rated Speed :	1500 RPM	1500 RPM

**TABULAR COLUMN:**

**OPEN CIRCUIT TEST:**

S.No	If (in Amps)	Eg (in volts)

EXP NO :1(b)

DATE:

**OPEN CIRCUIT AND LOAD CHARACTERISTICS OF  
D.C SELF EXCITED SHUNT GENERATOR**

**AIM:**

To conduct open circuit and load test on self-excited D.C shunt generator and to obtain the characteristics.

**APPARATUS REQUIRED:**

Sl.No	Name of the apparatus	Range	Type	Quantity
1	Voltmeter	(0-300) V	M.C	1
2	Ammeter	(0-10) A	M.C	1
		(0-2) A	M.C	1
3	Tachometer		Analog	1
4	Rheostat	230 ohm,1.7A	Wire wound	2
5	Single phase Resistive load	5kw	---	1
6	Connecting wires	--	---	As required

**PROCEDURE:**


Open circuit test :

- 1) To give the connection as per the circuit diagram.
- 2) Switch on the MCB.
- 3) To start the motor by using 3-point starter.
- 4) Then set the motor (prime mover) speed is equal to synchronous speed by adjusting the motor field rheostat.
- 5) To kept open position in generator side DPSTS.
- 6) Note down the voltmeter reading at  $I_f$  is zero.
- 7) Then apply the field current and adjust the generator field rheostat in step by step also note down the ammeter and voltmeter reading in each step.
- 8) Then switched off the prime mover by using MCB.

Load test :

- 1) To give the connection as per the circuit diagram.
- 2) Switch on the MCB.
- 3) To start the motor (prime mover) by using 3-point starter.
- 4) Then set the motor (prime mover) speed is equal to synchronous speed by adjusting the motor field rheostat.
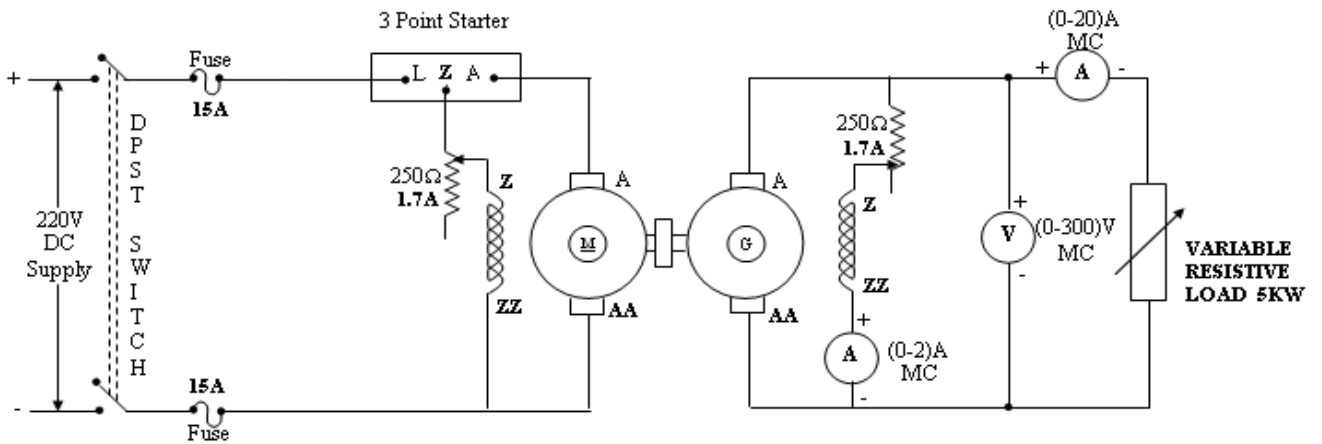
## CHARACTERISTICS OF DC SELF EXCITED GENERATOR



### LOAD TEST

Armature resistance  $R_a =$

S.NO	Load Voltage ( $V_L$ )	Field Current ( $I_f$ )	Load Current ( $I_L$ )	$I_a = I_L + I_f$	$E_g = V_L + I_a R_a$

- 5) Set the terminal voltage in generator side in rated by adjusting the generator field rheostat.
- 6) Switch on the generator side DPSTS.
- 7) Then apply the load in step by step also note down the ammeter and voltmeter reading in each step.
- 8) Then switched off the prime mover by using MCB.

**FORMULA USED:**

Open circuit test:

$$\text{Field resistance } R_F = \Delta_{E1} / I_{F1} = E_1 - E_o / I_{F1}$$

$$\text{Critical field resistance } R_c = \Delta_{E2} / I_{F2}$$

Load test:

$$I_a = I_L + I_f \quad E_g = V_L + I_a R_a$$

## MODEL GRAPH:


### Open circuit test

- Field current Vs Open circuit voltage (If Vs Eg)


### Load test:

- Armature current Vs Generated voltage (Internal Characteristics) ( $I_a$  Vs  $E_g$ )
- Load current Vs Load voltage (External Characteristics) ( $I_L$  Vs  $V_L$ )

### **Open circuit test:**

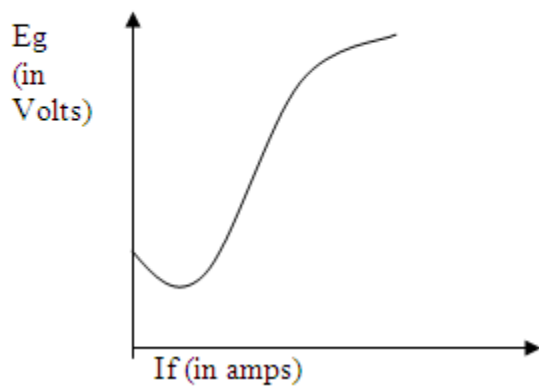


### **Load test:**

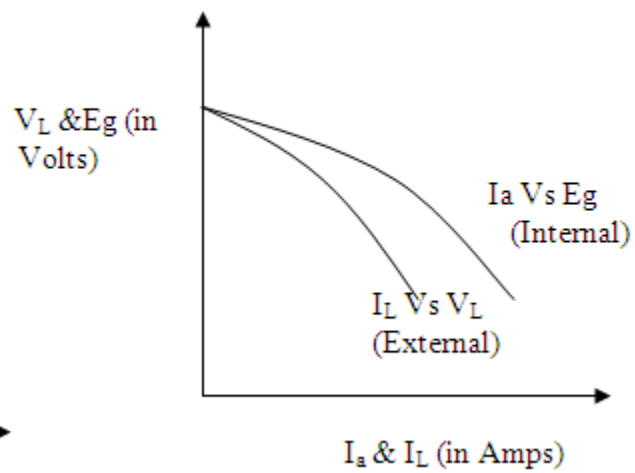

**RESULT:**

# CIRCUIT DIAGRAM

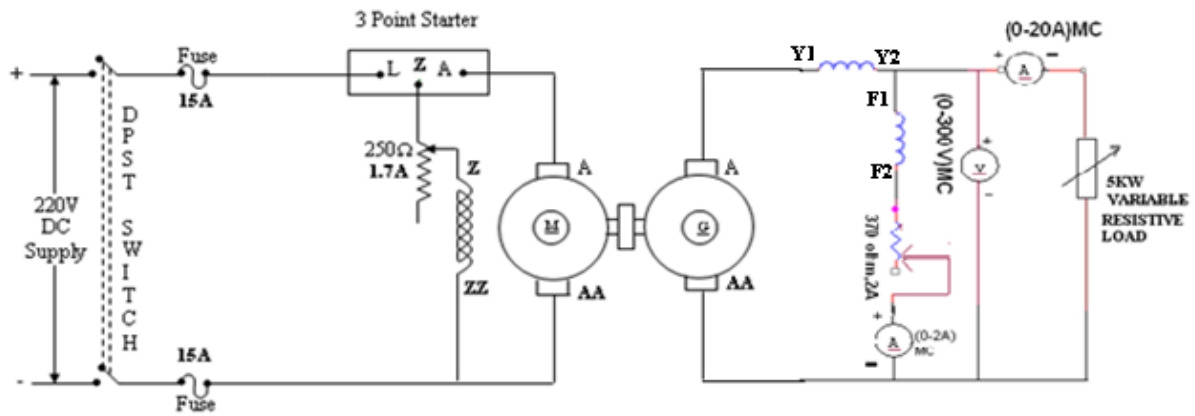

**FUSE RATING:**

125% of rated current

**NAME PLATE DETAILS:**

	<u>Motor</u>	<u>Generator</u>
Rated Voltage :	220V	220V
Rated Current :		
Rated Power :		
Rated Speed :	1500 RPM	1500 RPM


## LOAD TEST(cummulative)

Armature resistance  $R_a =$

Series Resistance ( $R_{se}$ ) =

S.NO	Load Voltage ( $V_L$ )	Field Current ( $I_f$ )	Load Current ( $I_L$ )	$I_a = I_L + I_f$	$E_g = V_L + I_a(R_a + R_{se})$

## MODEL GRAPH:

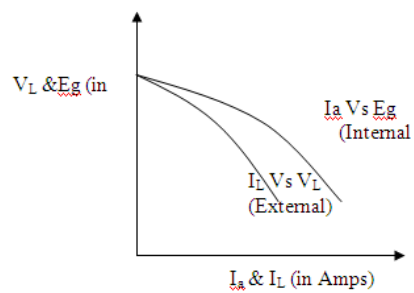



**EXP NO: 2**

**DATE:**

**LOAD CHARACTERISTICS ON DC COMPOUND GENERATOR**

**AIM:**

To perform load test on DC Compound generator and obtain characteristics curves.

**APPARATUS REQUIRED:**

Sl.No	Name of the apparatus	Type	Range	Quantity
1	Voltmeter	(0-300) V	M.C	1
2	Ammeter	(0-20) A	M.C	1
		(0-2) A	M.C	1
3	Tachometer		Analog	1
4	Rheostat	230 ohm, 1.7A	Wire wound	2
5	Single Phase Resistive load	5kw	---	1
6	Connecting wires	--	---	As required

**PROCEDURE:**

**Load test :**


- 1) To give the connection as per the circuit diagram.
- 2) Switch on the MCB.
- 3) To start the motor (prime mover) by using 3-point starter.
- 4) Then set the motor (prime mover) speed is equal to synchronous speed by adjusting the motor field rheostat
- 5) Set the terminal voltage in generator side in rated by adjusting the generator field rheostat.
- 6) Switch on the generator side DPSTS.
  
- 7) Then apply the load in step by step also note down the ammeter and voltmeter reading in each step.
- 8) Then switched off the prime mover by using MCB.

**FORMULA USED:**

$$I_a = I_L + I_f$$

$$E_g = V_L + I_a [R_a + R_{se}]$$

# CIRCUIT DIAGRAM

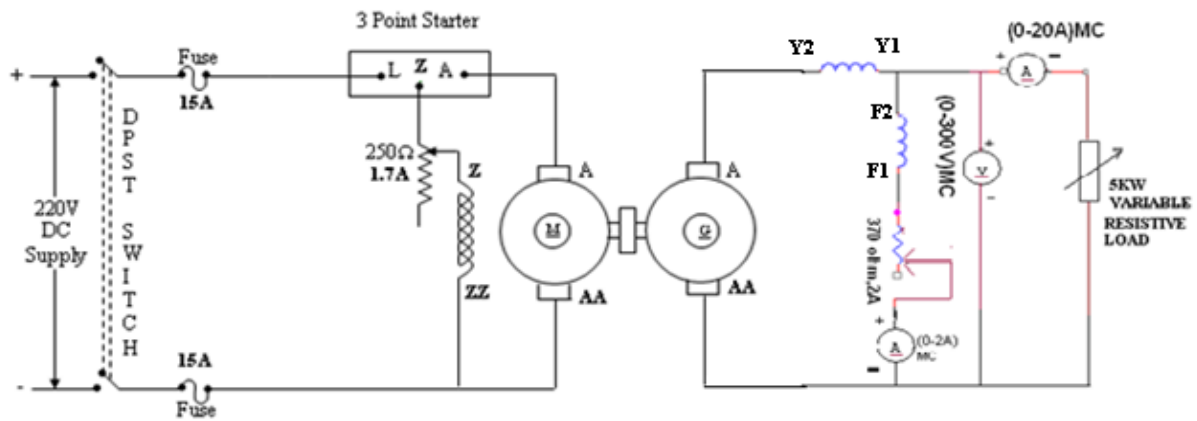

**FUSE RATING:**

125% of rated current

**NAME PLATE DETAILS:**

	<u>Motor</u>	<u>Generator</u>
Rated Voltage :	220V	220V
Rated Current :		
Rated Power :		
Rated Speed :	1500 RPM	1500 RPM

## LOAD TEST(differential)

Armature resistance  $R_a =$


Series Resistance ( $R_{se}$ ) =

S.NO	Load Voltage ( $V_L$ )	Field Current ( $I_f$ )	Load Current ( $I_L$ )	$I_a = I_L + I_f$	$E_g = V_L + I_a(R_a + R_{se})$

**MODEL CALCULATION:**

**RESULT:**

**CIRCUIT DIAGRAM:**

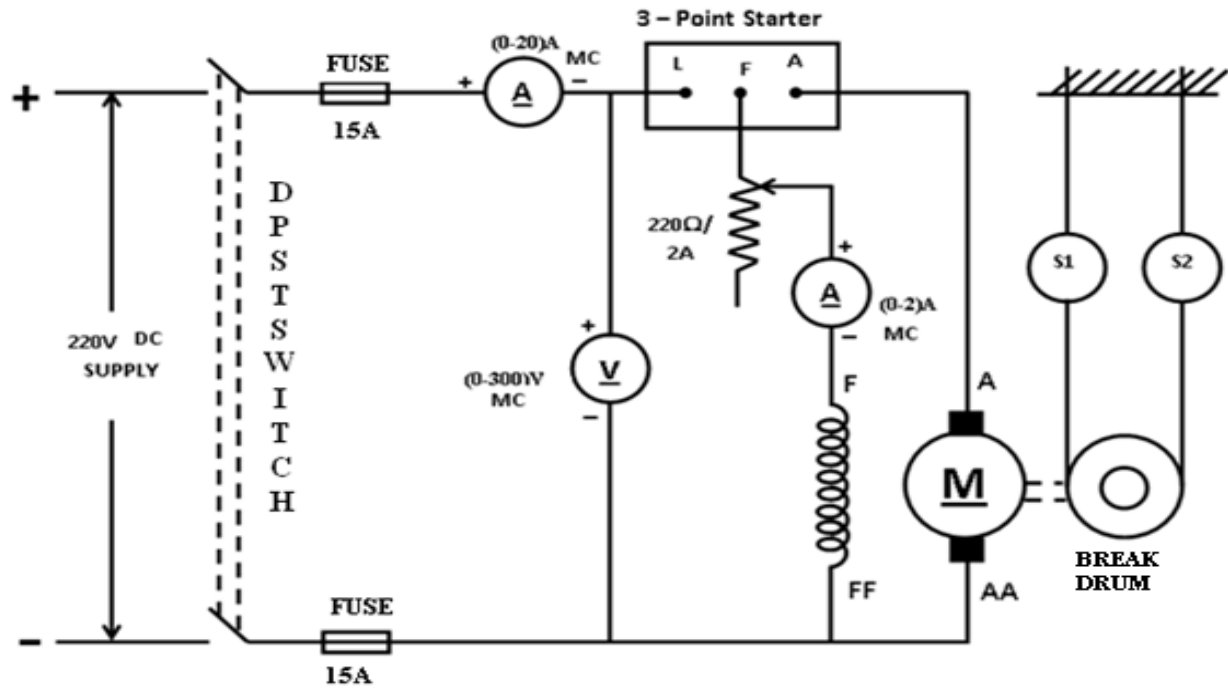

**FUSE RATING**

**NAME PLATE DETAILS**

**TABULAR COLUMN**

Sl. No.	Voltage, $V_L$ (V)	Current $I_L$ (A)	Spring balance		Speed Rpm	Torque N-m	Input $P_i$ watts	Output $P_o$ watts	Efficiency $In$ %
			$S_1$ Kg	$S_2$ Kg					

**EXP NO:3(a)**

**DATE :**

**LOAD TEST ON DC SHUNT MOTOR**

**AIM:**

To perform Load test on DC shunt motor and to draw the characteristics and performance curves.


**APPARATUS REQUIRED:**

Sl.No	Name of the apparatus	Range	Type	Quantity
1	Voltmeter	(0-300) V	M.C	1
2	Ammeter	(0-20) A	M.C	1
3	Tachometer		Analog	1
4	Rheostat	220 ohm,2A	Wire wound	1
5	Connecting wires	--	---	As required


**PROCEDURE:**

1. The Connections are made as per the circuit diagram.
2. The Field Rheostat is kept at minimum position.
3. The supply is given by closing DPSTS and by using 3- point starter motor is started.
4. The speed of the motor is adjusted to the rated value by varying field rheostat.

### Performance curves:

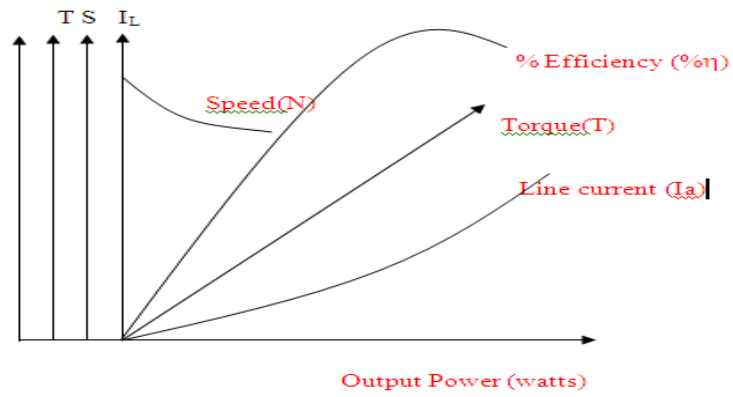

### Characteristics curves:

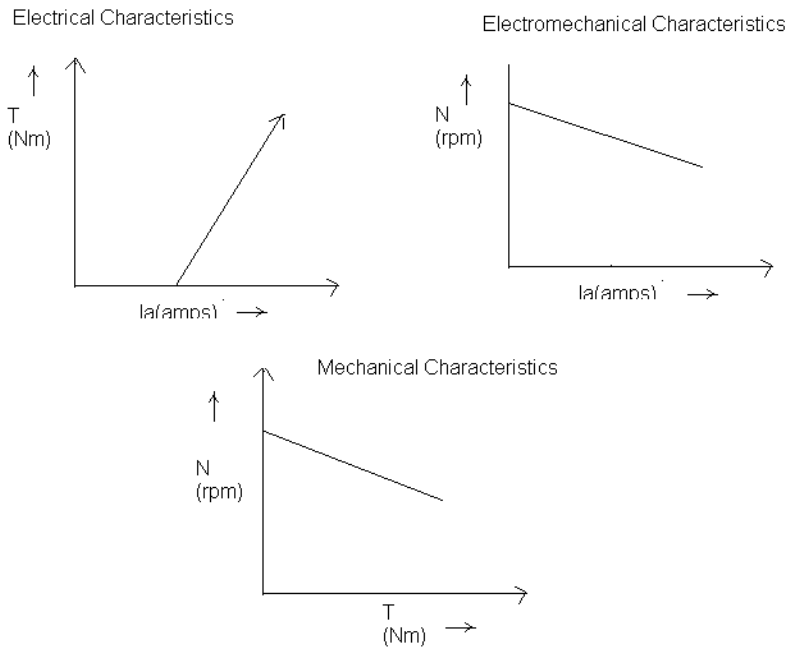

5. Now the load is applied on the brake drum and the corresponding ammeter and voltmeter readings are noted.
6. This procedure is repeated for different values of load up to the rated value of armature current.
7. Now the load is reduced and the supply is disconnected

**FORMULA USED:**

$$\text{Input Power } (P_i) = V_L I_L \text{ watts}$$

$$\text{Torque (T)} = (S_1 - S_2) \times R \times 9.81 \text{ N-m}$$

Where,

R- Radius of the brake drum in meter

$$\text{Output Power (Po)} = 2\pi NT/60 \text{ watts}$$


$$\% \text{ Efficiency} = \frac{\text{Output Power (Po)}}{\text{Input Power (Pi)}}$$

**SHUNT MOTOR CHARACTERISTICS**

- N Vs Ia
  - $N = k (V - I_a R_a) / \Phi$
  - Ish and  $\Phi$  are nearly constant
  - Speed nearly constant except Ia Ra drop.
- T Vs Ia
  - $T \propto I_a (\Phi = \text{constant})$
  - T ↑ ; Ia ↑
- N Vs T
  - Ia ↑ ; N ↓ ; T ↑

**RESULT:**

**CIRCUIT DIAGRAM:**

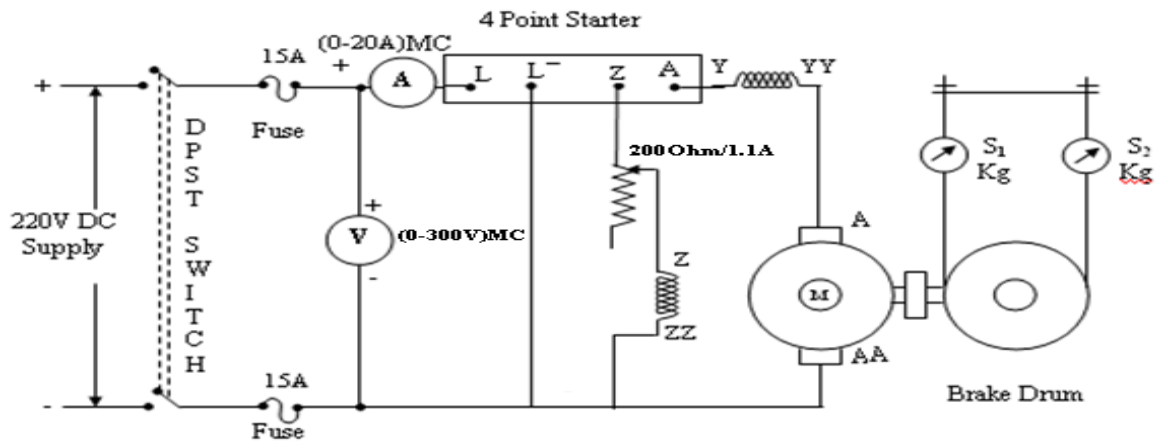

**FUSE RATING:**

**NAME PLATE DETAILS**

**TABULAR COLUMN:**

S.No	Voltage V (Volts)	Current I (Amps)	Spring Balance Reading		$(S_1 \sim S_2)$ Kg	Speed N (rpm)	Torque T (Nm)	Output Power P <sub>m</sub> (Watts)	Input Power P <sub>i</sub> (Watts)	Efficiency $\eta\%$
			S <sub>1</sub> (Kg)	S <sub>2</sub> (Kg)						



**EXP NO:** 3(b)

**DATE:**

**LOAD TEST ON DC COMPOUND MOTOR**

**AIM:**

To conduct load test on DC compound motor and to find its efficiency.


**APPARATUS REQUIRED:**

S.No.	Apparatus	Range	Type	Quantity
1	Ammeter	(0-20)A	MC	1
2	Voltmeter	(0-300)V	MC	1
3	Rheostat	200 $\Omega$ , 1.1A	Wire Wound	1
4	Tachometer	(0-1500) rpm	Digital	1
5	Connecting Wires	2.5sq.mm.	Copper	Few

**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. After checking the no load condition, and minimum field rheostat position, DPST switch is closed and starter resistance is gradually removed.
3. The motor is brought to its rated speed by adjusting the field rheostat.
4. Ammeter, Voltmeter readings, speed and spring balance readings are noted under no load condition.
5. The load is then added to the motor gradually and for each load, voltmeter, ammeter, spring balance readings and speed of the motor are noted.
6. The motor is then brought to no load condition and field rheostat to minimum position, then DPST switch is opened.

**MODEL GRAPH:**

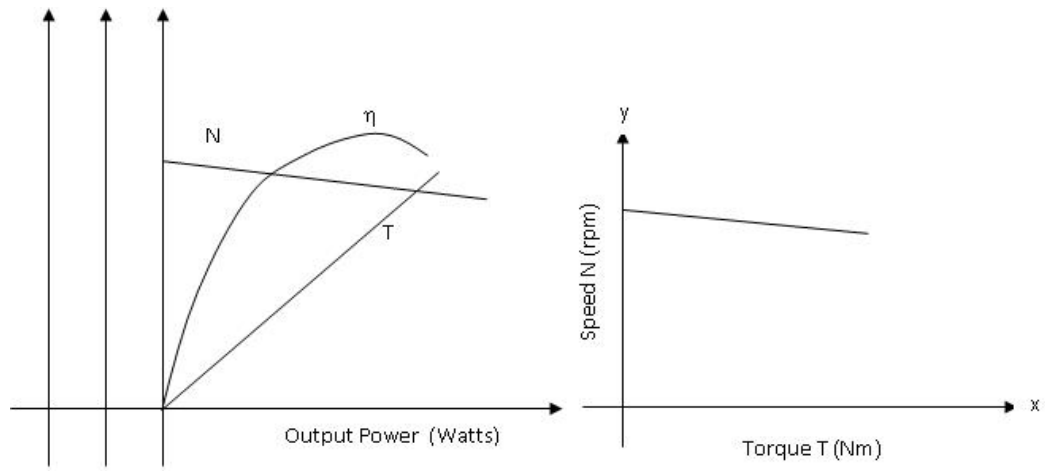

**MODEL CALCULATION:**

**FORMULA USED:**

Circumference of brake drum =  $2 \times \pi \times R$  in meter

R – Radius of the brake drum

Torque,  $T = (S_1 - S_2) \times 9.81 \times R$  in Nm

Input power,  $P_i = V_L \times I_L$  in Watts


Output power,  $P_m = (2 \times \pi \times N \times T) / 60$  in Watts

% Efficiency,  $\eta = (P_m / P_i) \times 100$

**RESULT:**

## LOAD TEST ON DC SERIES MOTOR

### CIRCUIT DIAGRAM:

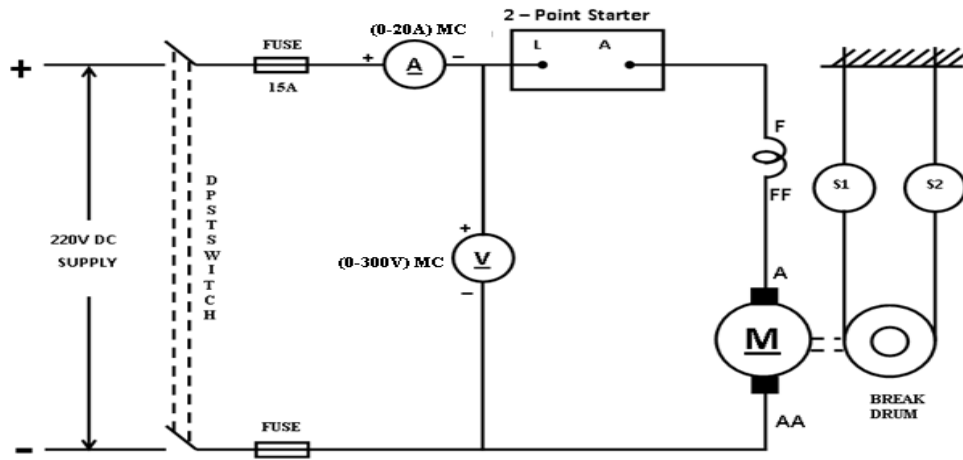

**FUSE RATING**

**NAME PLATE DETAILS**

### TABULAR COLUMN:

Sl. No.	Voltage, $V_L$ (V)	Current $I_L$ (A)	Spring balance		Speed Rpm	Torque N-m	Input $P_i$ watts	Output $P_o$ watts	Efficiency $I_n$ %
			$S_1$ Kg	$S_2$ Kg					

EXP NO: 4

DATE :

**LOAD TEST ON DC SERIES MOTOR**

**AIM:**

To perform Load test on DC Series motor and to draw the characteristics and performance curves.

**APPARATUS REQUIRED:**

Sl.No	Name of the apparatus	Range	Type	Quantity
1	Voltmeter	(0-300) V	M.C	1
2	Ammeter	(0-20) A	M.C	1
3	Tachometer		Analog	1
4	Connecting wires	--	---	As required

**FORMULA USED:**

Circumference of brake drum =  $2 \times \pi \times R$  in Meter

R – Radius of the brake drum


Torque,  $T = (S_1 - S_2) \times 9.81 \times R$  in Nm

Input power,  $P_i = V_L \times I_L$  in Watts

Output power,  $P_o = (2 \times \pi \times N \times T) / 60$  in Watts


% Efficiency,  $\eta = (P_o / P_i) \times 100$

### PERFORMANCE CURVES:

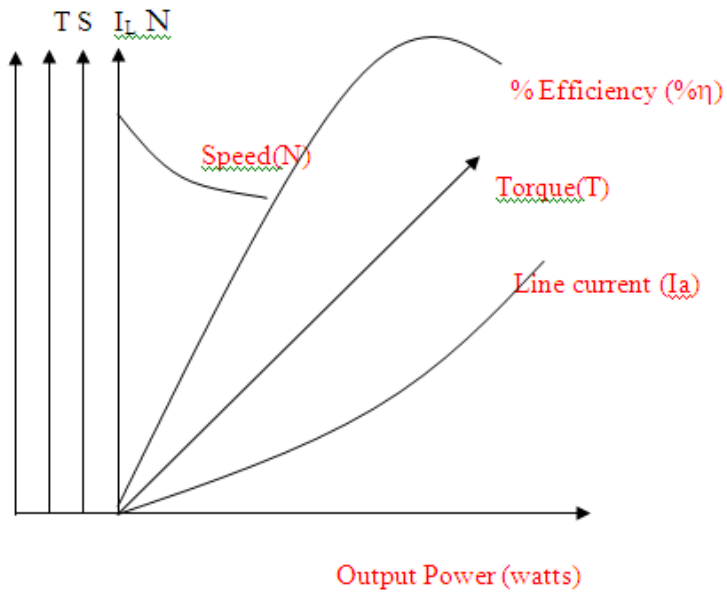


### CHARACTERISTICS CURVES:


Electrical Characteristics

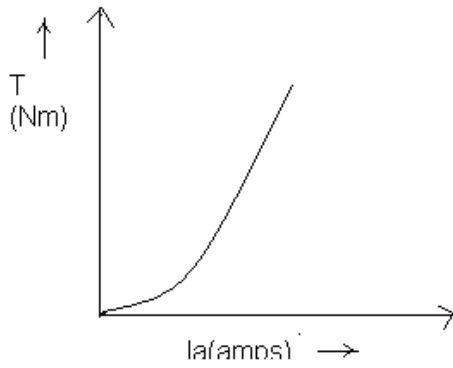

Electromechanical Characteristics

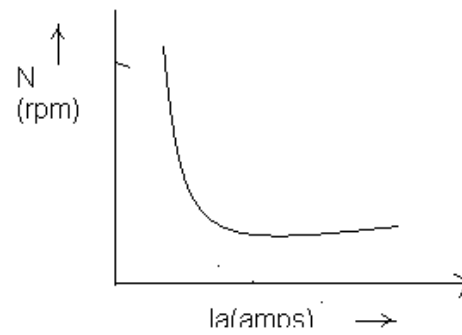

Mechanical Characteristics

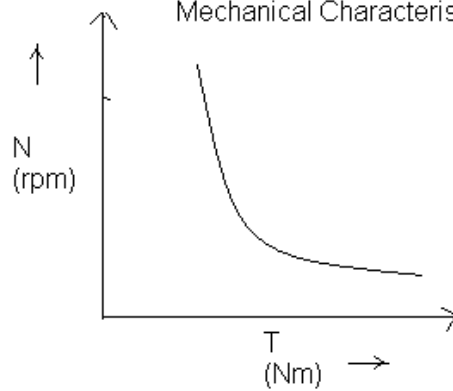


**MODEL CALCULATION:**

**RESULT:**

## SPEED CONTROL OF DC SHUNT MOTOR

### CIRCUIT DIAGRAM:

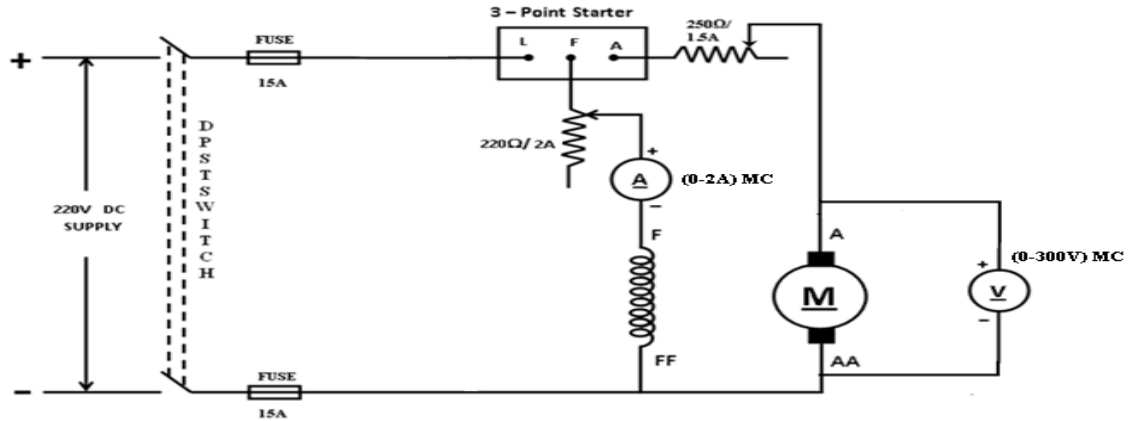

**FUSE RATING**

**NAME PLATE DETAILS**

### (i) Armature Voltage Control:

S.No.	$I_{f1} =$		$I_{f2} =$	
	Armature Voltage $V_a$ ( Volts)	Speed N (rpm)	Armature Voltage $V_a$ ( Volts)	Speed N (rpm)



**EXP NO:** 5(a)

**DATE:**

**SPEED CONTROL OF DC SHUNT MOTOR**

**AIM:**

To control the speed of the dc shunt motor by using armature control and field control method.

**APPARATUS REQUIRED:**

S.No.	Apparatus	Range	Type	Quantity
1	Ammeter	(0-20) A	MC	1
2	Voltmeter	(0-300) V	MC	1
3	Rheostats	250Ω, 1.5A	Wire Wound	Each 1
4	Tachometer	(0-3000) rpm	Digital	1
5	Connecting Wires	2.5sq.mm.	Copper	Few

**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. After checking the maximum position of armature rheostat and minimum position of field rheostat, DPST switch is closed

**(i) Armature Control:**

1. Field current is fixed to various values and for each fixed value, by varying the armature rheostat, speed is noted for various voltages across the armature.



**(ii) Field Control:**

1. Armature voltage is fixed to various values and for each fixed value, by adjusting the field rheostat, speed is noted for various field currents.
2. Bringing field rheostat to minimum position and armature rheostat to maximum position DPST switch is opened.

**Field Control:**

S.No.	$V_{a1} =$		$V_{a2} =$	
	Field Current $I_f$ (A)	Speed N (rpm)	Field Current $I_f$ (A)	Speed N (rpm)

**MODEL GRAPHS:**

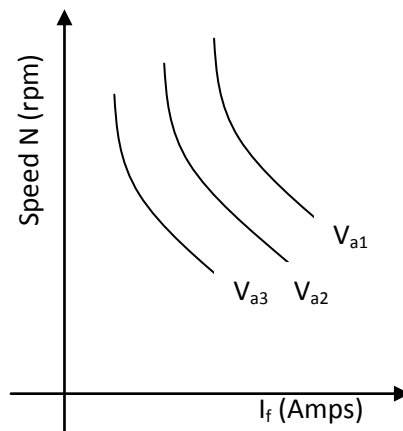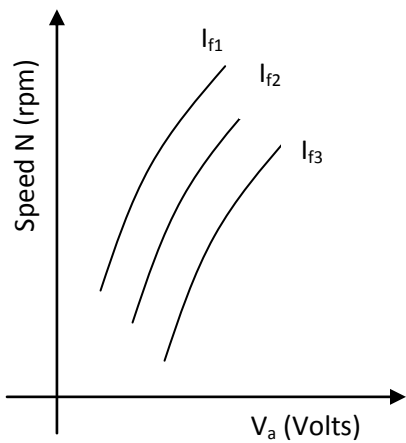


**MODEL CALCULATION:**

**RESULT:**

## SWINBURNE'S TEST OF D.C. SHUNT MOTOR

### CIRCUIT DIAGRAM: -

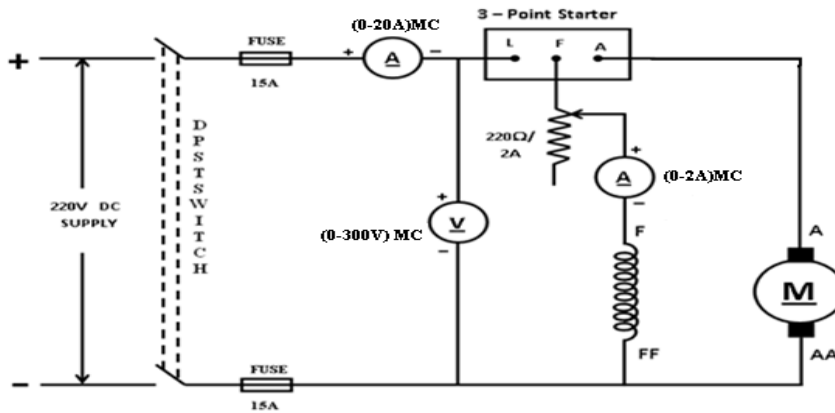

### NAME PLATE DETAILS

### TABULAR COLUMNS

#### (i) Motor on No Load

$V_o$	$I_o$	$I_f$	$I_a = I_o - I_f$	Speed (N)
Volts	Amps	Amps	Amps	RPM
				<b>1500</b>

EXP NO: 5(b)

DATE :

**SWINBURNE'S TEST OF D.C. SHUNT MOTOR**

**AIM:**

To perform Swinburne's test and to predetermine the efficiency of a given D.C. Shunt machine

**APPARATUS REQUIRED:**

S.No.	Apparatus	Range	Type	Quantity
1	Ammeter	(0-20) A	MC	1
2	Voltmeter	(0-300) V	MC	1
3	Rheostats	250Ω, 1.5A	Wire Wound	Each 1
4	Tachometer	(0-3000) rpm	Digital	1
5	Connecting Wires	2.5sq.mm.	Copper	Few

**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. The supply is switched ON by closing the DPST switch.
3. The field rheostat is adjusted till the motor attains its rated speed.
4. The readings of the ammeters and voltmeter are noted under no load conditions.
5. The rheostat is brought back to the minimum position and the supply is switched OFF.
6. The DC resistance of the armature is determined using a voltmeter and an ammeter.

**PREDETERMINATION OF LOSSES AND EFFICEINCY AT DIFFERENT LOADS:**

(i) As a Motor:

<b>SL. NO</b>	<b>Load Voltage <math>V_L</math> Volts</b>	<b>Load Current <math>I_L</math> Amps</b>	<b>Armature Current <math>I_a</math> Amps</b>	<b>Copper losses <math>I_a^2 R_a</math> Watts</b>	<b>Total losses <math>W_i + W_c</math> Watts</b>	<b>Input Power <math>V_L I_L</math> Watts</b>	<b>Output Power I/P -losses Watts</b>	<b>Efficiency <math>\eta</math> %</b>
1								
2								
3								
4								

**FORMULA:**

$$\text{Constant Losses } W_c = V_o - (I_o - I_f)^2 R_a \text{ Watts}$$

**As a Motor:**

$$\text{Input power} = V_L I_L \text{ Watts}$$

$$I_a = I_L - I_f \text{ Amps}$$

$$\text{Armature Cu loss} = I_a^2 R_a \text{ Watts}$$

$$\text{Total Loss} = W_c + \text{Cu loss Watts}$$

$$\text{Output power} = \text{Input} - \text{Total loss Watts}$$

$$\% \text{ Efficiency} = \text{Output/Input} * 100$$

**As a Generator:**

$$I_a = I_L + I_f \text{ Amps}$$

$$\text{Armature Cu loss} = I_a^2 R_a \text{ Watts}$$

$$\text{Total Loss} = W_c + \text{Cu loss Watts}$$

$$\text{Output power} = V_L I_L \text{ Watts}$$

$$\text{Input power} = \text{Output} + \text{Total loss Watts}$$


$$\% \text{ Efficiency} = \text{Output/Input}$$

(ii) As a Generator:

SL. NO	Load Voltage $V_L$ Volts	Load Current $I_L$ Amps	Armature Current $I_a$ Amps	Copper losses $I_a^2 R_a$ Watts	Total losses $W_i + W_c$ Watts	Output Power $V_L I_L$ Watts	Input Power $O/p + \text{losses}$ Watts	Efficiency $\eta$ %
1								
2								
3								
4								

**MODEL GRAPH:**

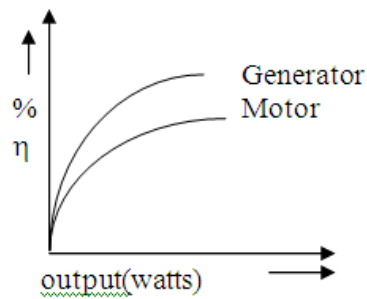1. Output power Vs efficiency ( as a motor)
2. Output power Vs efficiency ( as a generator)






**MODEL CALCULATION:**

**RESULT:**

**CIRCUIT DIAGRAM:**

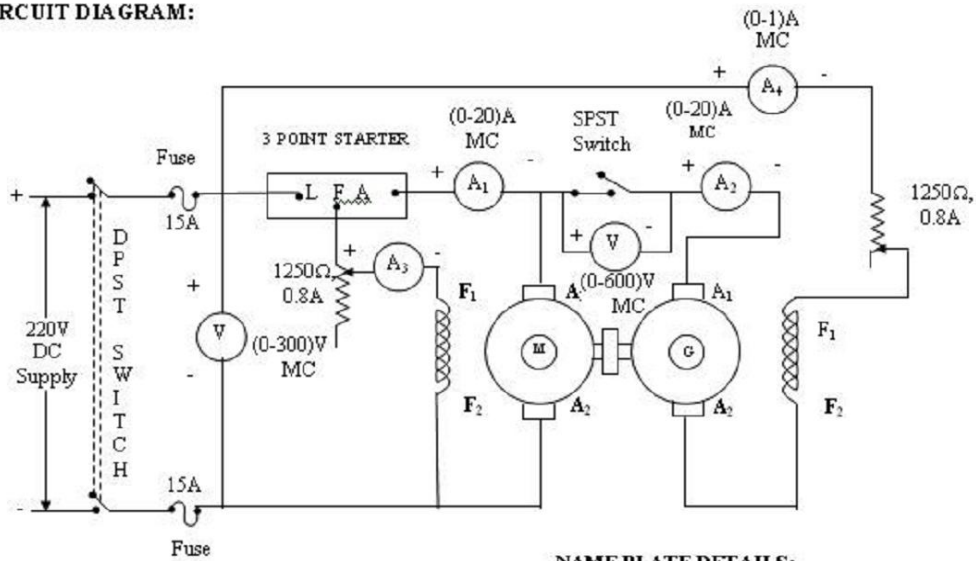

**NAME PLATE DETAILS:**

SHUNT MOTOR

SHUNT GENERATOR

Rated Voltage : 220V  
 Rated Current : 21A  
 Rated Power : 3.5KW  
 Rated Speed : 1500 rpm

220V  
 21A  
 7.5KW  
 1500rpm

**TABULAR COLUMNS:**

Motor			Generator			Armature Cu Loss of Generator	Armature Cu Loss of Motor	Shunt Cu loss of generator
V <sub>m</sub> Volts	I <sub>m</sub> Amps	I <sub>fm</sub> Amps	V <sub>g</sub> Volts	I <sub>g</sub> Amps	I <sub>fg</sub> Amps	(I <sub>g</sub> + I <sub>fg</sub> ) <sup>2</sup> R <sub>a</sub> Watts	(I <sub>g</sub> +I <sub>m</sub> -I <sub>fg</sub> ) <sup>2</sup> R <sub>a</sub> Watts	V <sub>g</sub> I <sub>fg</sub> Watts

EXP NO: 6

DATE :

**HOPKINSON'S TEST**

**AIM:**

To conduct the Hopkinson's test on the given pair of DC machines and to obtain the performance curve.

**APPARATUS REQUIRED:**


SL.NO	APPARATUS	RANGE	TYPE	QTY
1	Voltmeter	0 – 600 V	MC	1
2	Voltmeter	0 – 300 V	MC	2
3	Ammeter	0 – 20 A	MC	2
4	Ammeter	0 – 2 A	MC	2
5	Tachometer		Digital	1
6	SPST knife switch			1

**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. The supply is switched ON by closing the DPST switch.
3. The motor is started using three point starter.
4. The direction of rotation of the motor is checked if it is proper otherwise the field terminals of the motor are interchanged.
5. The field rheostat of the motor is adjusted till the motor attains its rated speed.
6. The field rheostat of the generator of the generator till the voltmeter connected across the SPST switch reads zero.
7. The SPST switch is closed.
8. The readings of the ammeter and voltmeter are noted and tabulated.

**MODEL GRAPH:**

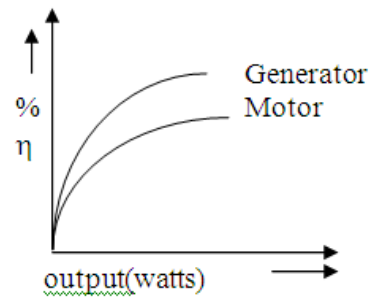1. Output power Vs efficiency ( as a motor)
2. Output power Vs efficiency ( as a generator)




**FORMULAE:**

1. Armature Cu loss of generator =  $(I_g + I_f)^2 R_a$  Watts
2. Armature Cu loss of motor =  $(I_g + I_m - I_{fm})^2 R_a$  Watts
3. Shunt Cu loss of generator =  $V_g I_f$  Watts
4. Shunt Cu loss of motor =  $V_m I_{fm}$  Watts
5. Power drawn from supply =  $V_m I_m$  Watts
6. Stray loss  $W_c = V_m I_m - \{(I_g + I_f)^2 R_a + (I_g + I_m - I_{fm})^2 R_a + V_g I_f + V_m I_{fm}\}$  Watts
7. Stray loss of single machine =  $W_c/2$
8. Total loss in generator =  $W_c/2 + (I_g + I_f)^2 R_a + V_g I_f$  Watts
9. Total loss in motor =  $V_m I_{fm} + (I_g + I_m - I_{fm})^2 R_a + W_c/2$  Watts
10. Output of generator =  $V_g I_g$  Watts
11. Input of generator = Output + losses
12. Efficiency of generator =  $\text{output power}/\text{input power} * 100 \%$
13. Input to the motor =  $V_m (I_g + I_m)$  Watts
14. Output power of motor = Input – losses Watts
15. Efficiency of motor =  $\text{Output power}/\text{Input power} * 100\%$

**RESULT:**

**CIRCUIT DIAGRAM**

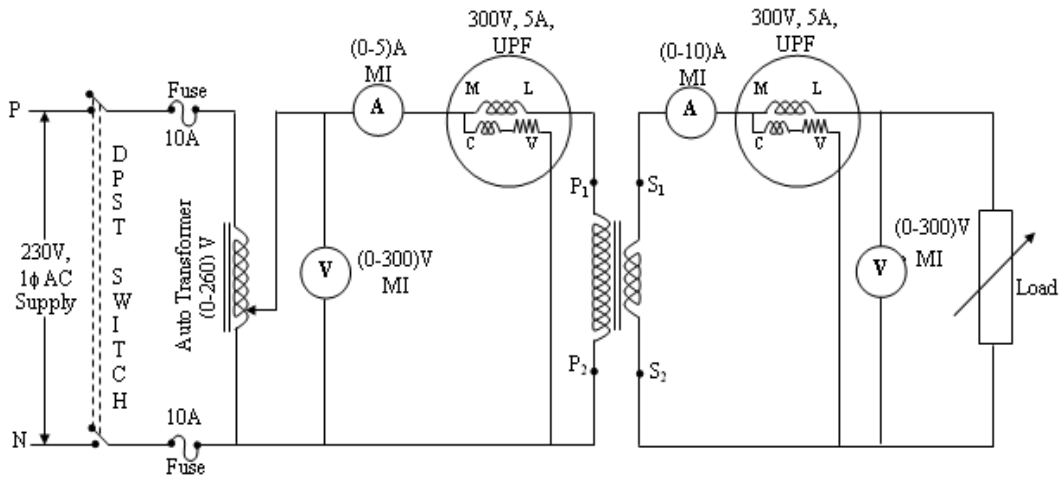

**FUSE RATINGS**

**NAME PLATE DETAILS:**

**TABULAR COLUMN:**

S.No	Load	Primary			Secondary			Input Power $W_1 \times MF$	Output Power $W_2 \times MF$	Efficiency $\eta$ %	% Regulation
		$V_1$ (Volt)	$I_1$ (Amp)	$W_1$ (Watt)	$V_2$ (Volts)	$I_2$ (Amp)	$W_2$ (Watt)				

EXP NO: 7(a)

DATE:

**LOAD TEST ON A SINGLE PHASE TRANSFORMER**

**AIM:**

To conduct load test on single phase transformer and to find efficiency and percentage regulation.


**APPARATUS REQUIRED:**

S.No.	Apparatus	Range	Type	Quantity
1	Ammeter	(0-10)A & (0-5) A	MI	2
2	Voltmeter	(0-150)V & (0-300) V	MI	2
3	Wattmeter	(300V, 5A) & (150V, 5A)	Upf	2
4	Auto Transformer	1 $\phi$ , (0-260)V	-	1
5	Resistive Load	5KW, 230V	-	1
6	Connecting Wires	2.5sq.mm	Copper	Few

**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. After checking the no load condition, minimum position of auto transformer and DPST switch is closed.
3. Ammeter, Voltmeter and Wattmeter readings on both primary side and secondary side are noted.
4. The load is increased and for each load, Voltmeter, Ammeter and Wattmeter readings on both primary and secondary sides are noted.
5. Again no load condition is obtained and DPST switch is opened.

**MODEL GRAPHS:**

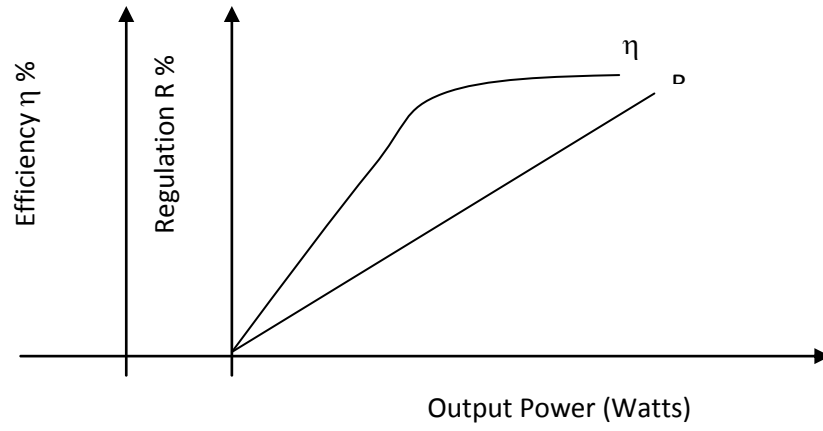



**FORMULAE:**

Output Power =  $W_2$  x Multiplication factor

Input Power =  $W_1$  x Multiplication factor


$$\text{Efficiency } \eta \% = \frac{\text{Output Power}}{\text{Input Power}} \times 100\%$$

$$\text{Regulation R \%} = \frac{V_{NL} - V_{FL}(\text{Secondary})}{V_{NL}} \times 100\%$$

**RESULT:**

**CIRCUIT DIAGRAM:**

**OPEN CIRCUIT TEST:**

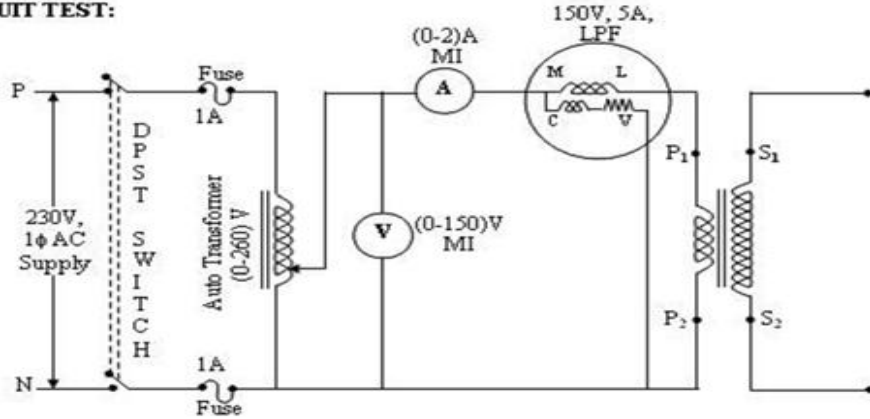

**FUSE RATING:**

10% of rated current  

$$\frac{10 \times 5}{100} = 0.5A$$

**NAME PLATE DETAILS:**

	<u>Primary</u>	<u>Secondary</u>
Rated Voltage :	115V	230V
Rated Current :	10A	5A
Rated Power :	1KVA	1KVA

**TABULAR COLUMN**

**OPEN CIRCUIT TEST:**

multiplication factor=

S.NO	Vo(volts)	Io(amps)	Wo(watts)	
			Observed	Actual(mf* Observed )

EXP NO :8

DATE :

**OPEN CIRCUIT & SHORT CIRCUIT TEST ON A SINGLE PHASE  
TRANSFORMER**

**AIM:**

To predetermine the efficiency and regulation of a transformer by conducting open circuit test and short circuit test and to draw equivalent circuit.

**APPARATUS REQUIRED:**

S.No.	Apparatus	Range	Type	Quantity
1	Ammeter	(0-2)A	MI	1
		(0-5) A	MI	1
2	Voltmeter	(0-150)V	MI	2
3	Wattmeter	(150V, 5A)	LPF	1
		(150V, 5A)	UPF	1
4	Connecting Wires	2.5sq.mm	Copper	Few

**PROCEDURE:**


**OPEN CIRCUIT TEST:**

1. Connections are made as per the circuit diagram.
2. After checking the minimum position of Autotransformer, DPST switch is closed.
3. Auto transformer variac is adjusted get the rated primary voltage.
4. Voltmeter, Ammeter and Wattmeter readings on primary side are noted.
5. Auto transformer is again brought to minimum position and DPST switch is opened.

**SHORT CIRCUIT TEST:**

1. Connections are made as per the circuit diagram.
2. After checking the minimum position of Autotransformer, DPST switch is closed.
3. Auto transformer variac is adjusted get the rated primary current.
4. Voltmeter, Ammeter and Wattmeter readings on primary side are noted.
5. Auto transformer is again brought to minimum position and DPST switch is opened

**SHORT CIRCUIT TEST:**

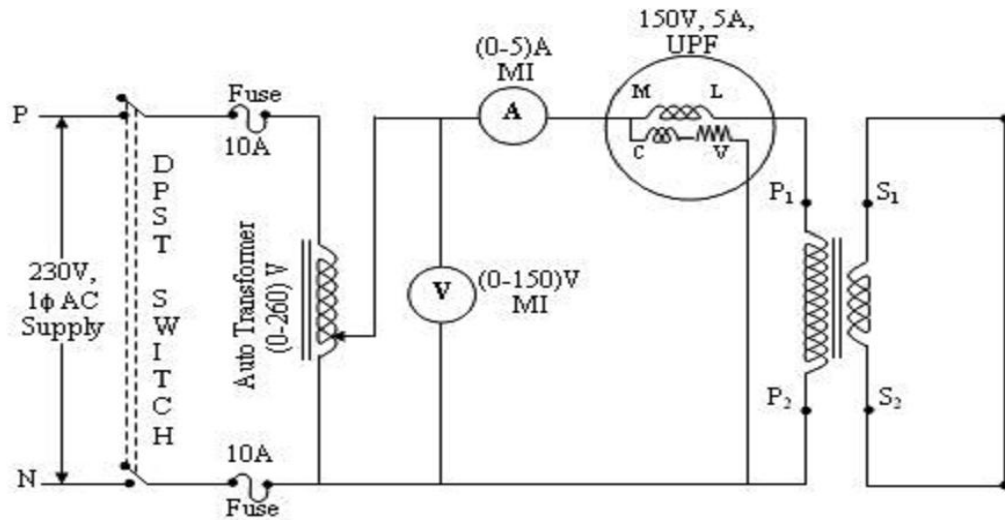

**FUSE RATING:**

125% of rated current

$$\frac{125 \times 5}{100} = 6.25A$$

**NAME PLATE DETAILS:**

	<u>Primary</u>	<u>Secondary</u>
Rated Voltage :	230V	115V
Rated Current :	5A	10A
Rated Power :	1KVA	1KVA

**SHORT CIRCUIT TEST:**

multiplication factor=

S.NO	Vsc(volts)	Isc(amps)	Wsc(watts)	
			Observed	Actual(mf* Observed )

## FORMULAE USED:

### 1. OC Test

$$W_0 = V_0 I_0 \cos \Phi_0$$

$$I_w = I_0 \cos \Phi_0$$

$$I_\mu = I_0 \sin \Phi_0$$

$$R_0 = V_0 / I_w$$

voltage

$$X_0 = V_0 / I_\mu$$

Where,

$W_0$  - no load power

$I_0$  - no load current

$V_0$  - no load voltage

$R_0$  - circuit resistance

$X_0$  - circuit reactance

$\cos \Phi_0$  - PF between no load current and

$I_w$  - working current component

$I_\mu$  - Magnetizing current component

### 1. SC Test

$$W_{sc} = V_{sc} I_{sc} \cos \Phi_{sc}$$

$$R_{01} = V_{sc} / I_{sc}^2$$

$$Z_{01} = V_{sc} / I_{sc}$$

$$X_{01} = \text{square root of } Z_a^2 - R_a^2$$

$W_{sc}$  = Short circuit power

$V_{sc}$  = Short circuit voltage

$I_{sc}$  = Short circuit current

$R_{01}$  = Total effective resistance

$Z_{01}$  = total effective impedance

### % Regulation

1) % lagging power factor =  $I_{sc} [R_{01} \cos \Phi_0 + X_{01} \sin \Phi_0] * 100 / V_0$

2) % leading power factor =  $I_{sc} [R_{01} \cos \Phi_0 - X_{01} \sin \Phi_0] * 100 / V_0$

3) Efficiency =  $\frac{x * KVA * PF}{[x * KVA * PF] + W_0 + x^2 V_{sc}}$

$X_{01}$  = total effective reactance


**TABULATION FOR EFFICIENCY**

$I_2 =$        $V_2 =$

S.NO	LOAD(X)	COS $\Phi$	I/P POWER $P_i = XV_2 I_2 \text{COS } \Phi + W_0 + X^2 W_{sc}$	O/P POWER $P_o = XV_2 I_2 \text{COS } \Phi +$	EFFICENCY $\eta = P_o / P_i$
1	Half load 0.5				
2	Full				

**MODEL GRAPHS:**


1. Output power Vs efficiency

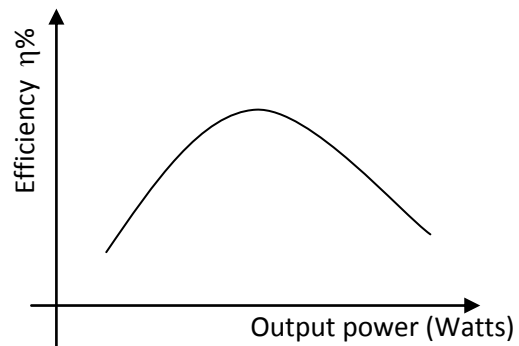

**MODEL CALCULATION:**

**RESULT:**

**CIRCUIT DIAGRAM:**

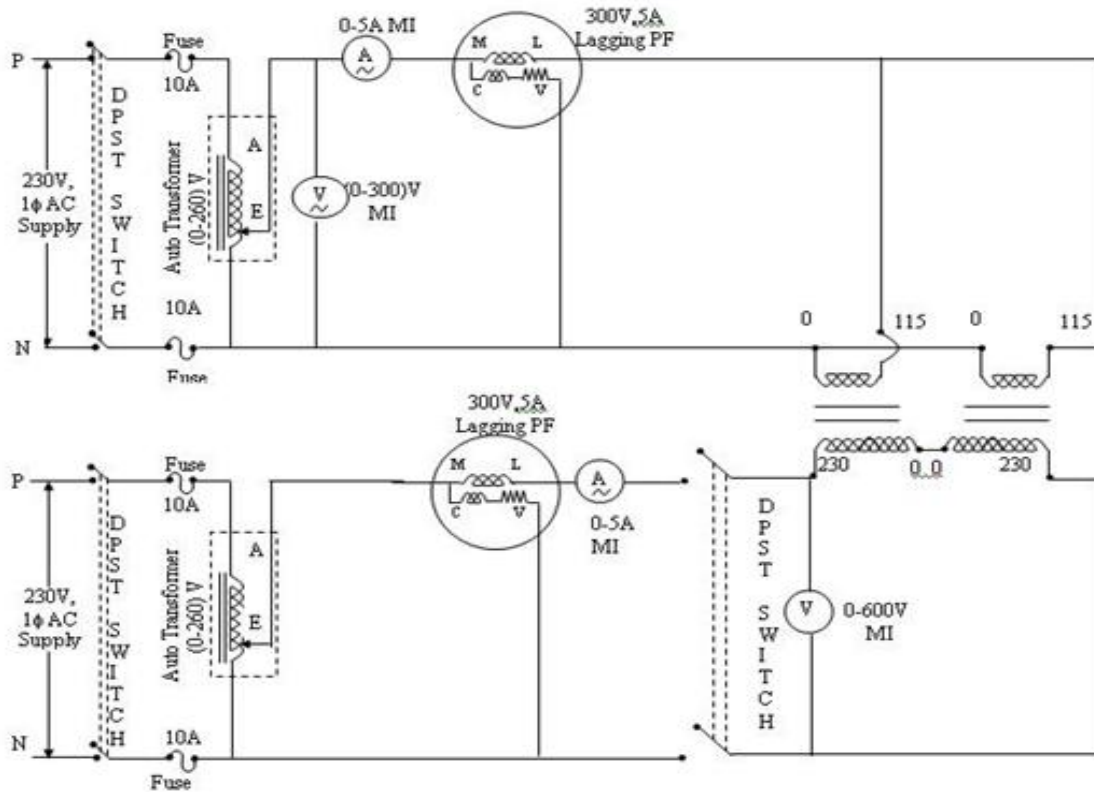

**NAME PLATE DETAILS**

**FUSE RATING**

**TABULAR COLUMNS:**

TFR.1 Current $I_1$ A	TFR.2 Current $I_2$ A	TFR.1 Voltage $V_1$ V	TFR.2 Voltage $V_2$ V	TFR.1 $W_1$ Watts	TFR.2 $W_2$ Watts



EXP NO : 9

DATE :

**SUMPNERS TEST**

**AIM:**

To predetermine the efficiency of the transformer at any desired load and power factor by conducting the Sumpners test.

**APPARATUS REQUIRED:**

SL.NO.	APPARATUS	TYPE	RANGE	QUANTITY
1.	Ammeter	MI	0 – 1 A	1
		MI	0 – 5 A	1
2.	Voltmeter	MI	0 – 300 V	1
		MI	0 – 600 V	1
		MI	0 – 150 V	1
3.	Wattmeter	LPF	300 V/2.5A	1
		UPF	150 V/5A	1
4	Transformer	Single phase	1 KVA 230/230 – 115 V	2
5.	Autotransformer	Single phase	230 V/0 – 270 V	2
6.	SPST knife switch			1

**PROCEDURE:**

1. Connect as per the circuit diagram.
2. Close the DPST switch.
3. Adjust the variac of the auto transformer connected to transformer 1 to get the rated voltage.
4. Note down the reading of ammeter, voltmeter & wattmeter of transformer1.
5. Close the SPST switch if the voltmeter connected across the SPST switch reads zero. It not the interchange the terminals of second transformer secondary to get zero reading at SPST switch.
6. Adjust the variac of the auto transformer connected to transformer 2 to get the rated current.
7. Note down the reading of ammeter, voltmeter & wattmeter of transformer2
8. Bring the auto transformer variac to zero position & switch off the supply.

## PREDETERMINATION OF EFFICIENCY AT DIFFERENT LOADS

(i) At Unity Power Factor

Load Current I Amps	% of full load X (as decimal fraction)	Core Losses $W_i = W_1/2$ Watts	Copper losses $W_C = W_2 /2 * X^2$ Watts	Total Losses $W_i + W_C$ Watts	Output Power Watts	Input Power Watts	Efficiency $\eta$ %
	¼ (0.25)						
	½ (0.5)						
	¾ (0.75)						
	1(full load)						

(ii) At 0.8 Power Factor (Lag)

Load Current I Amps	% of full load X (as decimal fraction)	Core Losses $W_i = W_1/2$ Watts	Copper losses $W_C = W_2 /2 * X^2$ Watts	Total Losses $W_i + W_C$ Watts	Output Power Watts	Input Power Watts	Efficiency $\eta$ %
	¼ (0.25)						
	½ (0.5)						
	¾ (0.75)						
	1(full load)						

## FORMULAE:

Core losses  $W_i = W_1/2$  Watts

Copper losses,  $W_c = W_2/2 * X^2$  (Watts)

Where,  $X$  = percentage of Load

Total losses =  $W_c + W_i$  Watts


Output power =  $KVA * 100 * X * p.f$  Watts

Input power = Output power + losses Watts

Efficiency =  $Output / Input * 100$

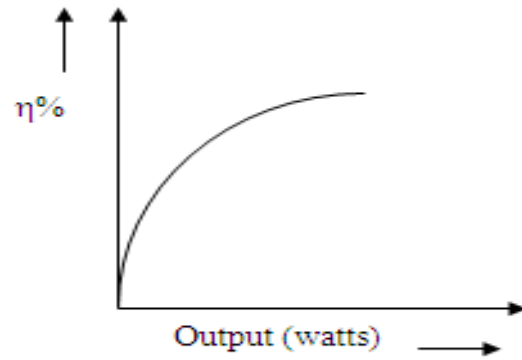**GRAPH:**


Output power Vs Efficiency at UPF and 0.8 power factor.



**MODEL CALCULATION:**

**RESULT:**

**CIRCUIT DIAGRAM:**

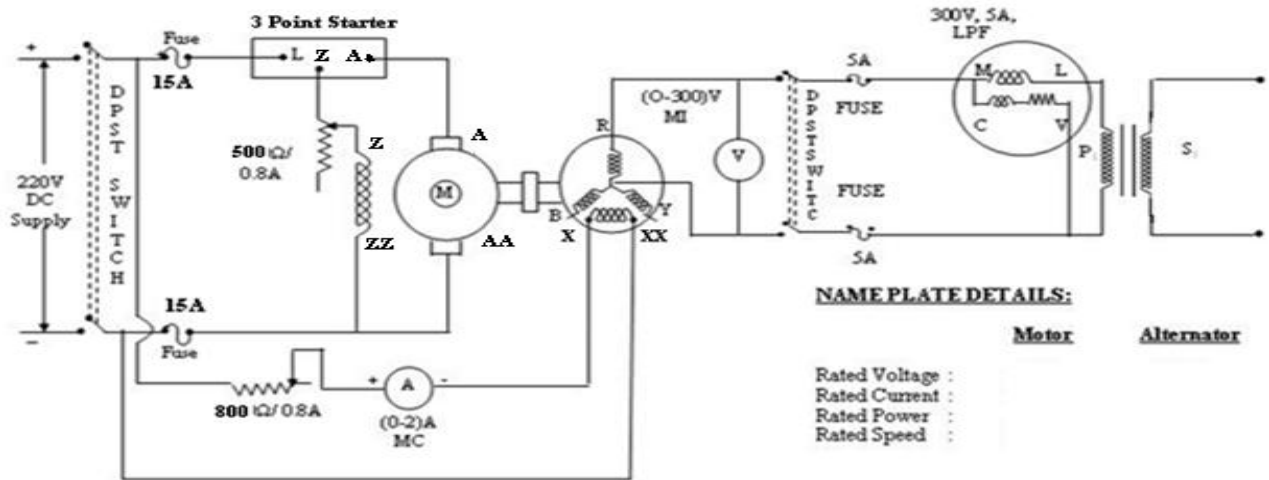

**FUSE RATING:**  
125% of rated current

**NAME PLATE DETAILS:**

**Meter**      **Alternator**

Rated Voltage :  
Rated Current :  
Rated Power :  
Rated Speed :

**NAME PLATE DETAILS:**

**Primary**      **Secondary**

Rated Voltage :  
Rated Current :  
Rated Power :

**TABULAR COLUMN:**

S.NO.	Speed N (rpm)	Frequency f (Hz)	Voltage V (Volts)	Wattmeter reading Watts	$W_i / f$ Joules	$W_h = A * f$	$W_e = B * f^2$	Total Iron loss $W_i$ (Watts) $W_i = W_h + W_e$

EXP NO: 10

DATE:

**SEPARATION OF NO LOAD LOSSES IN A SINGLE PHASE  
TRANSFORMER**

**AIM:**

To separate the eddy current loss and hysteresis loss from the iron loss of single phase transformer.


**APPARATUS REQUIRED:**

S. No.	Name of the Apparatus	Range	Type	Quantity
1	Rheostat	1250 $\Omega$ , 0.8A	Wire Wound	2
2	Wattmeter	300 V, 5A	LPF	1
3	Ammeter	(0-2) A	MC	1
4	Voltmeter	(0-300) V	MI	1
5	Connecting Wires	2.5sq.mm	Copper	Few

**PROCEDURE:**

1. Connections are given as per the circuit diagram.
2. Supply is given by closing the DPST switch.
3. The DC motor is started by using the 3 point starter and brought to rated speed by adjusting its field rheostat.
4. By varying the alternator field rheostat gradually the rated primary voltage is applied to the transformer.
5. The frequency is varied by varying the motor field rheostat and the readings of frequency are noted and the speed is also measured by using the tachometer.
6. The above procedure is repeated for different frequencies and the readings are tabulated.
7. The motor is switched off by opening the DPST switch after bringing all the rheostats to the initial position.

**MODELGRAPH:**

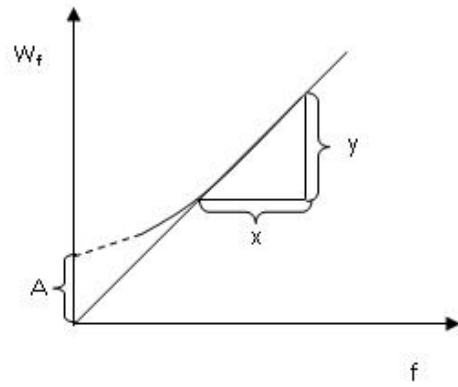



**FORMULA USED:**

1. Frequency,  $f = (P \cdot N_s) / 120$  in Hz  $P = \text{No. of Poles}$  &  $N_s = \text{Synchronous speed in rpm}$ .
2. Hysteresis Loss  $W_h = A * f$  in Watts  $A = \text{Constant (obtained from graph)}$
3. Eddy Current Loss  $W_e = B * f^2$  in Watts  $B = \text{Constant (slope of the tangent drawn to the curve)}$
4. Iron Loss  $W_i = W_h + W_e$  in Watts  
 $W_i / f = A + (B * f)$

Here the Constant A is distance from the origin to the point where the line cuts the Y- axis in the graph between  $W_i / f$  and frequency f. The Constant B is  $\Delta(W_i / f) / \Delta f$

**MODEL CALCULATION:****RESULT:**